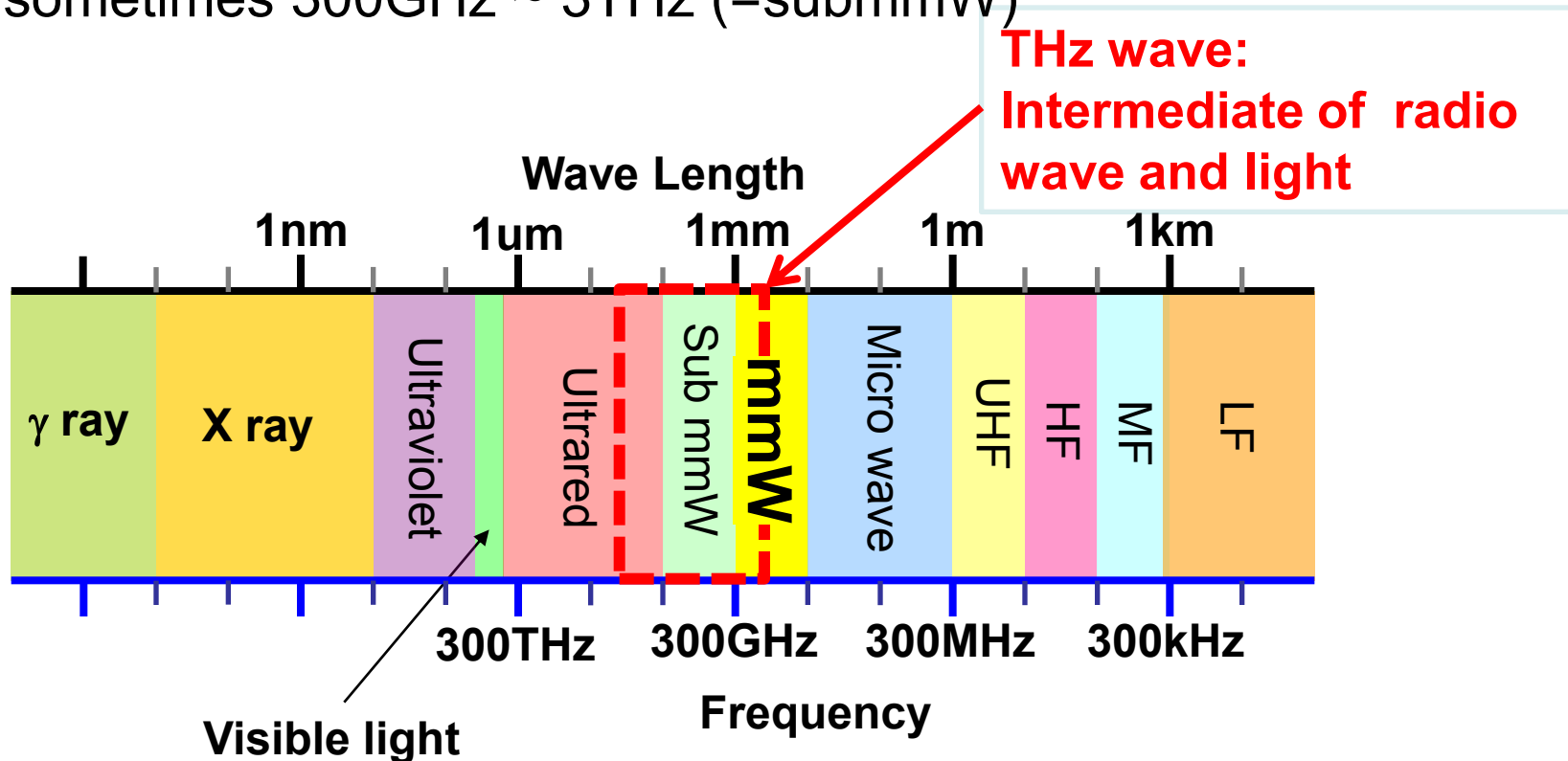


Millimeter-Wave and Terahertz CMOS Design

Minoru Fujishima

What is mmW & THz?


- Definition of millimeter wave (mmW)
 - 30GHz ~ 300GHz (wave length: 1mm ~ 10mm)
- Definition of Terahertz (THz)
 - 100GHz ~ 10THz (wave length: 30 μ m ~ 3mm)
 - sometimes 300GHz ~ 3THz (=submmW)




MOSFET Performance in THz Region

ITRS 2010
 $f_{max} = 450\text{GHz}$ (2013)
 $= 990\text{GHz}$ (2020)

MSG / MAG
 estimation

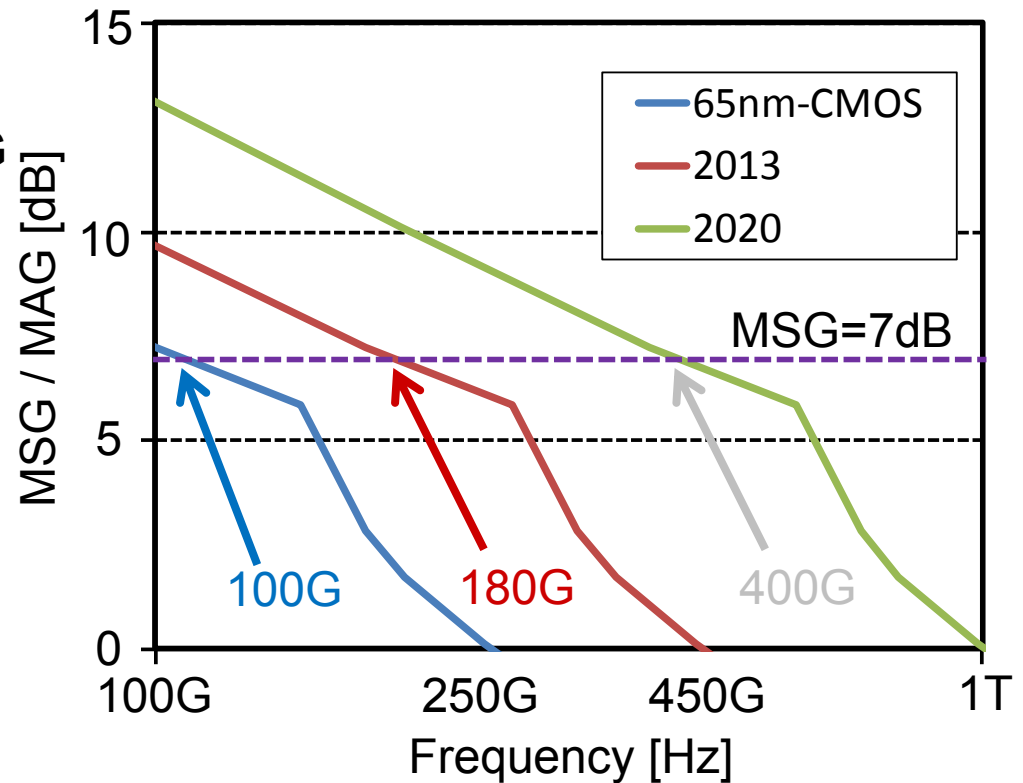


MSG=7dB

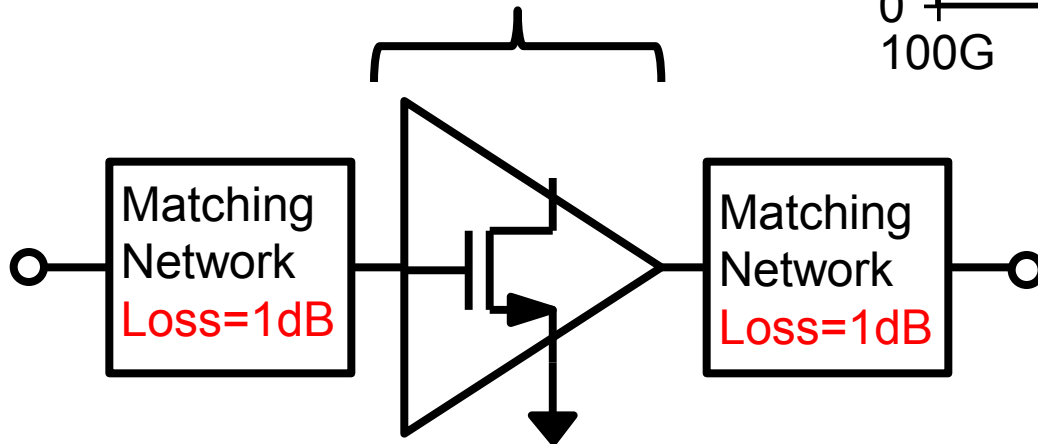


Estimated Gain of Amplifier
 Gain = 5dB @ **100GHz (65nm)**
 = 5dB @ **180GHz (2013)**
 = 5dB @ **400GHz (2020)**

Wireless Communication Trend

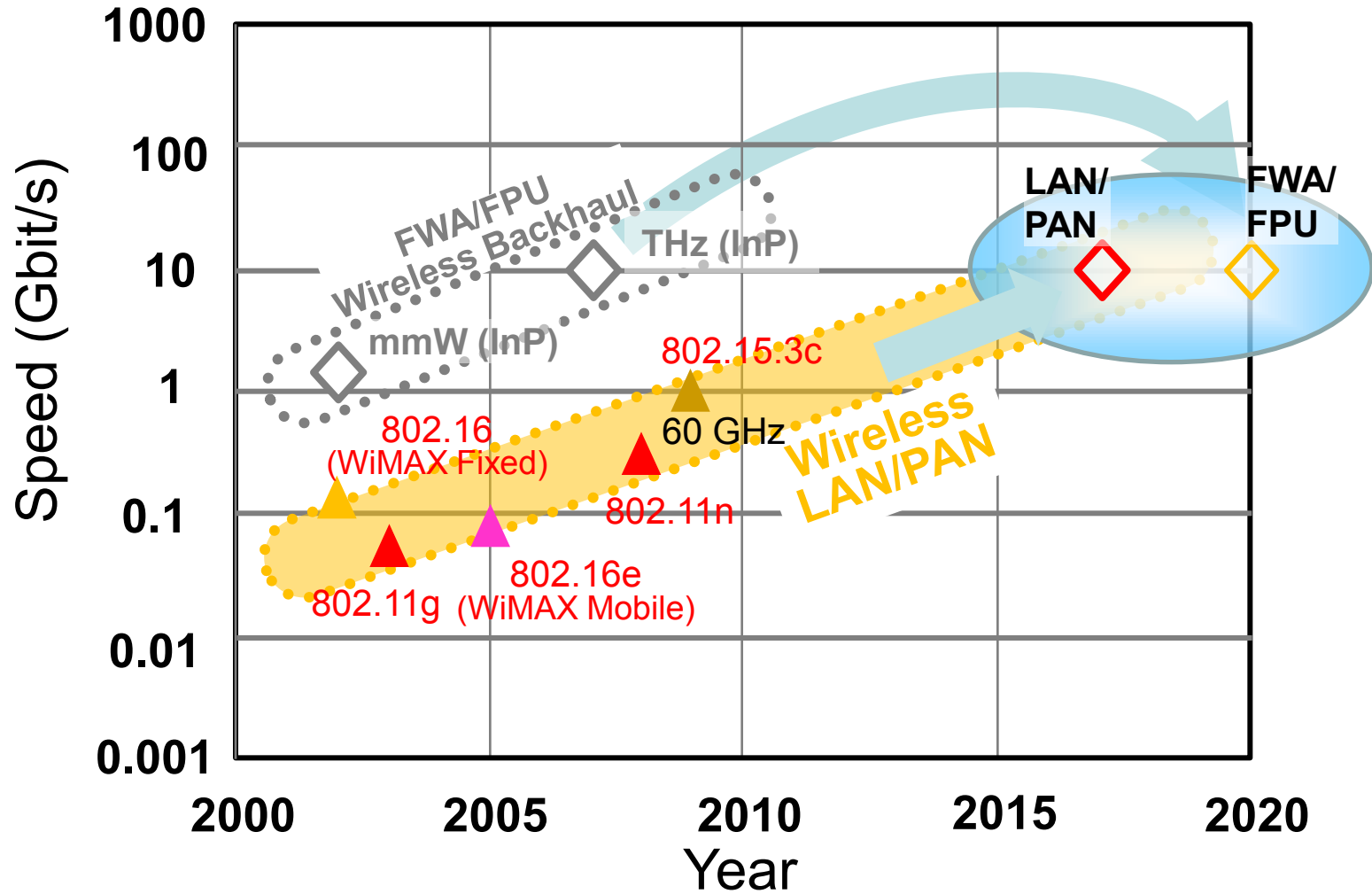

After T. Nagatsuma (Osaka Univ), Doc.: IEEE 802.15-10-0149-01-0thz

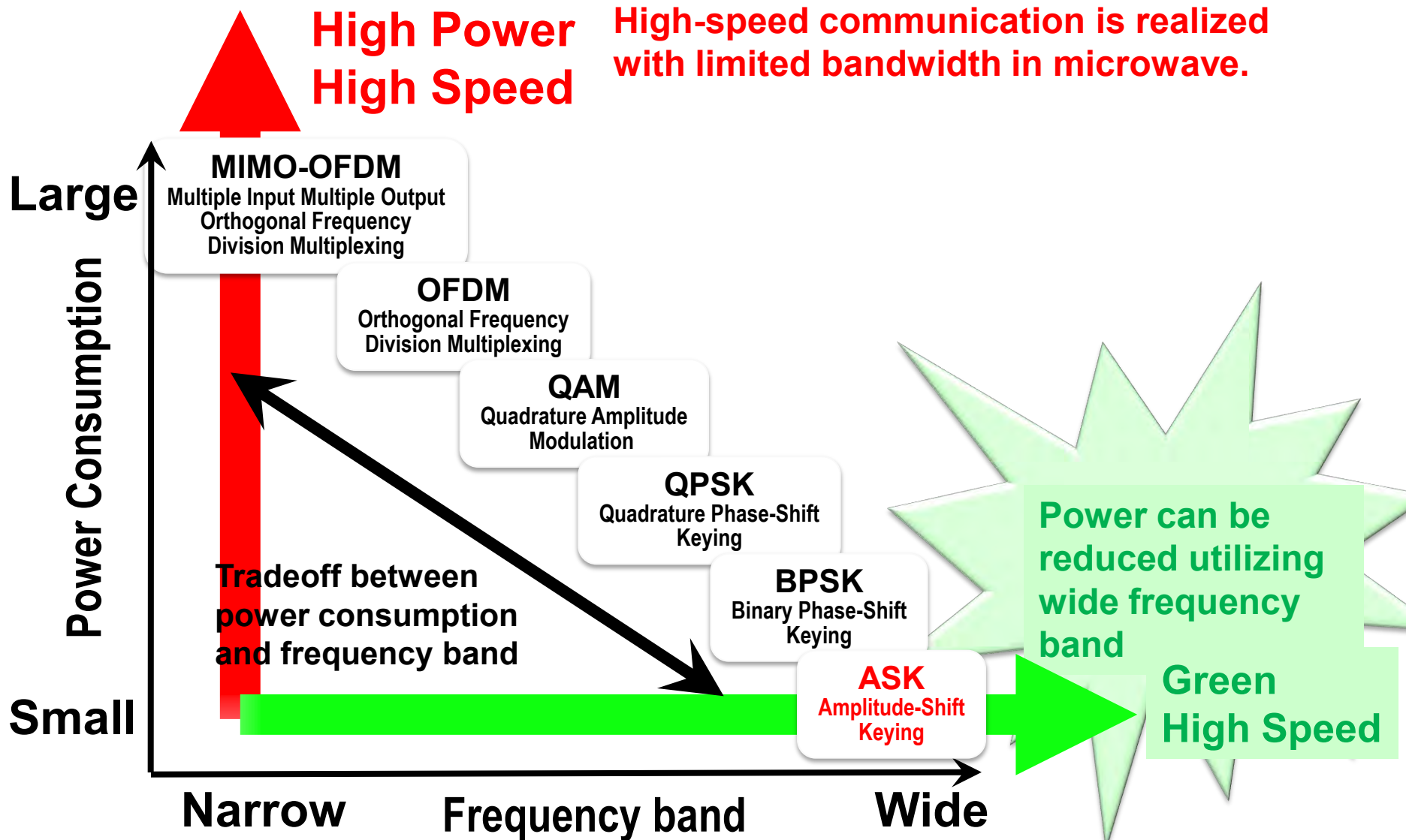
Strategies for Ultrahigh-Speed Wireless Communication




Contents

- mmW / THz CMOS Design
- 60GHz HDMI Transceiver
- 120 / 140GHz Dual Channel Receiver


Chip Development Process

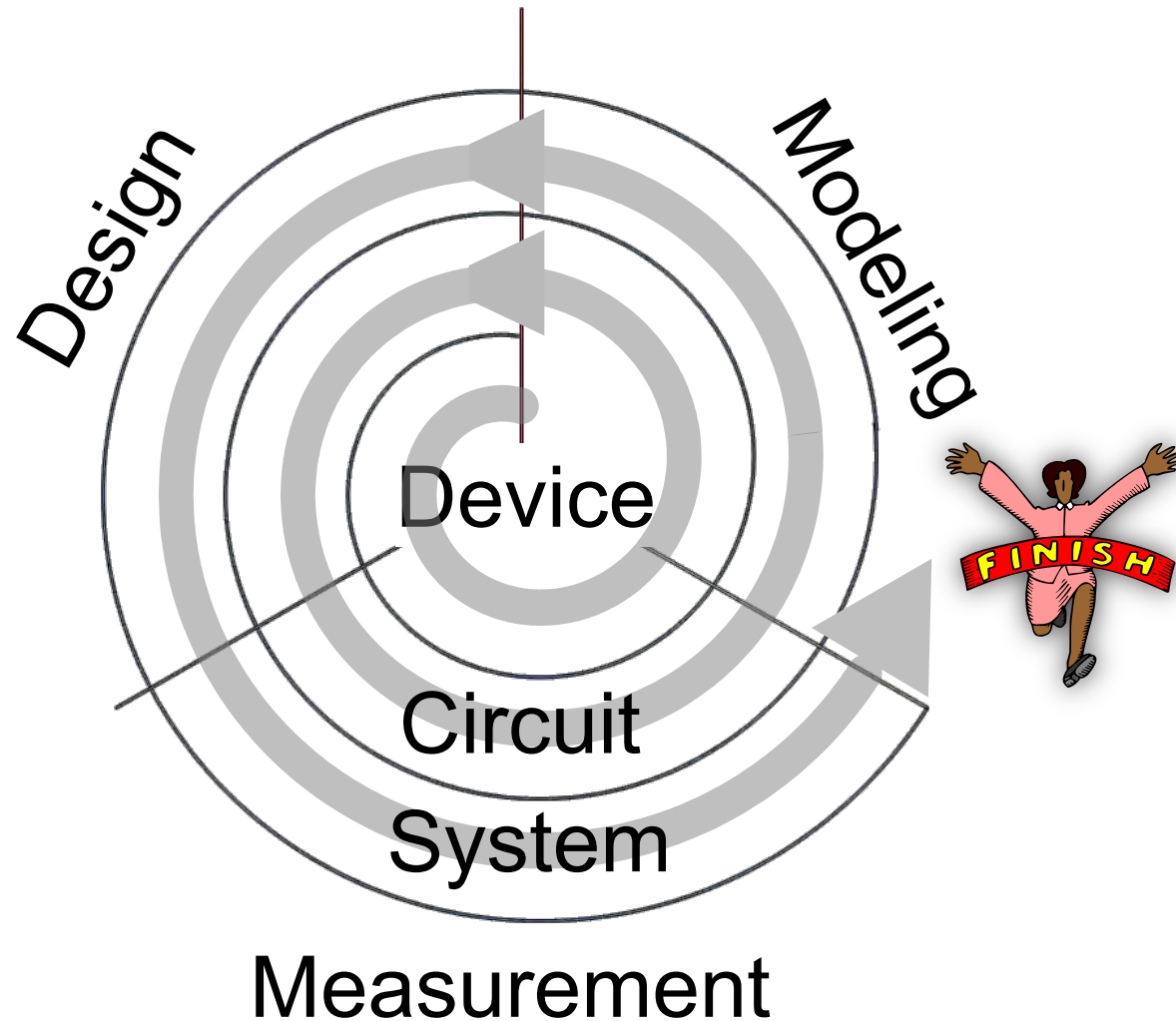



Three Development Tasks

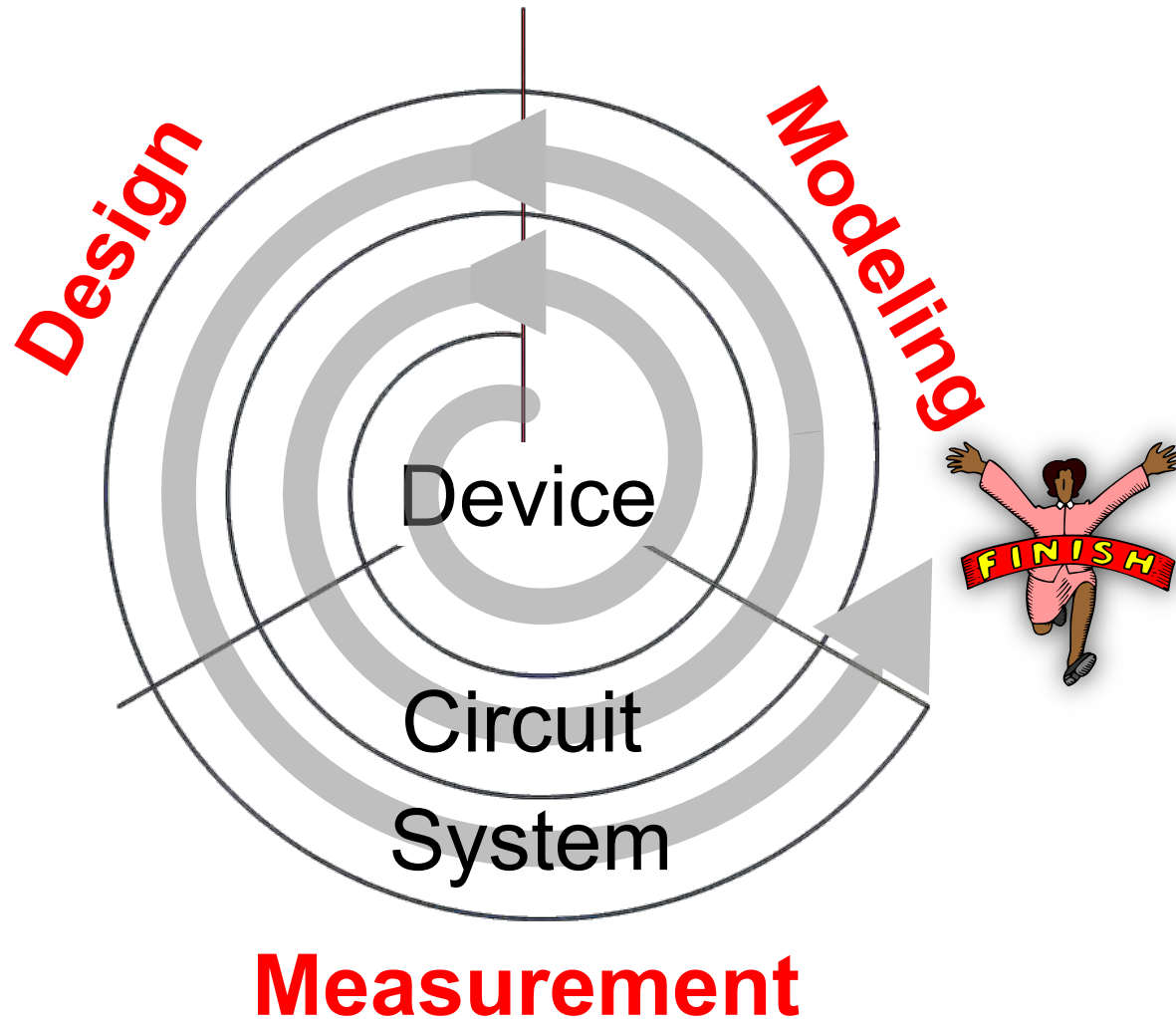


Three Development Layers

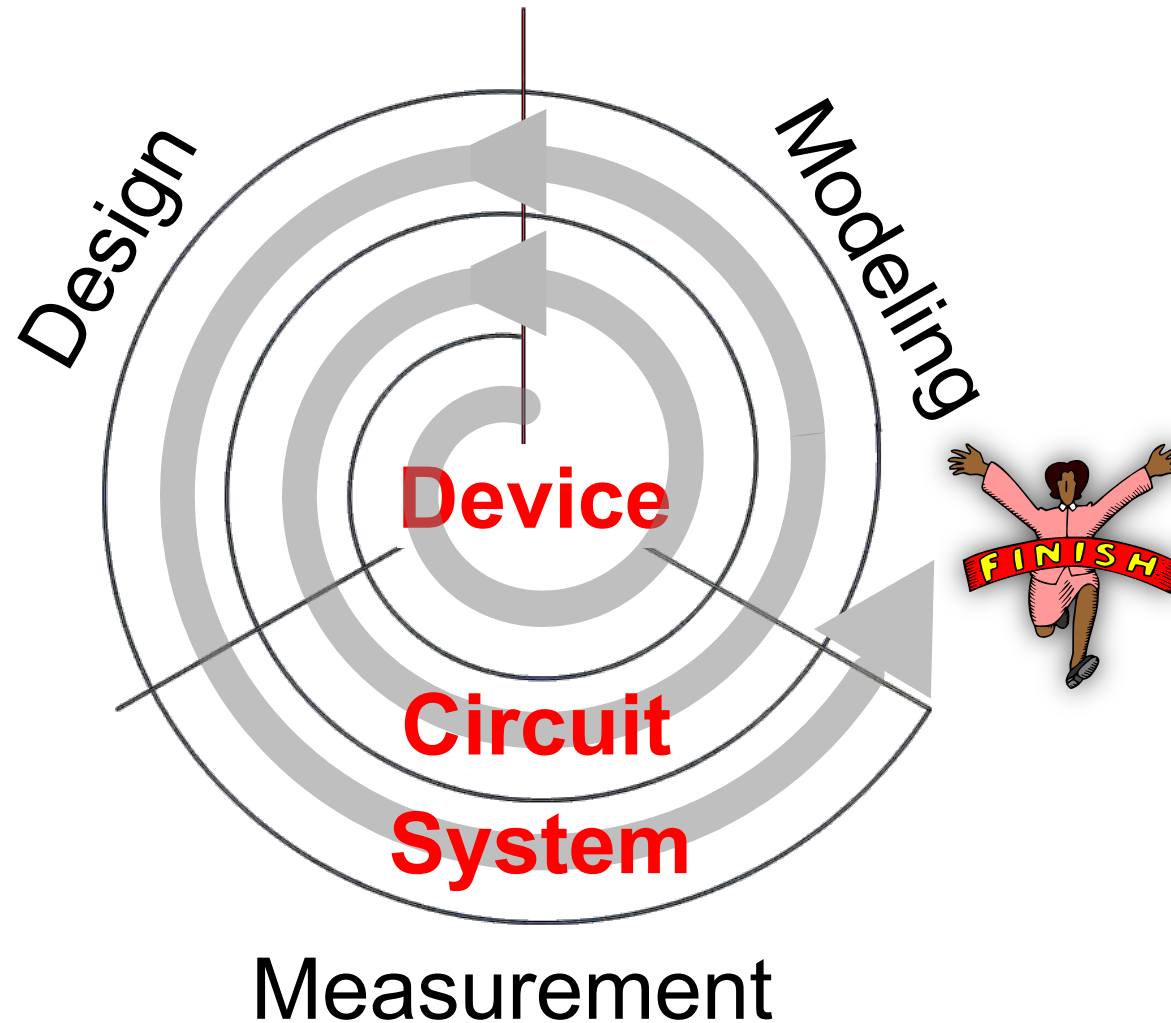

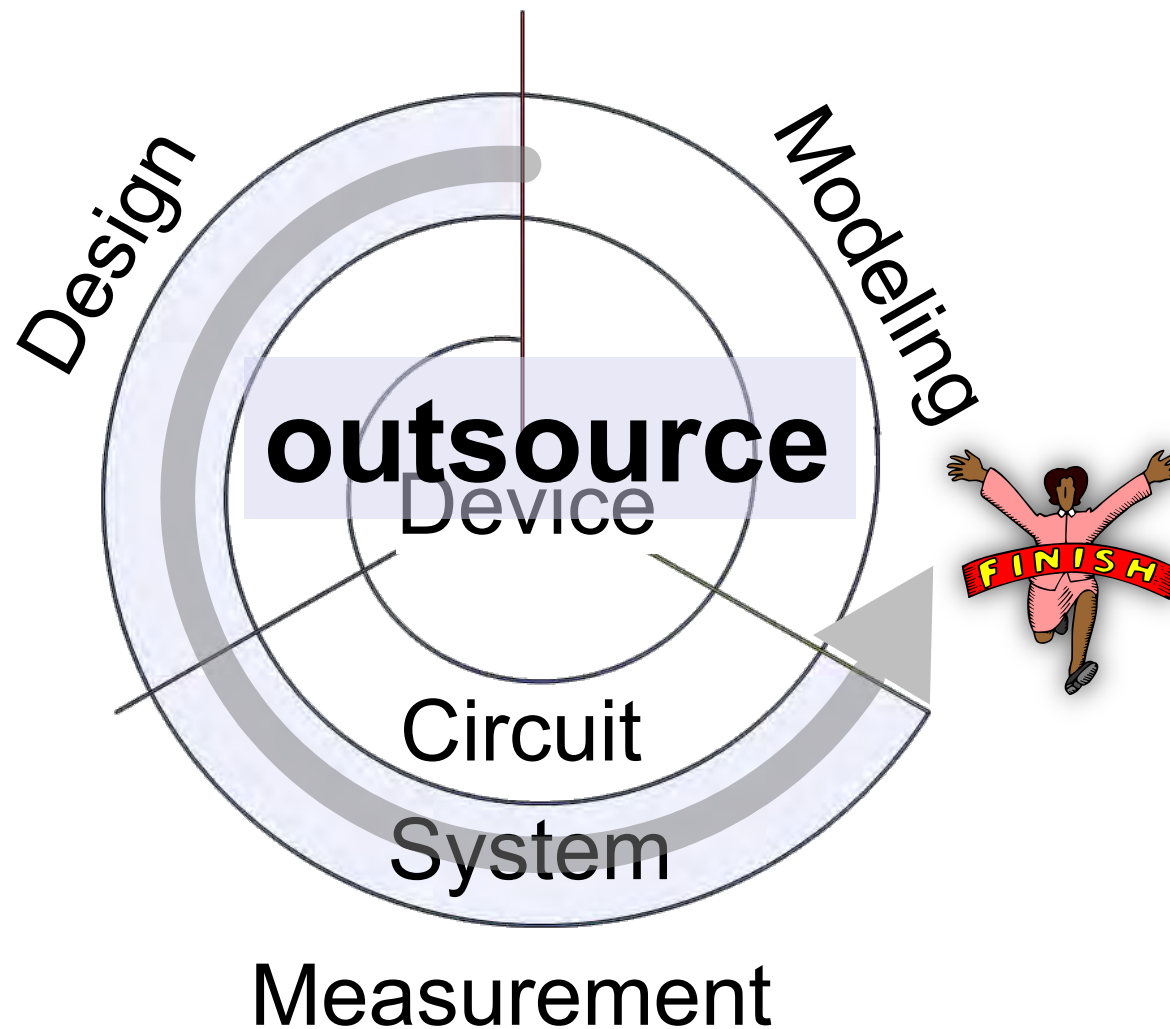


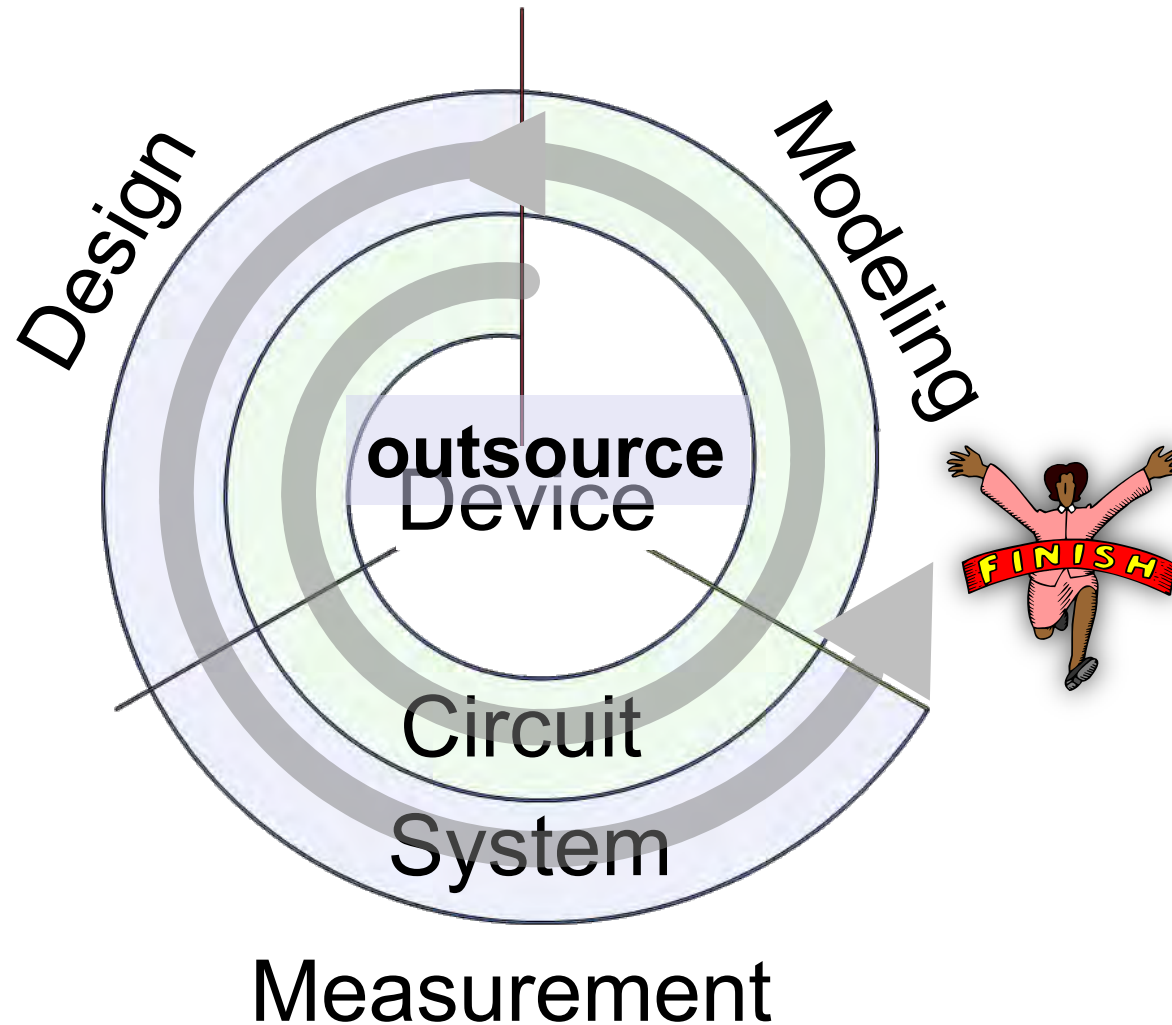

Millimeter-Wave Design



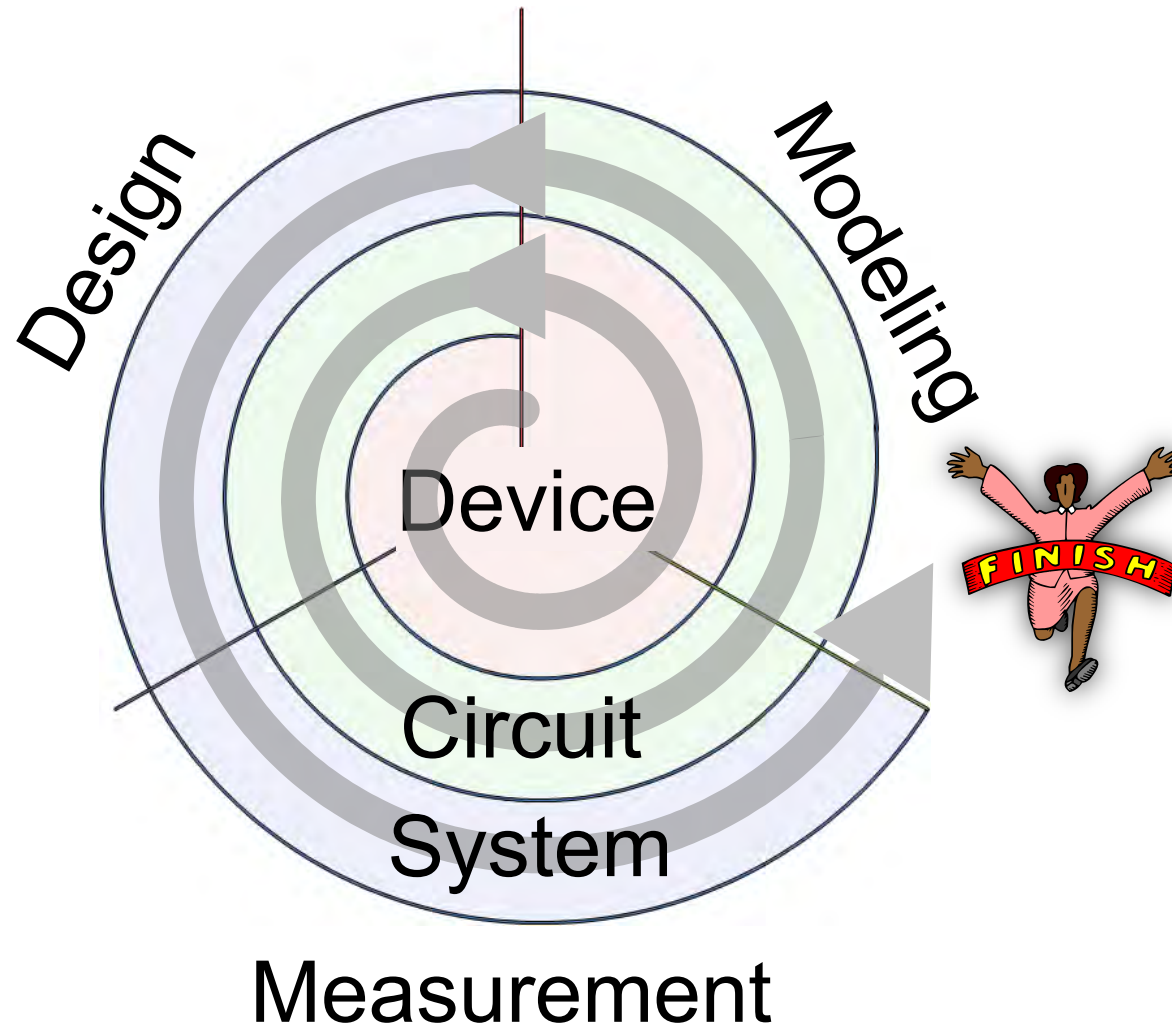


Millimeter-Wave Design



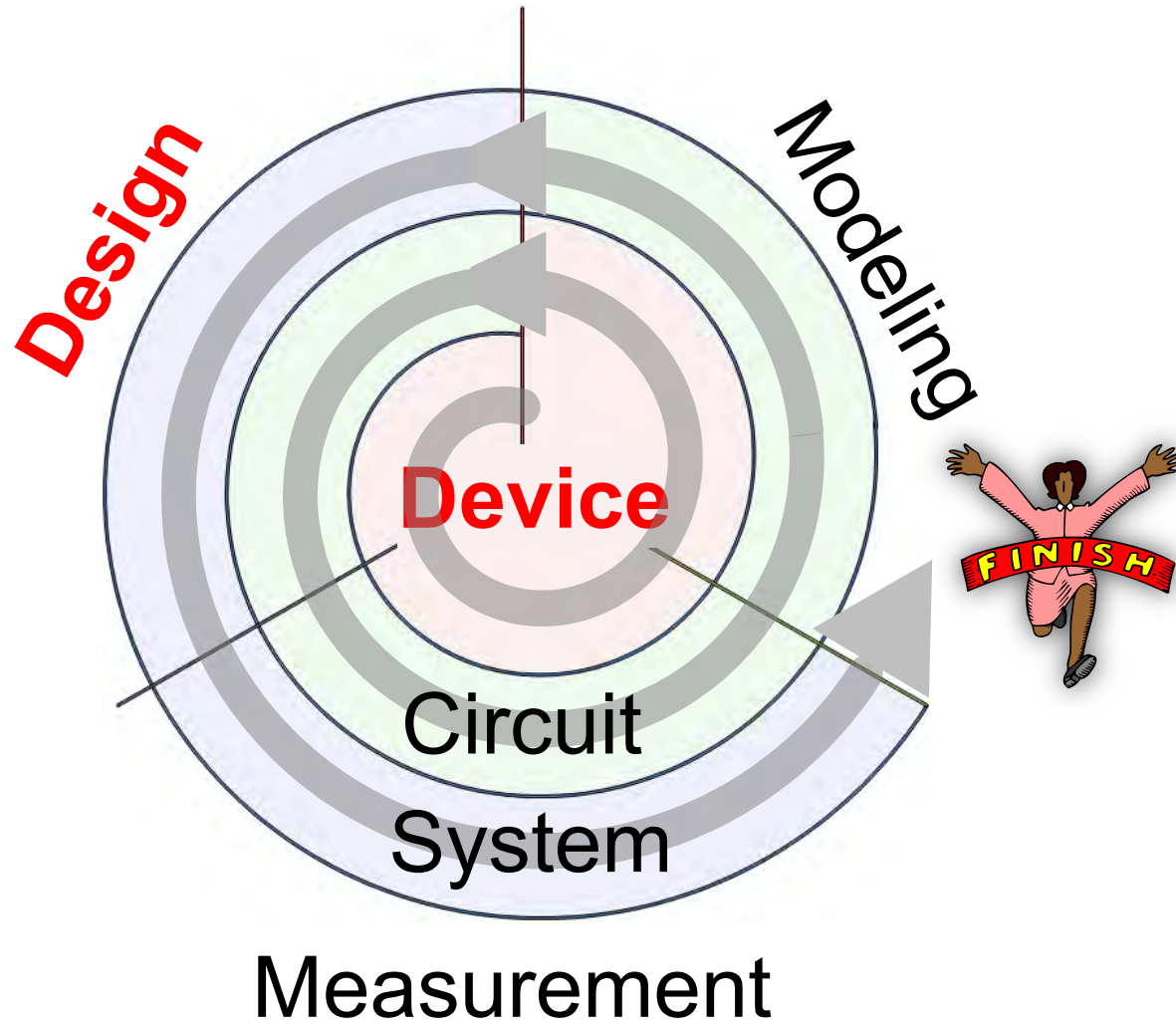


mmW Layout Issue

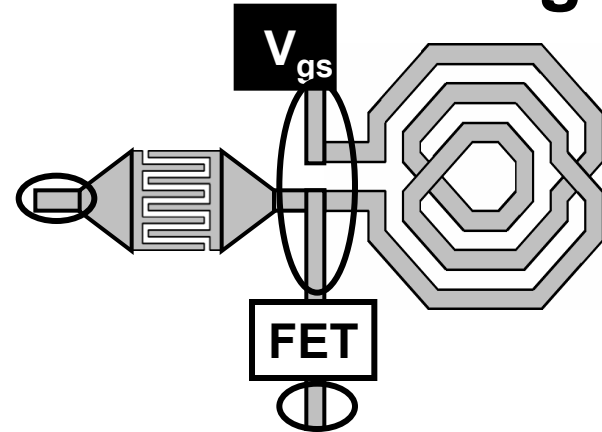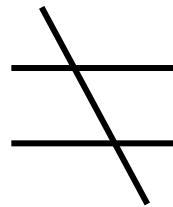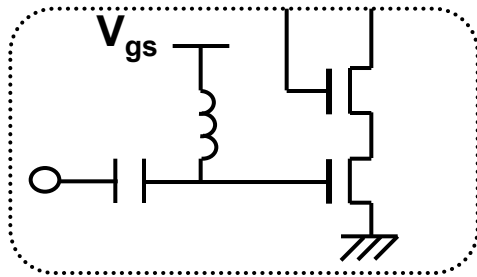- ✓ Design without transmission line for analog/RF




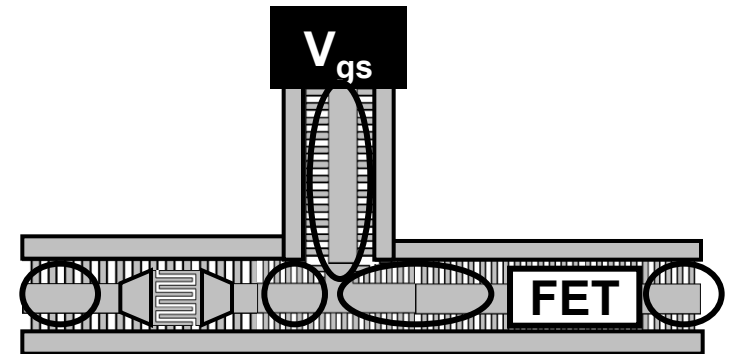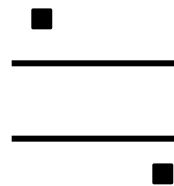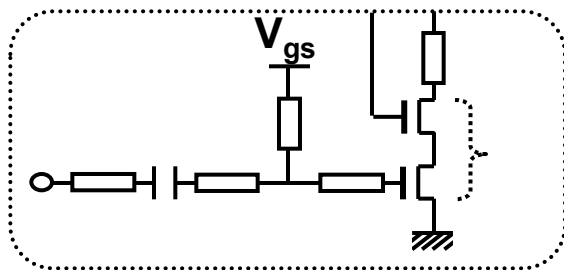- ✓ Design with transmission line for millimeter wave



Modeled transmission line is used for interconnect.

Bond-Based Design

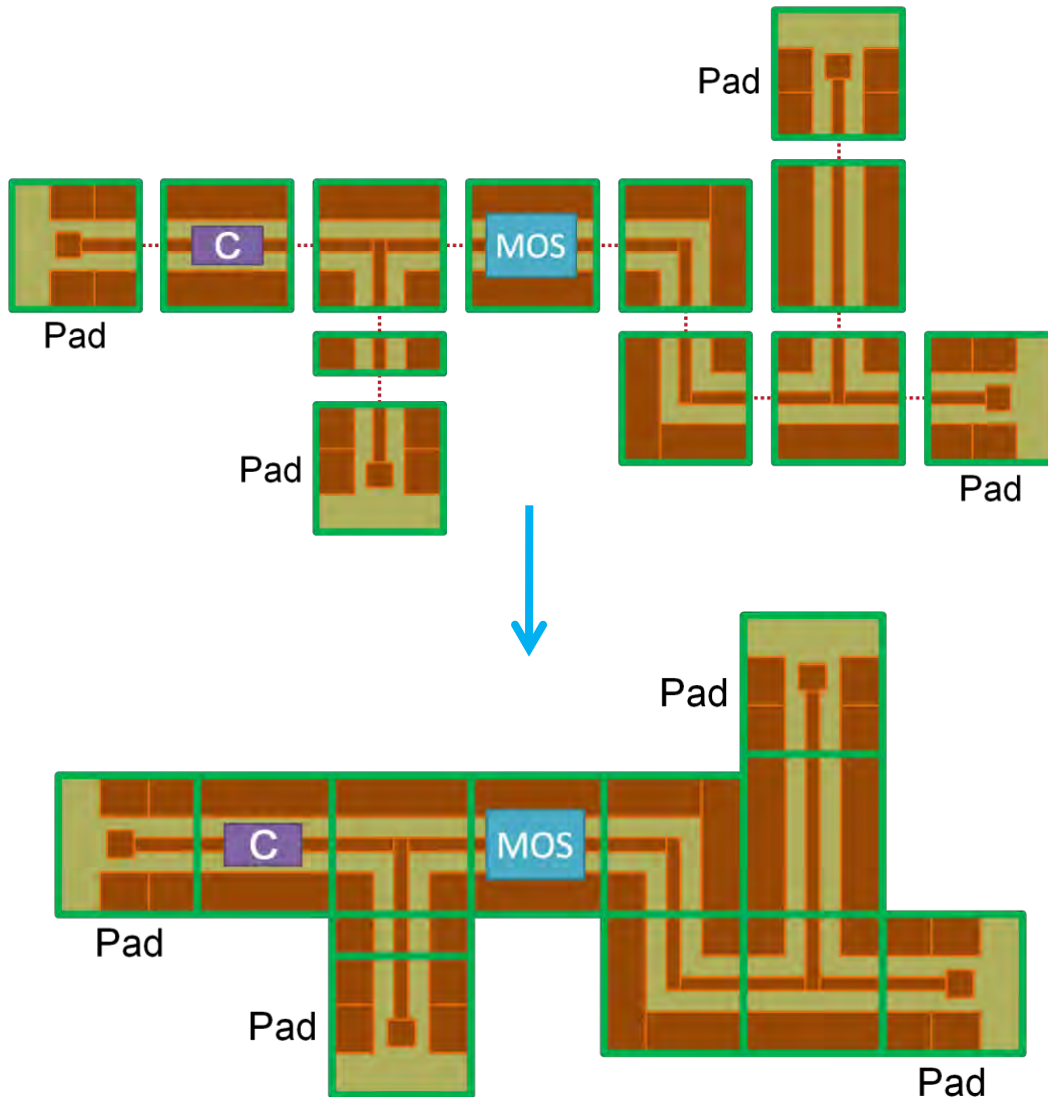


- Use Device Tiles
 - ◆ MOSFET
 - ◆ Transmission Line
 - ◆ Pad
 - ◆ etc.

- Interface for tiles
 - ◆ Transmission Line

- No Parasitic Wire Connect
- No LPE is required

Device model including transmission line interface is necessary.


mmW Decoupling Issue

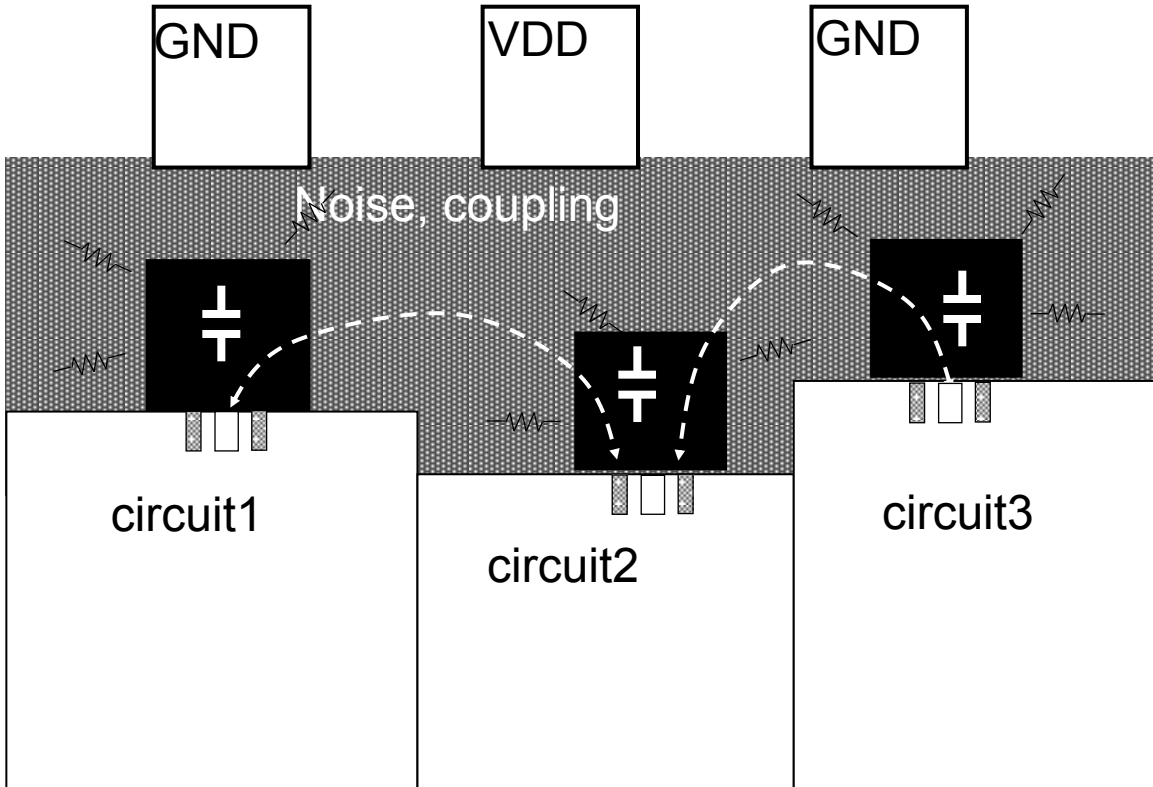

Decoupling capacitors have own parasitic impedance. Large C does not always work as a decoupling in millimeter wave.

Dedicated decoupling device for millimeter wave is required.

Millimeter-Wave Decoupling

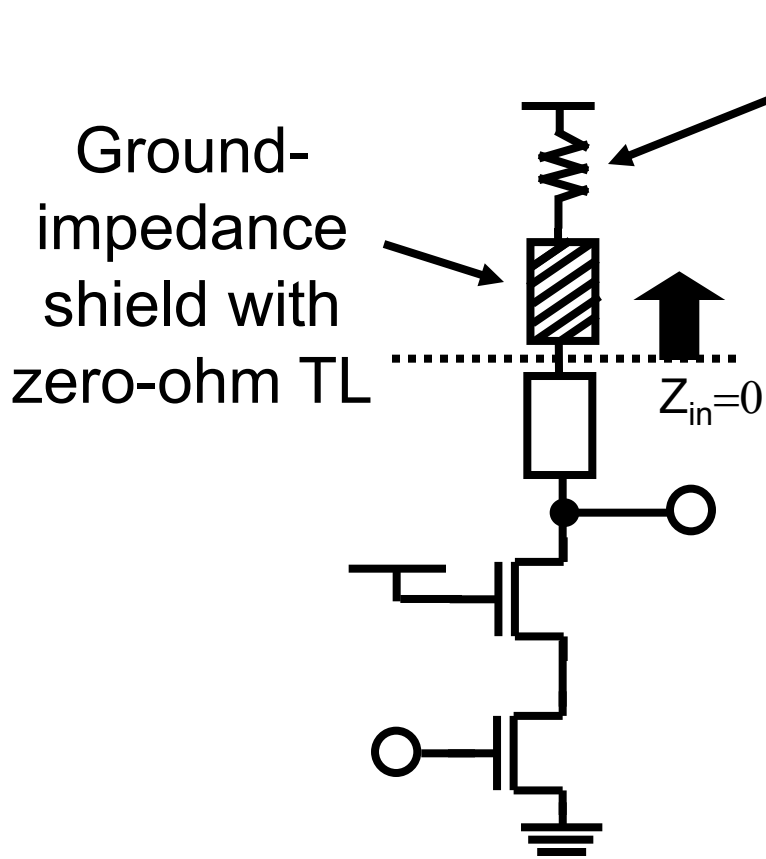


Parasitic
ground
impedance

- A transmission line with ultralow characteristic impedance (0Ω TL) shields the ground impedance.

Single-ended amplifier
with zero-ohm TL


Impedance of Short Stub

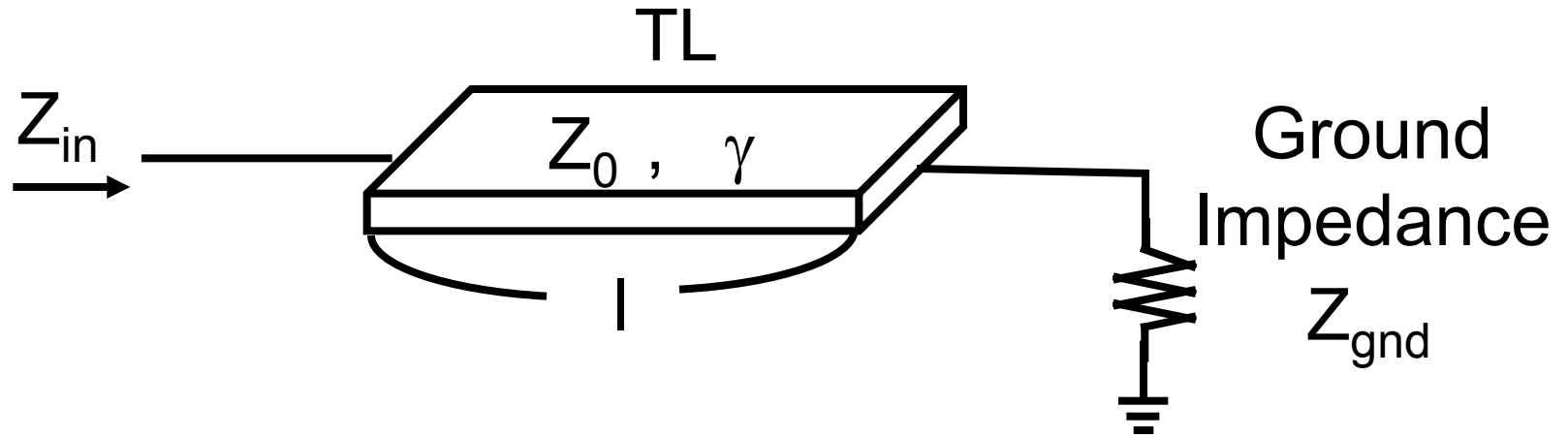


$$Z_{in} = Z_0 \frac{(Z_{gnd} + Z_0) + (Z_{gnd} - Z_0)e^{-2\gamma l}}{(Z_{gnd} + Z_0) - (Z_{gnd} - Z_0)e^{-2\gamma l}}$$

$$\rightarrow 0 \quad \text{if } Z_0 \rightarrow 0 \quad (0\Omega \text{ TL})$$


Characteristic Impedance of 0Ω TL

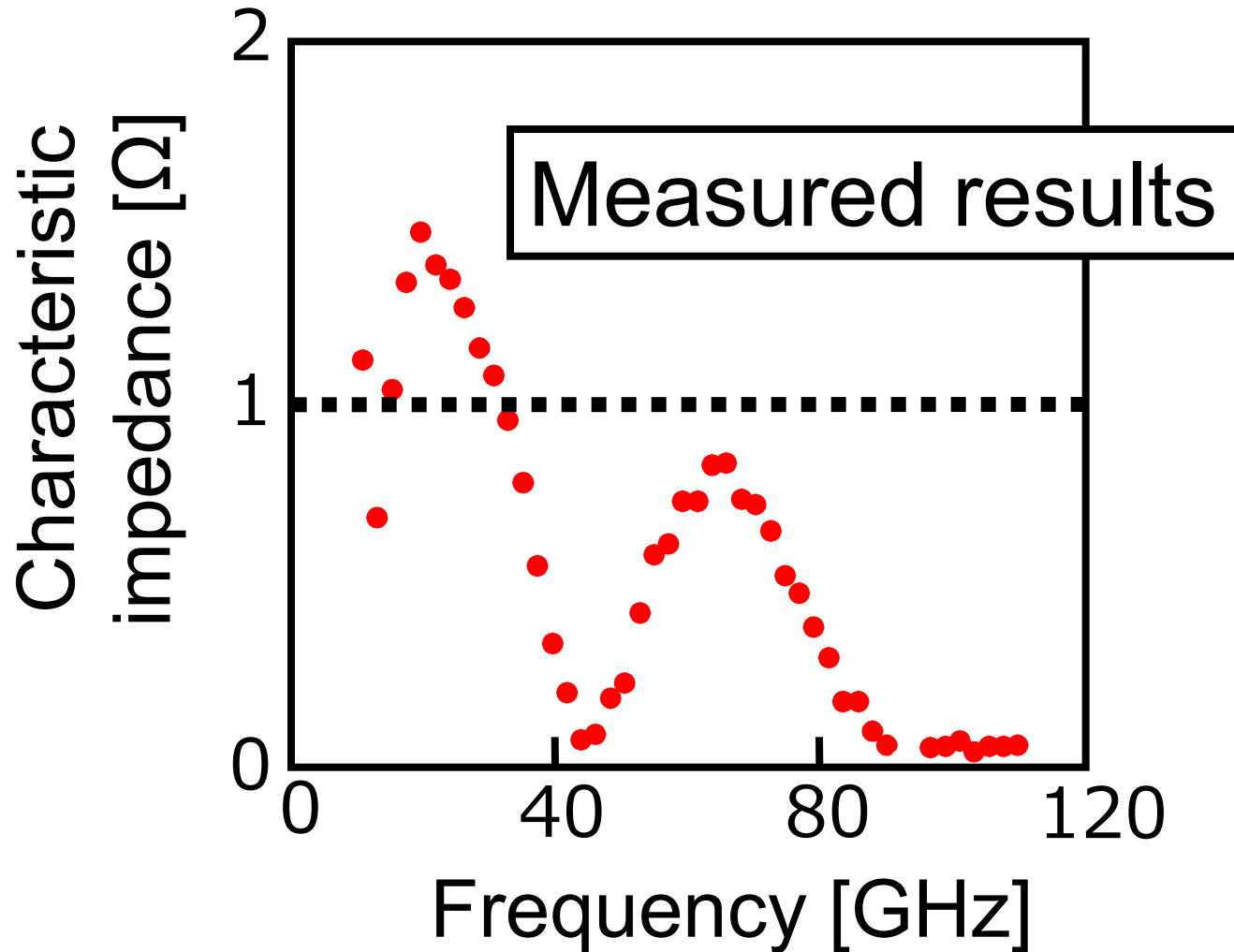


Millimeter-Wave Design

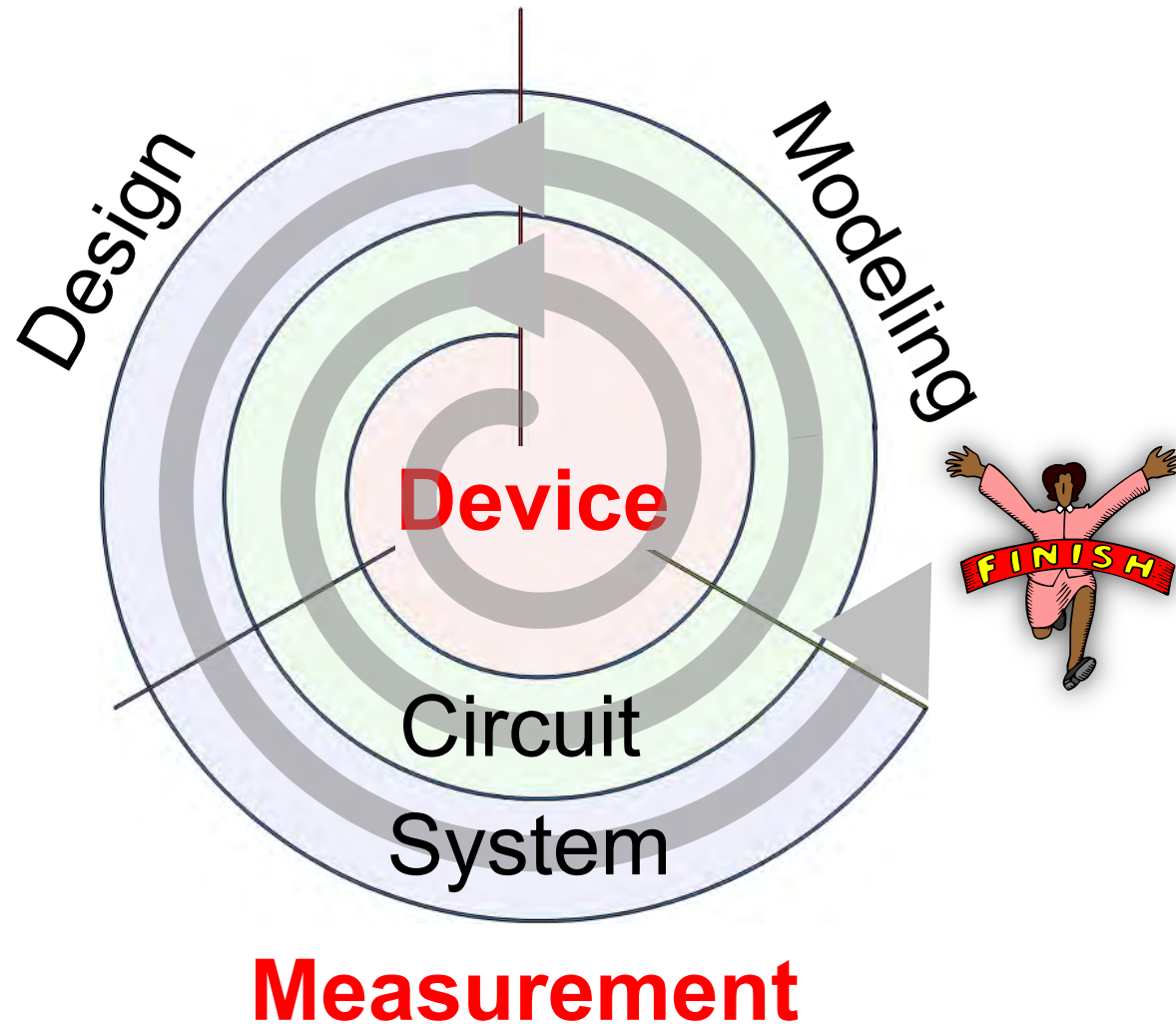


Transmission Line Evaluation

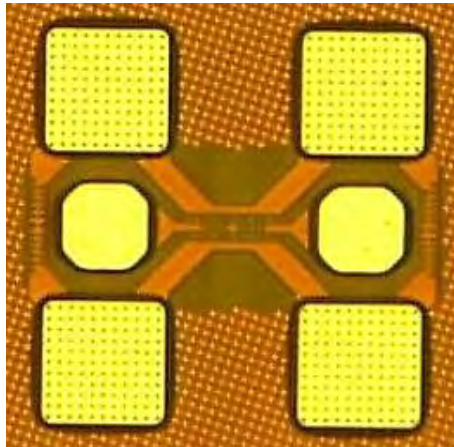


THRU
(0 μ m)

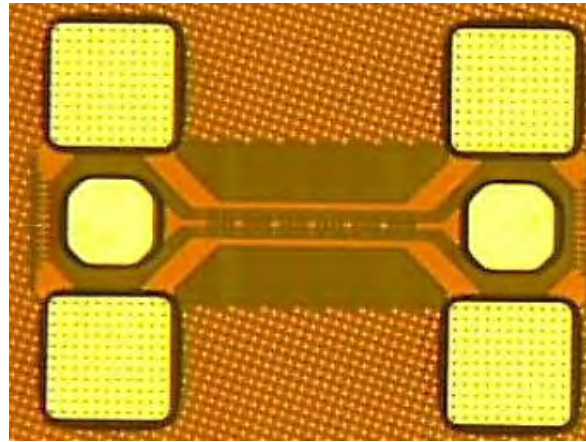


TL4
(80 μ m)

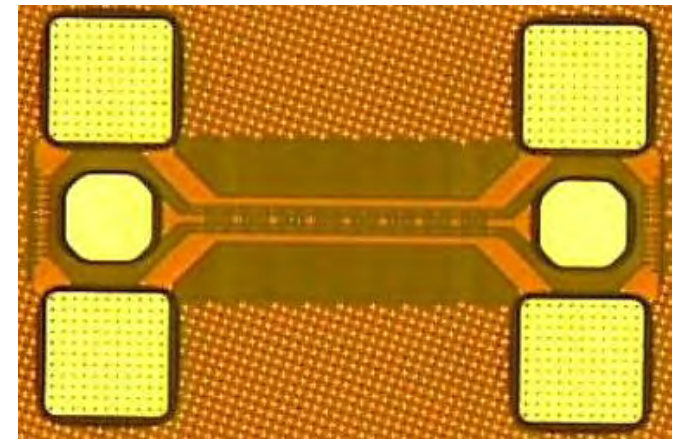

TL6
(120 μ m)

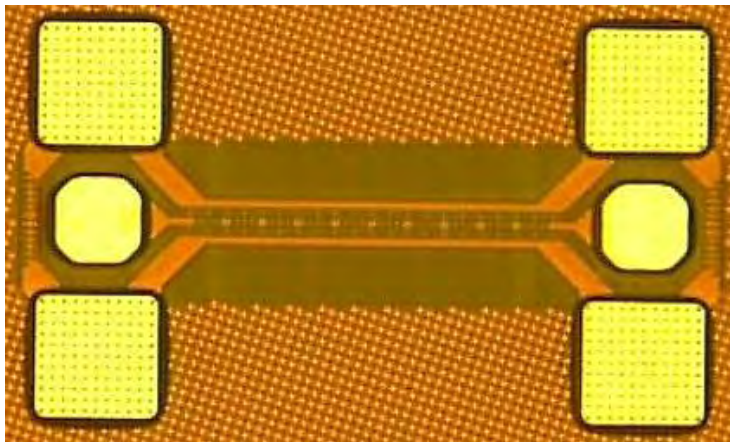


TL8
(160 μ m)

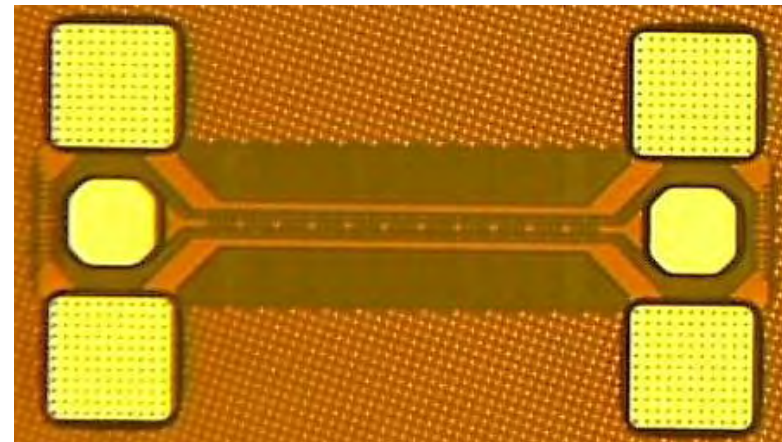

TL9
(180 μ m)


Measurement Issues

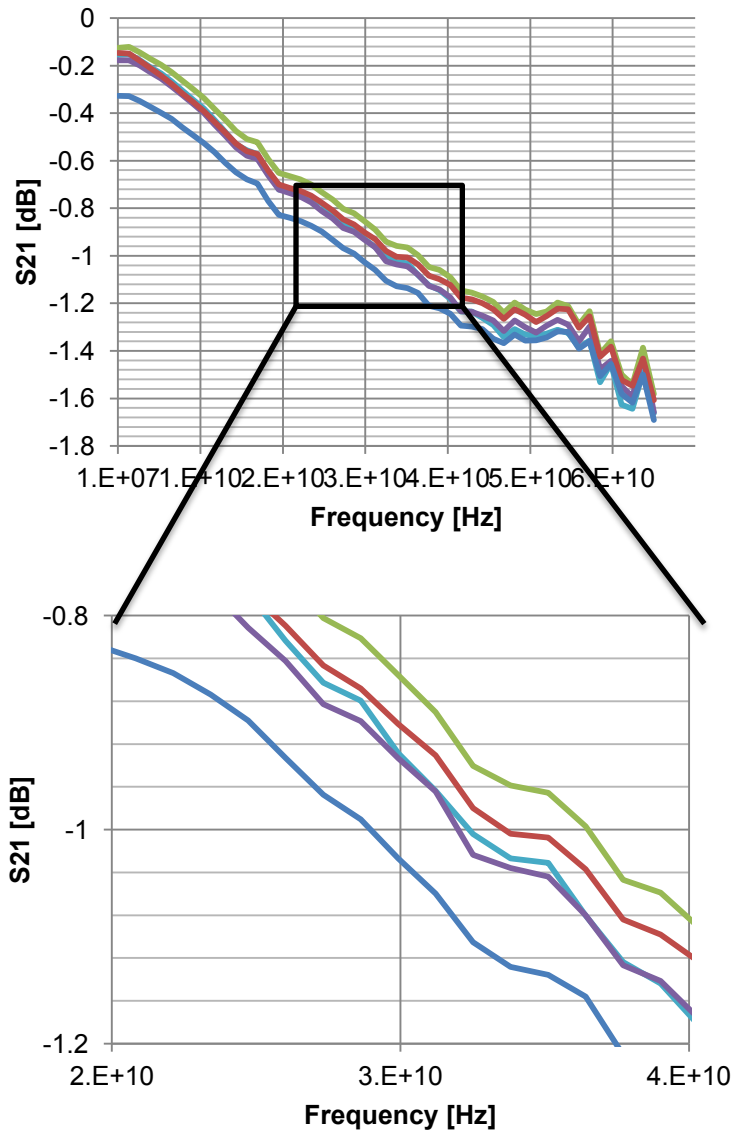

- TL9
- TL8
- TL6
- TL4
- THRU

The S21 should be...
 THRU > TL4 > TL6 > TL8 > TL9
 However, in this case...
 TL6 > TL4 > TL9 > TL8 > THRU


After de-embedding...

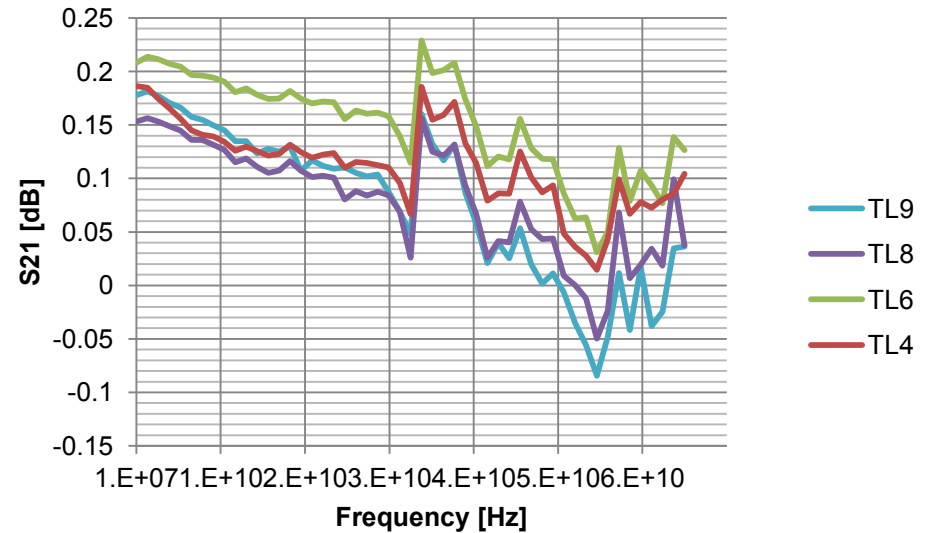


S21 become positive !!

Caused by irreproducible probing!

(a) touch down

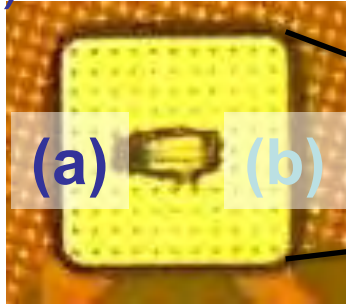


(b) skate

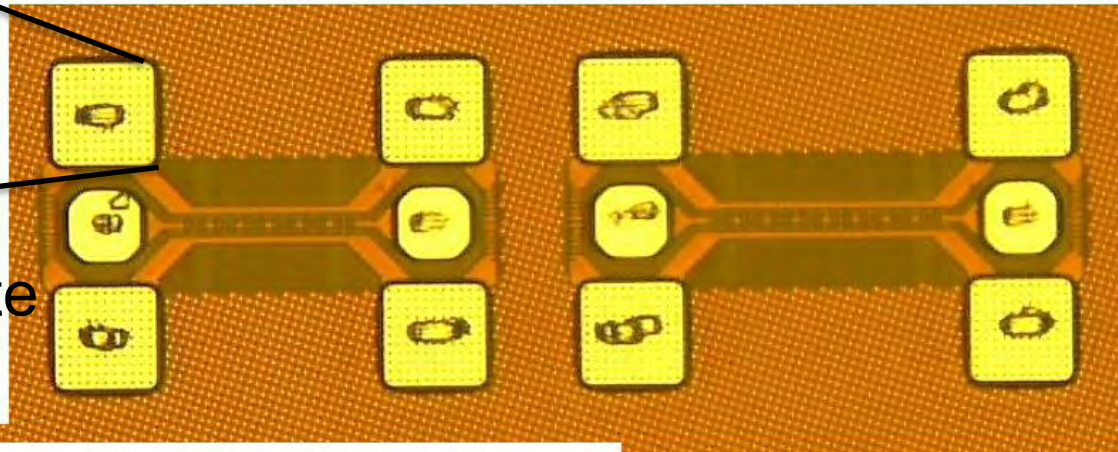

TL4

TL6

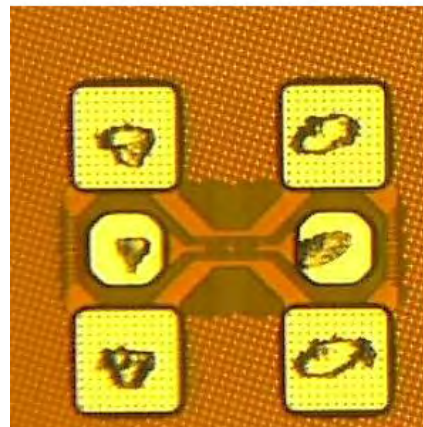

THRU


Probe positions were irreproducible.



Length & contact resistance are fluctuating.


Accurate Probing

By utilizing
scotch tape
marker...

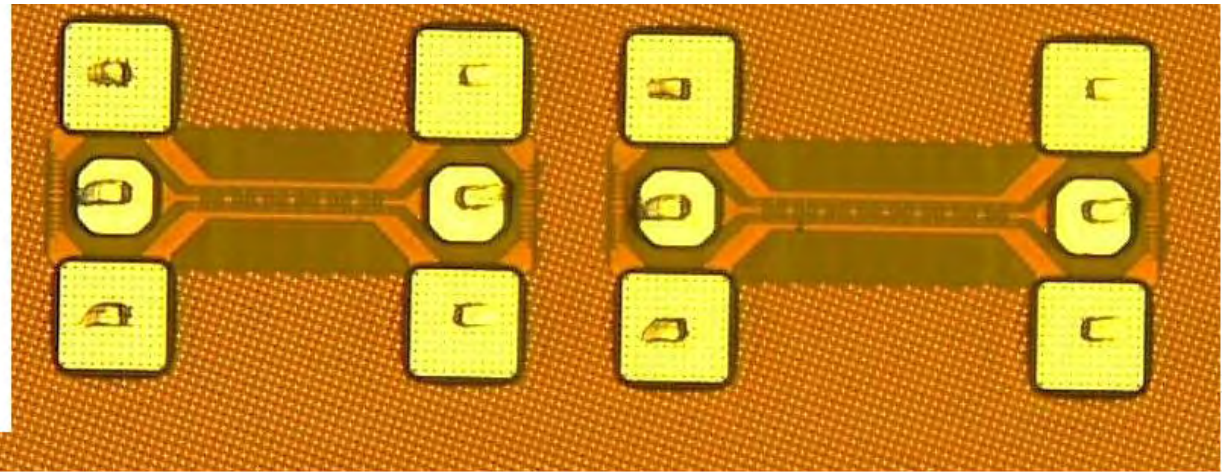


TL4

TL6

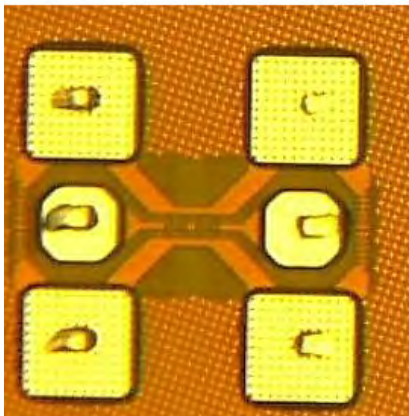

THRU


Measured Results

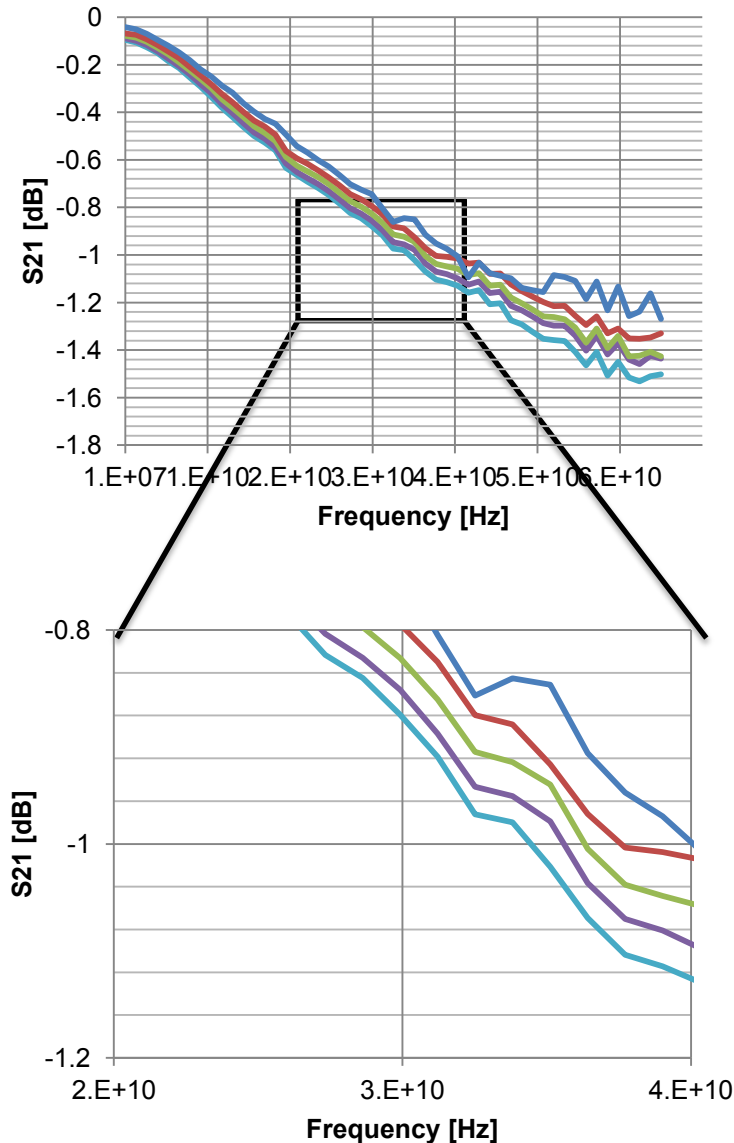

- TL9
- TL8
- TL6
- TL4
- THRU


The S21 is expected order
 THRU > TL4 > TL6 > TL8 > TL9

After de-embedding...

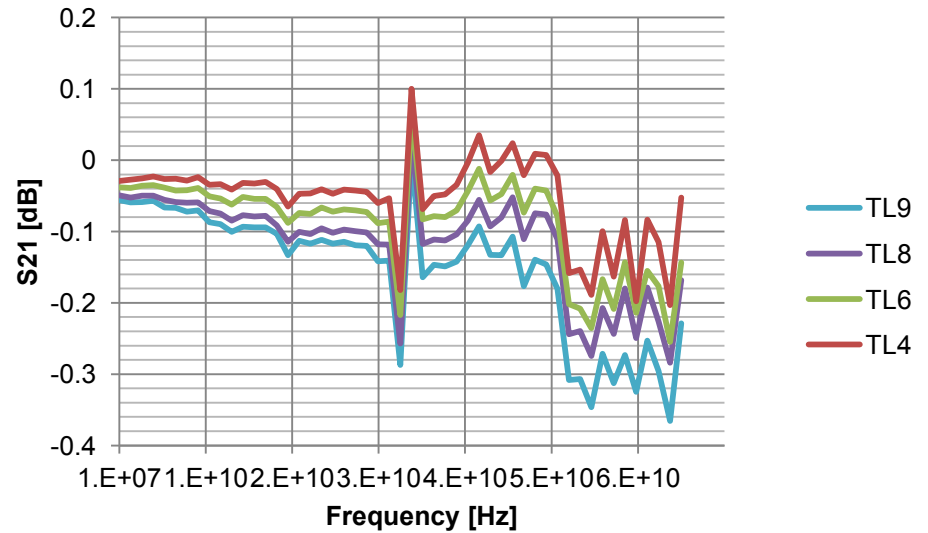


S21 become normal

Millimeter-Wave Design

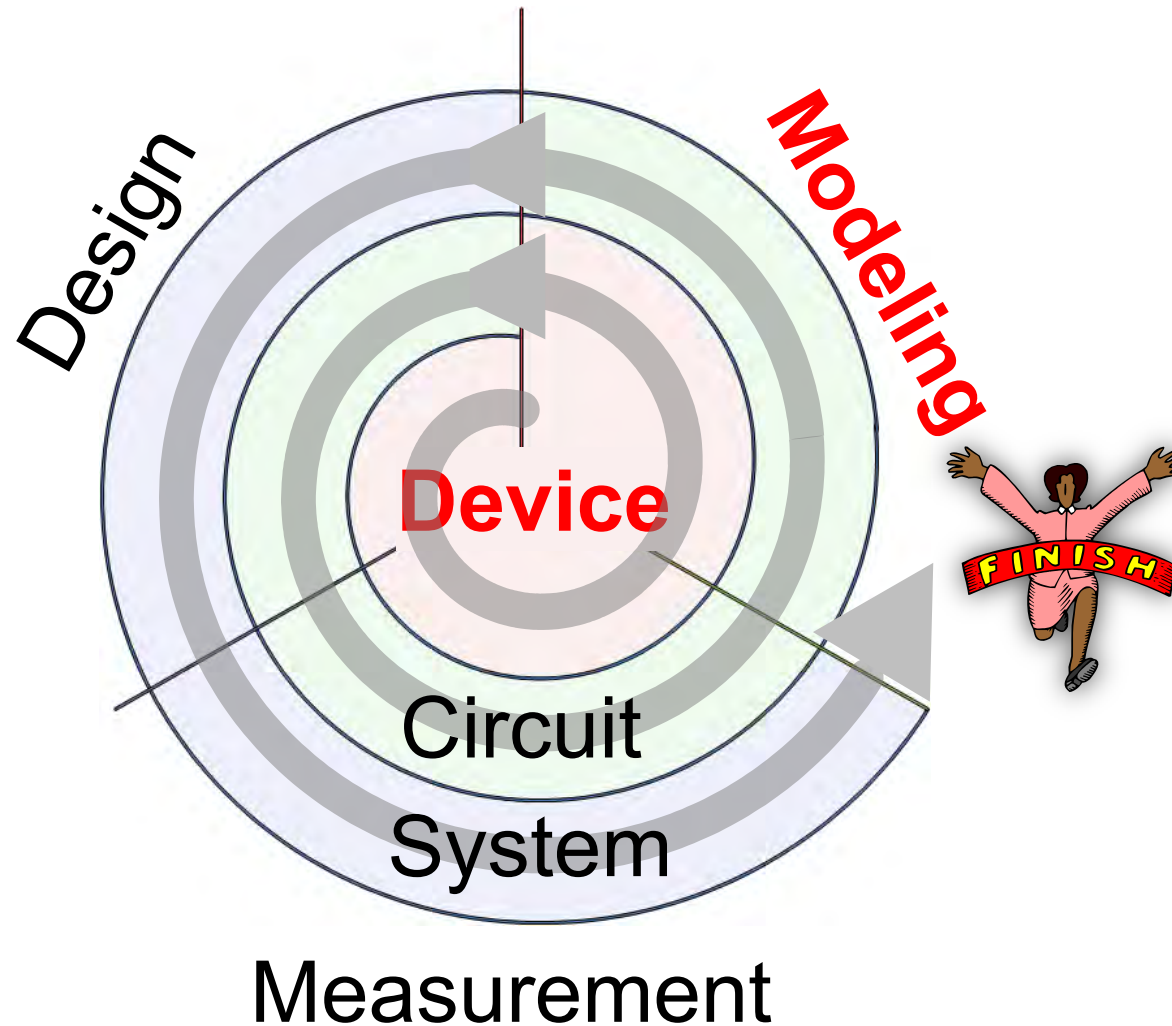

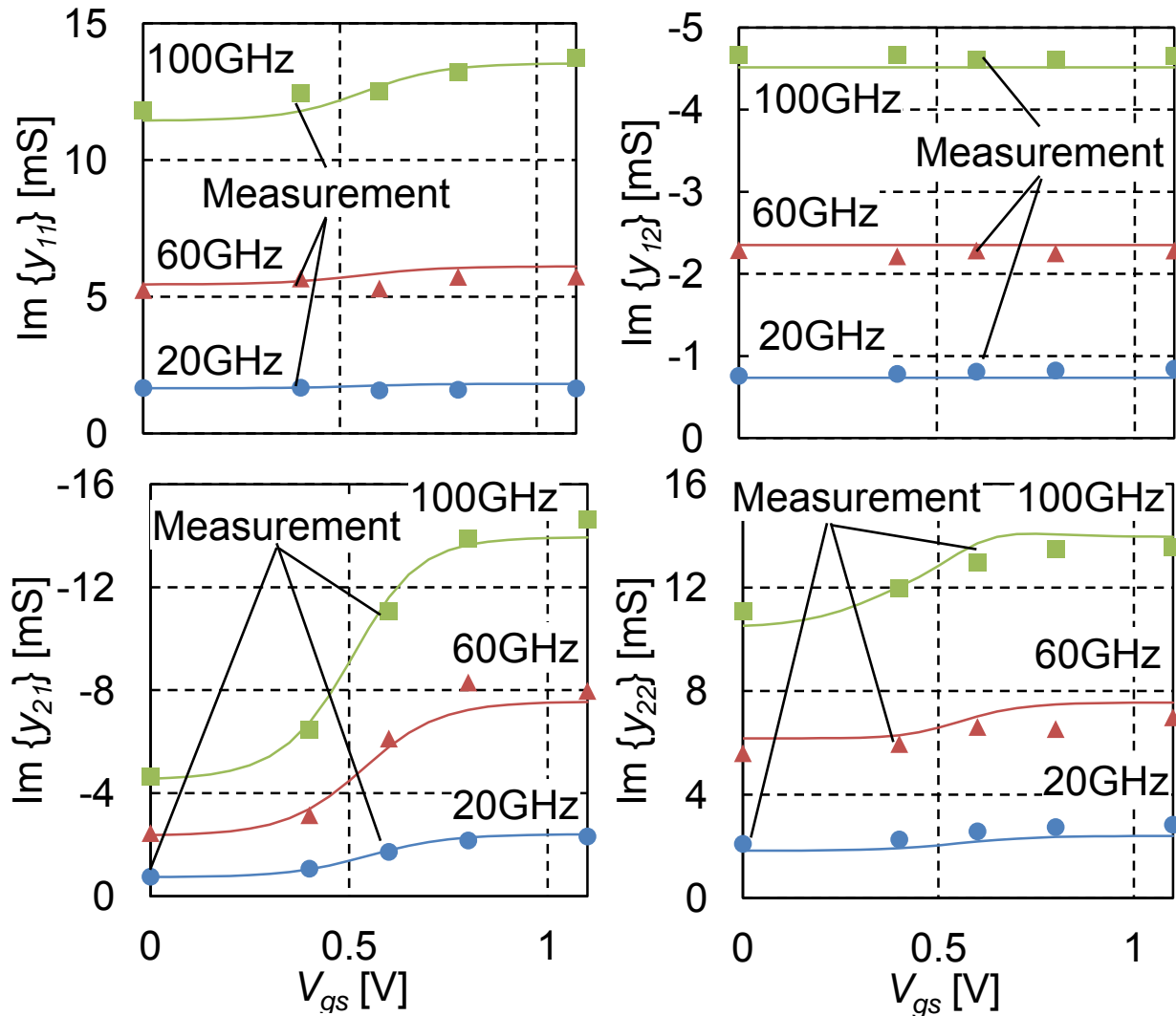
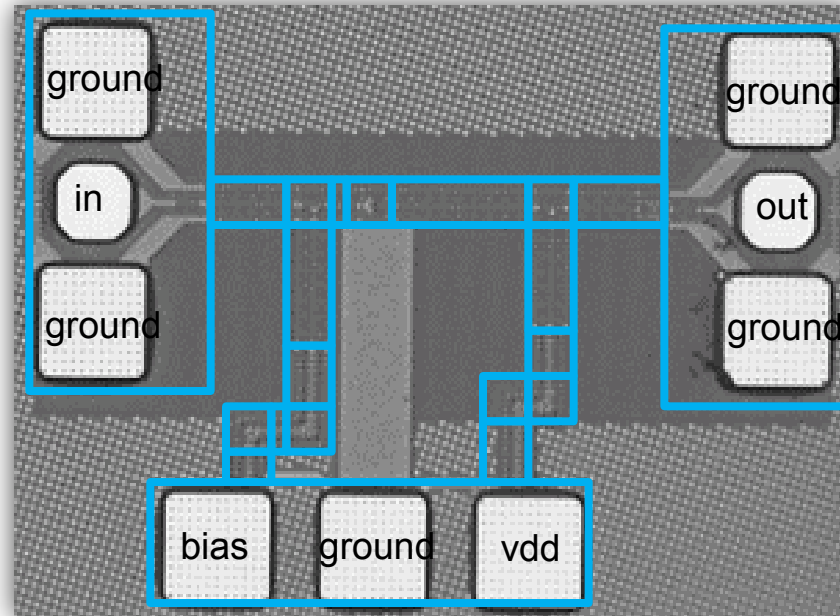
Admittance Comparison




Verification using Amplifier

65nm-CMOS Technology



Tiles




Simplified Circuit Diagram

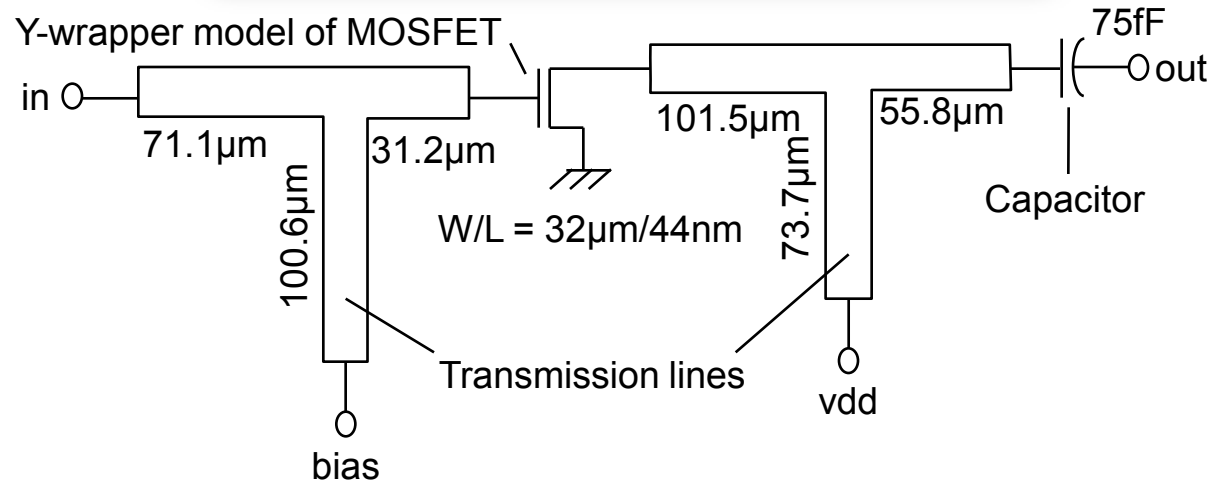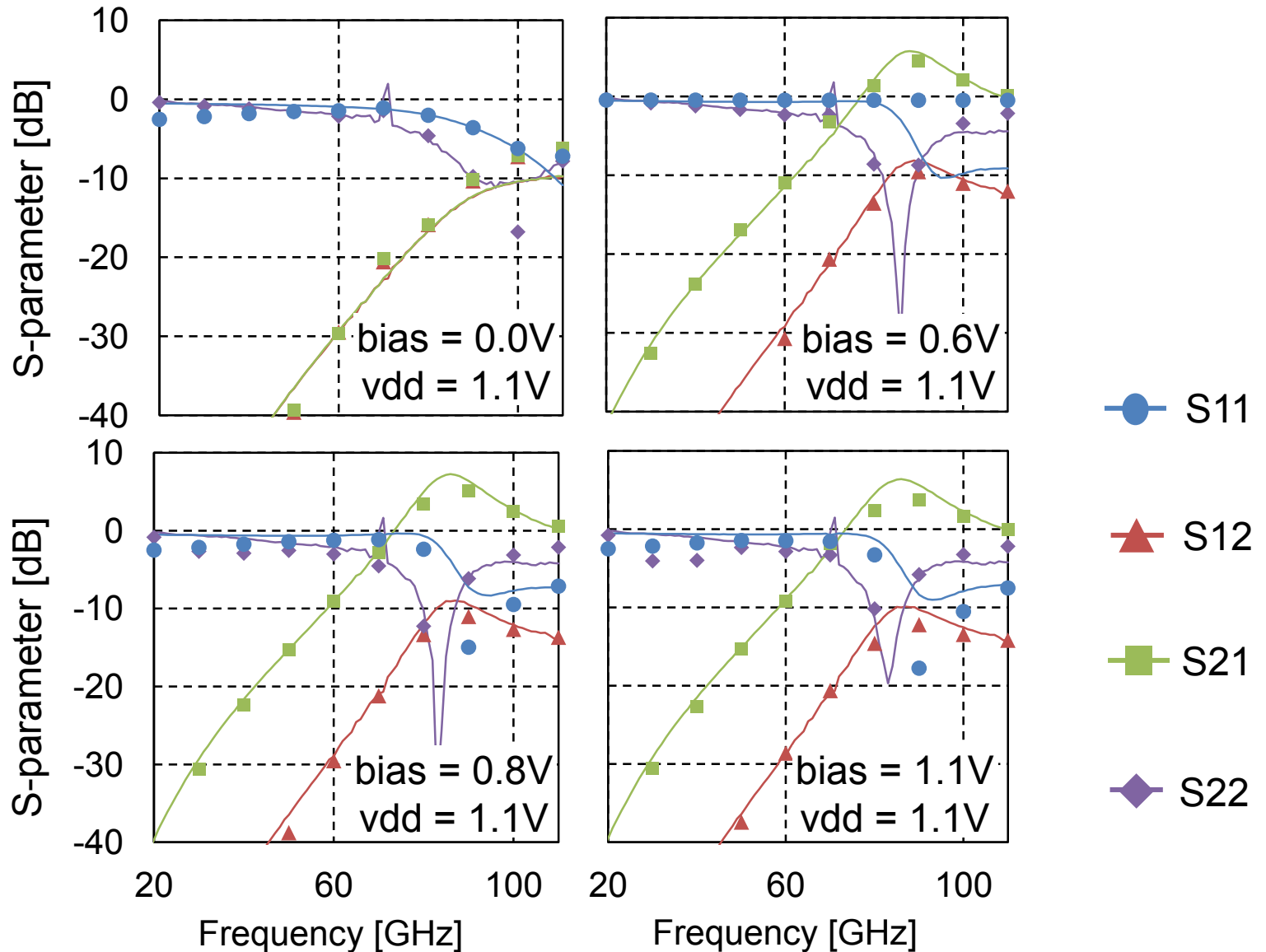


Measured and Simulated Results




Millimeter-Wave Design

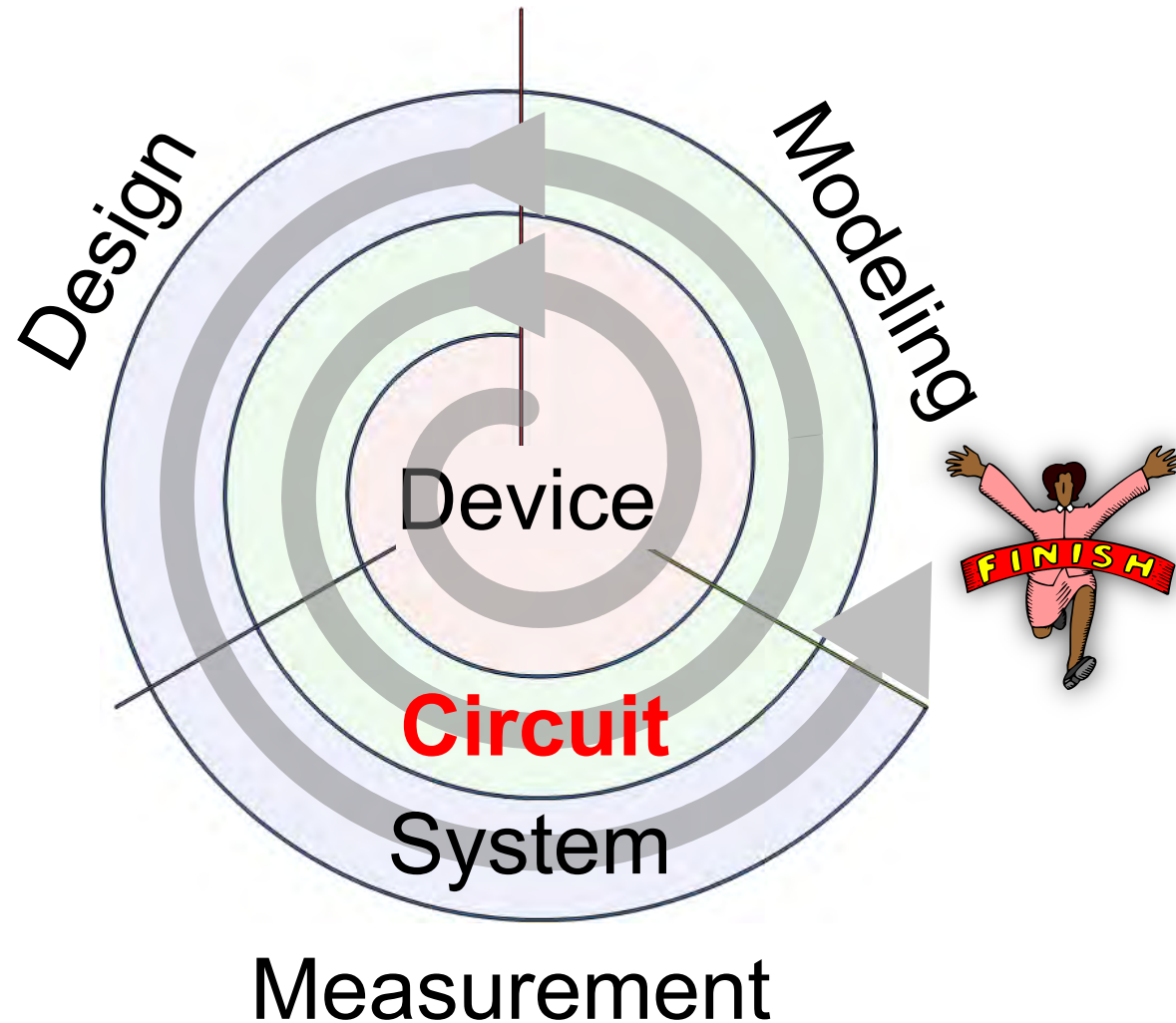

Wideband 140GHz CMOS Amp.


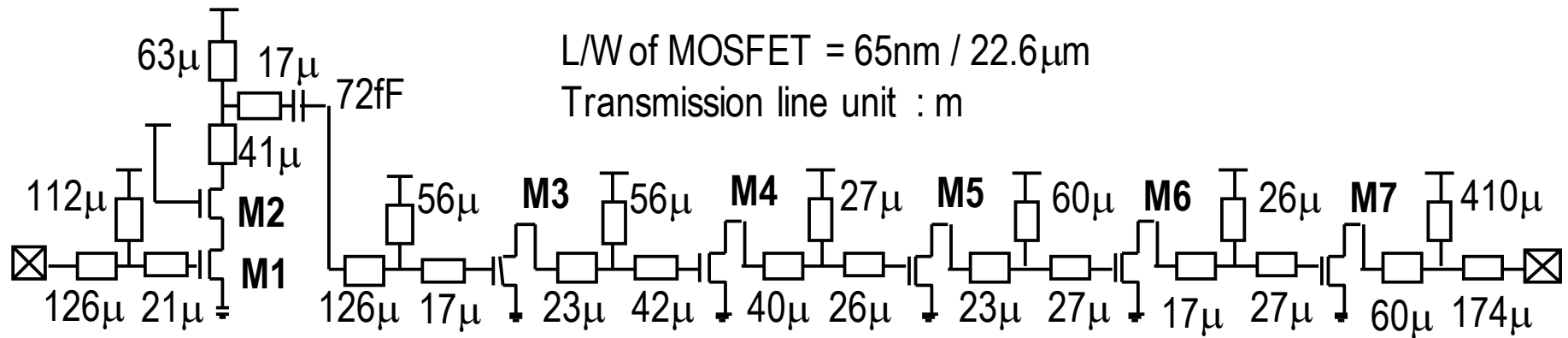


Input

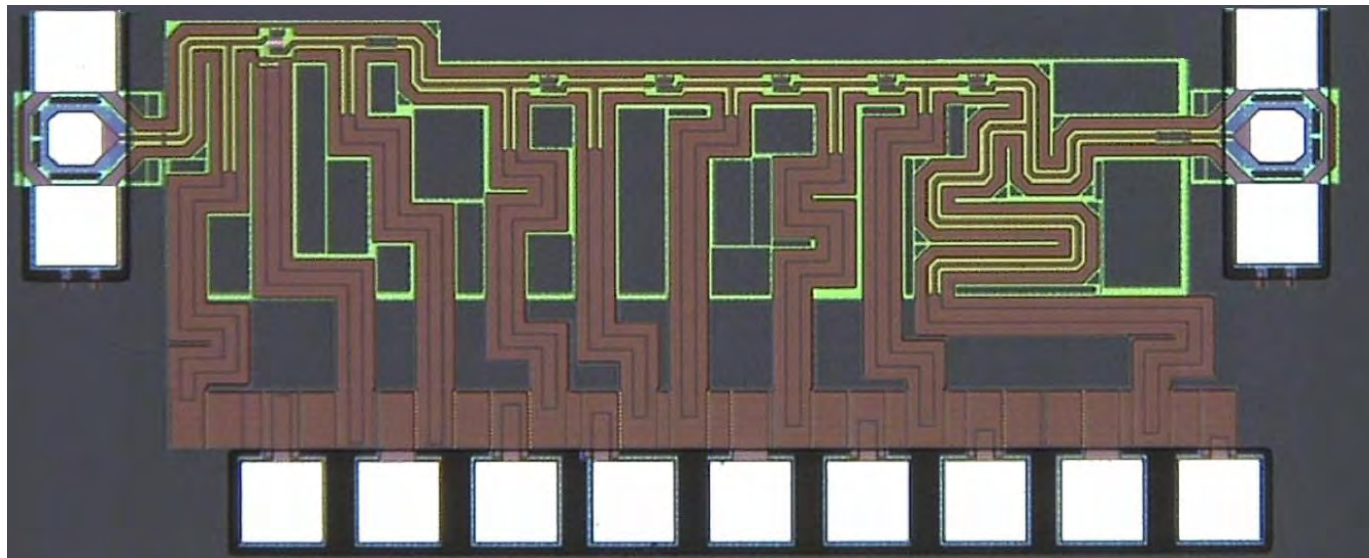

Output

Wideband LNA

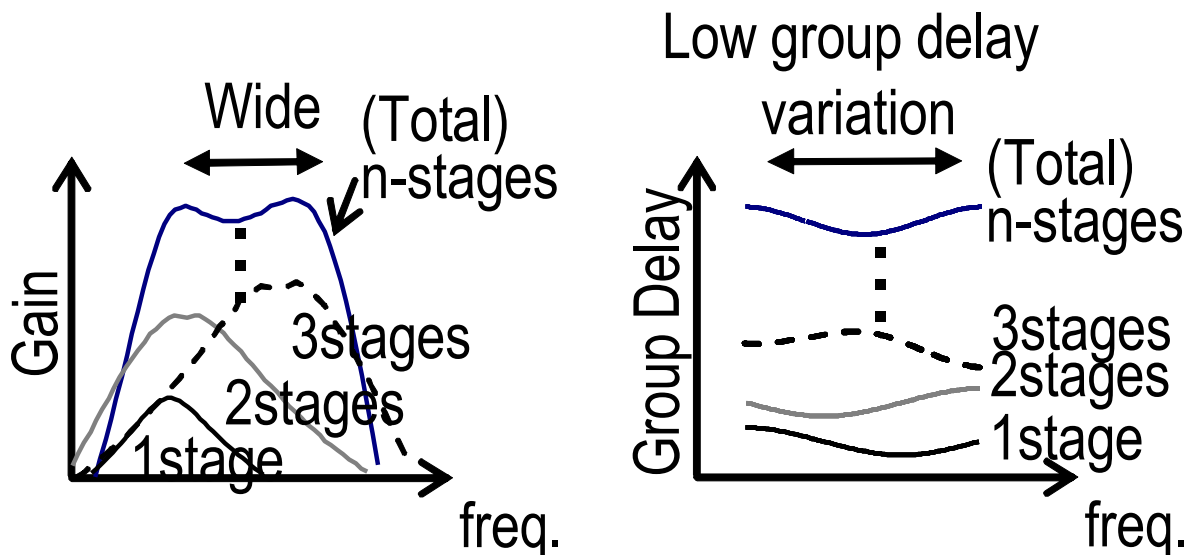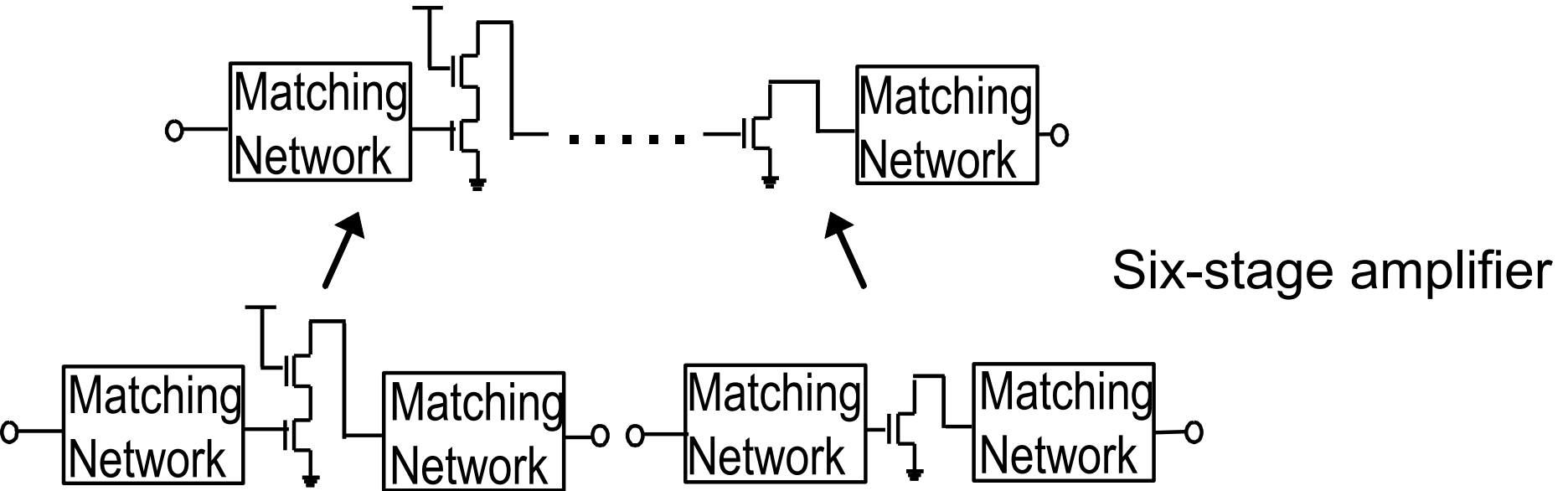


Center frequencies in matching networks are distributed to flatten frequency responses of power gain and group delay.

Measurement Results


Freq. [GHz]	0.1dB-BW [GHz]	3dB-BW [GHz]	Peak Gain [dB]	GD @3dB-BW [ps]	P _{DC} [mW]	Technology [nm]
136.1	12	27.6	9.9	46.2 ± 13.1	57.1	65

↑
Specification
Summary

→
Frequency
Characteristics

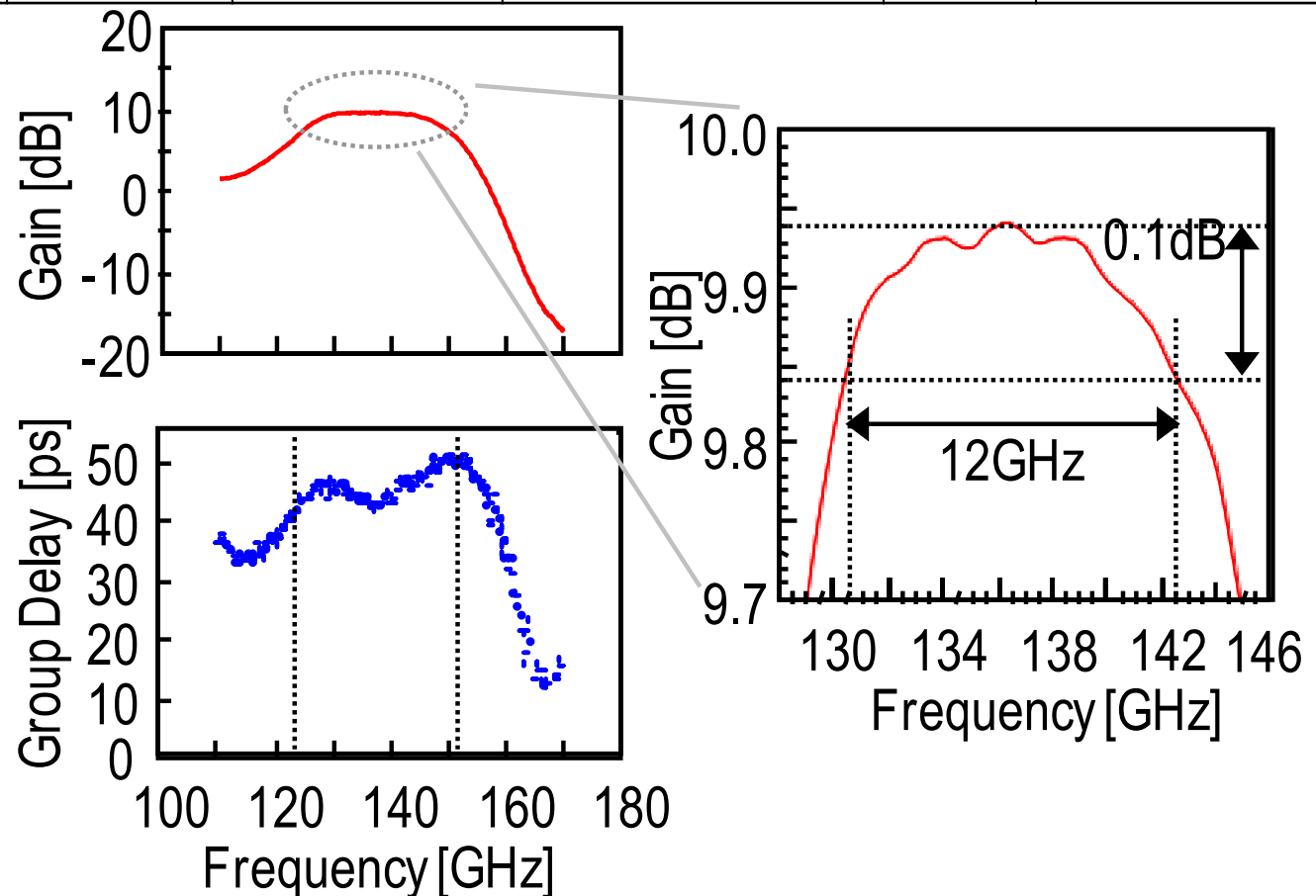

Millimeter-Wave Design

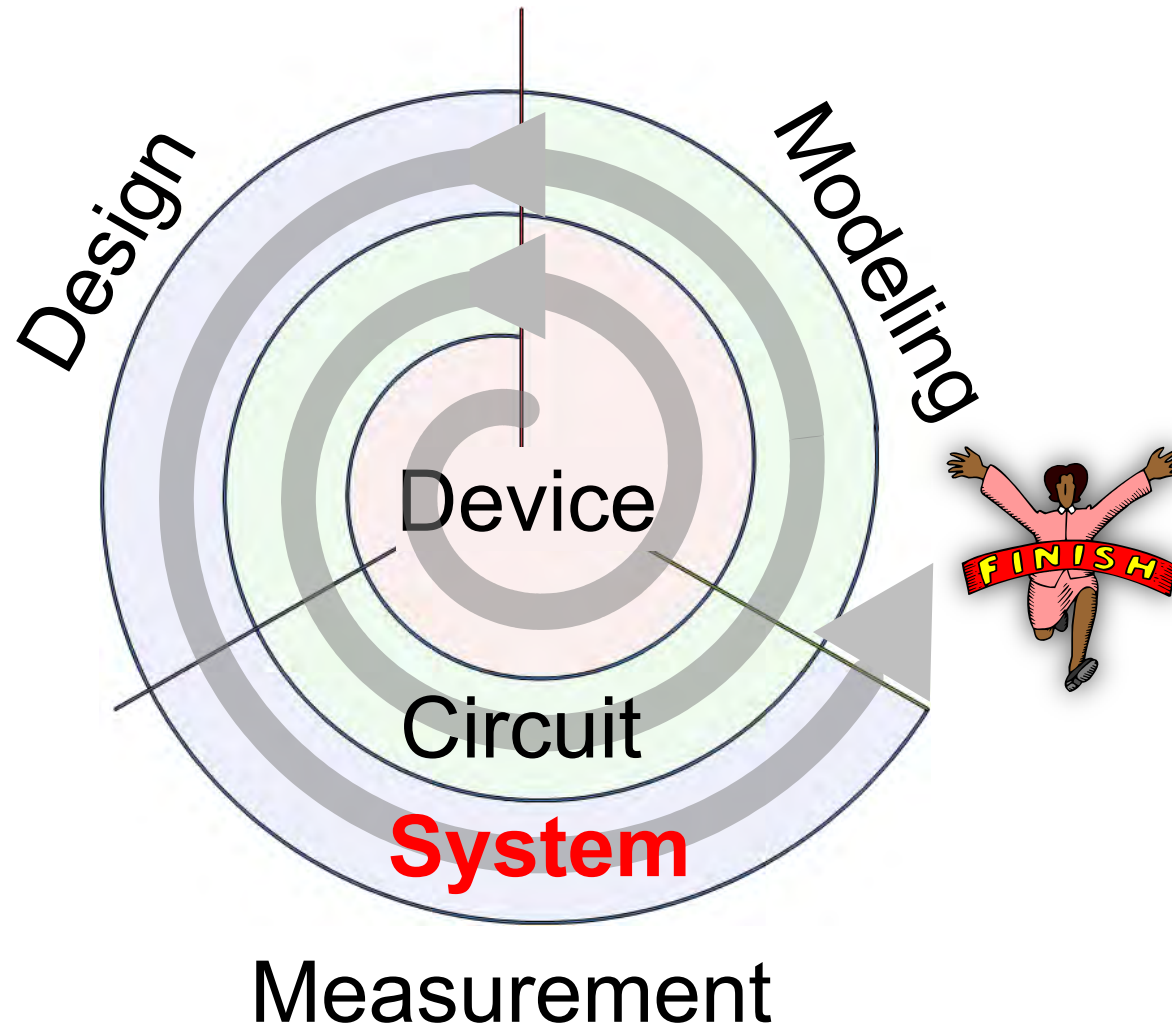


Promising Application: Indoor PAN

THz will be exciting if and when ...

1. Bit rates unmatched by any other wireless technologies are offered.
 - Historically, wireless technology that offers more throughput (even at short ranges) is interested.
2. Costs are comparable to existing technologies
 - The market wants more for the same cost. Going 10x faster captures the market, but charging 10x more is not allowed.
3. Power/bit is less than existing technology
 - Going 10x faster is done with the same battery used by the same technology.

Rick Roberts (Intel), 802.15 THz IG

So what might make a winning solution?

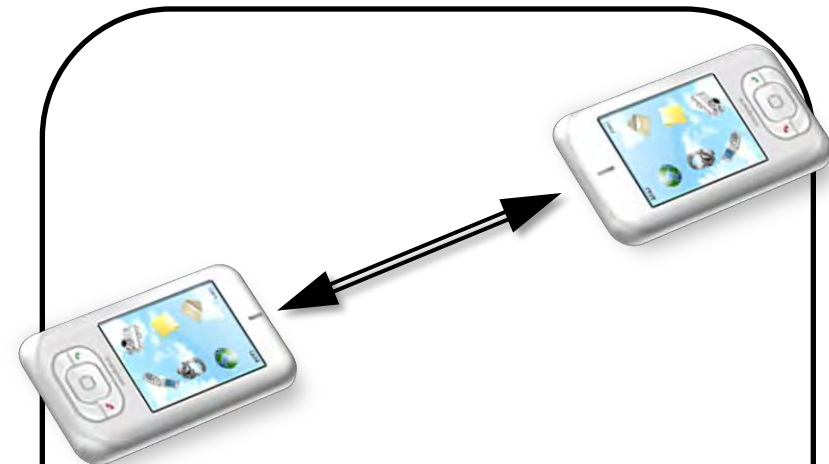


Distance: LOS ~1 meter
 Bit Rates: 20 to 50+ Gbps
 Cost: comparable to Bluetooth
 Power consumption:
 comparable to Bluetooth

Contents


- mmW / THz CMOS Design
- **60GHz HDMI Transceiver**
- 120 / 140GHz Dual Channel Receiver

Wideband 60GHz Regulations

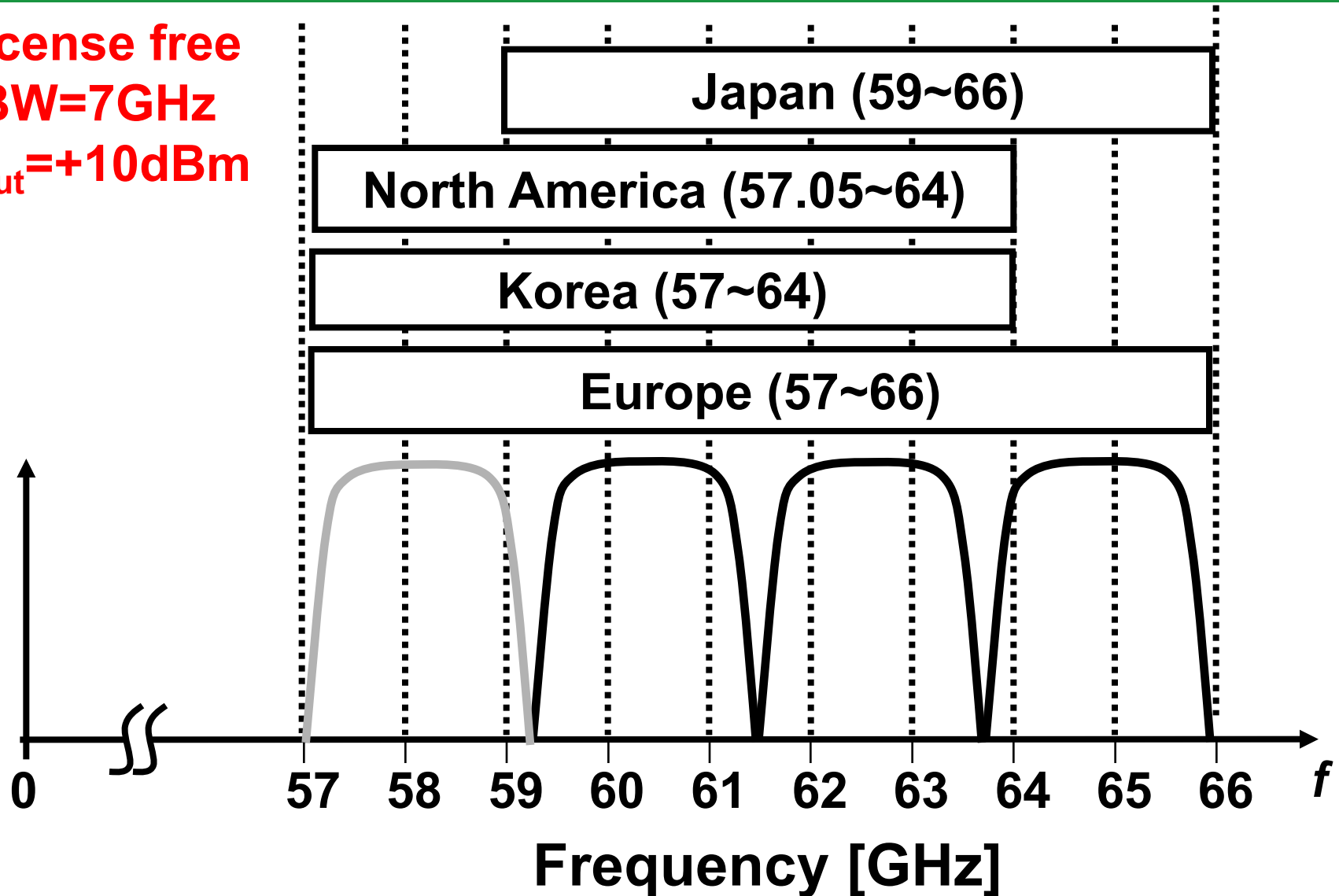License free
BW=7GHz
 $P_{out}=+10\text{dBm}$




Target Application: Mobile Streaming

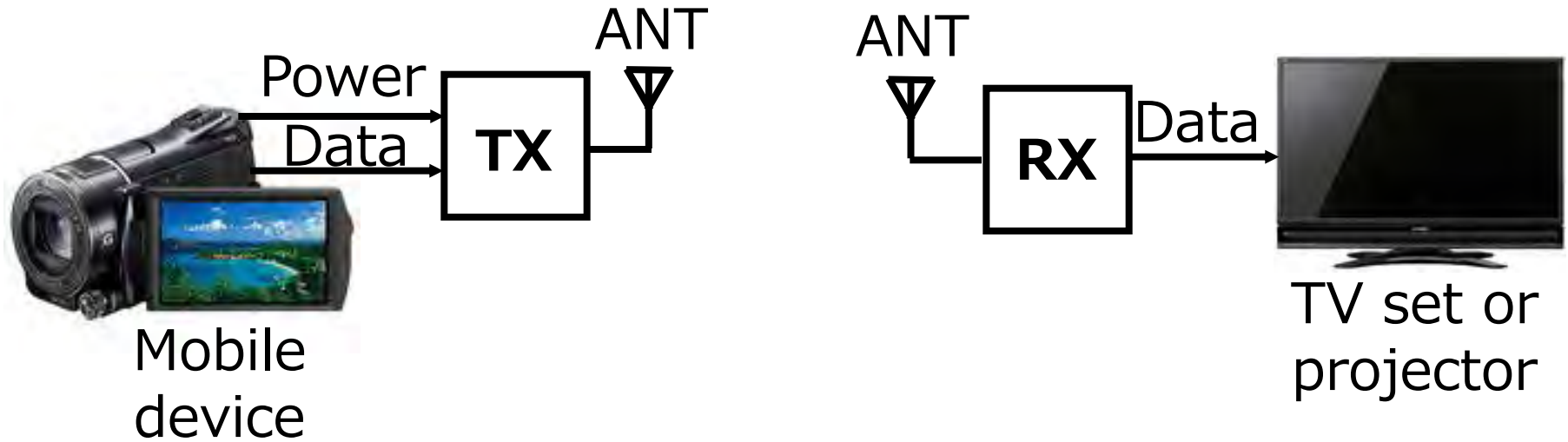

Mobile streaming application for mmw.


TX Power consumption should be reduced for mobile streaming applications.

mmWave Simplex Communication

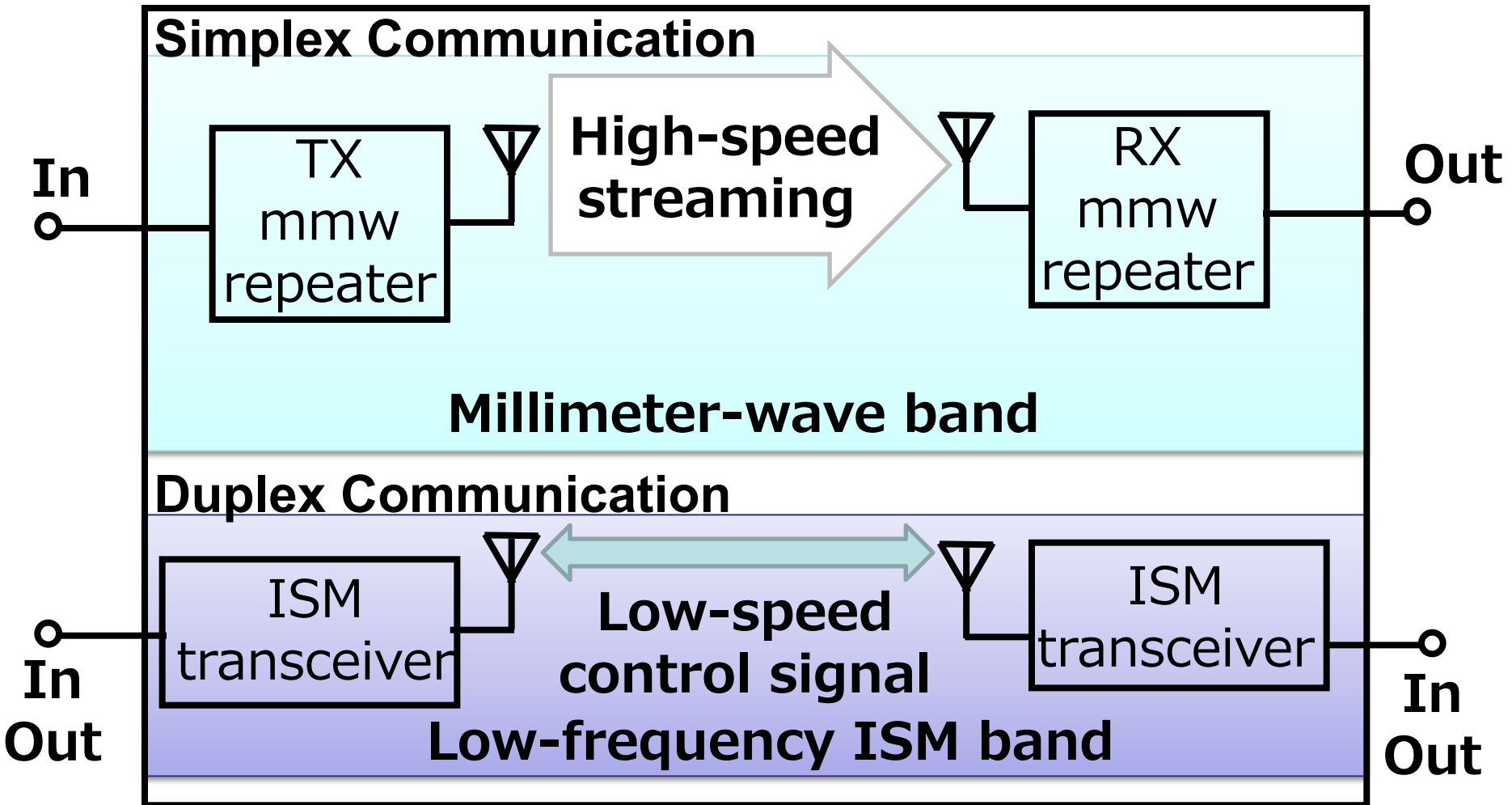


Repeater for Low Power


Tx "Repeater"

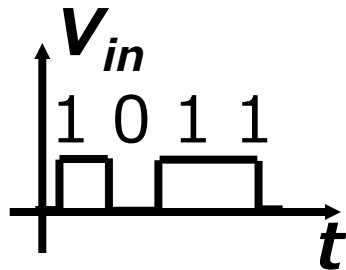

IN

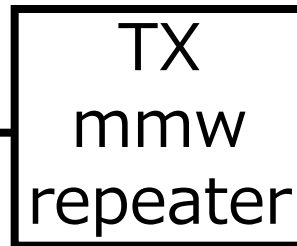

OUT

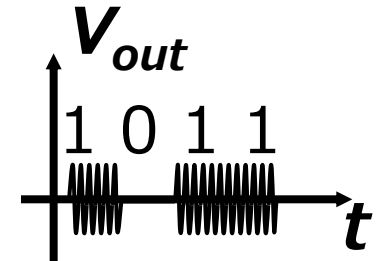


Input waveform


Output waveform

Digital data transferred from baseband to mmWave.


Rx "Repeater"

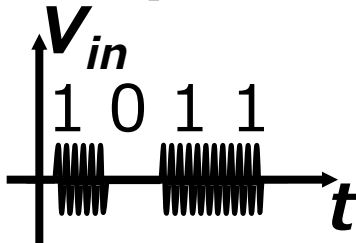

IN

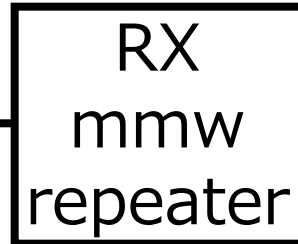

OUT

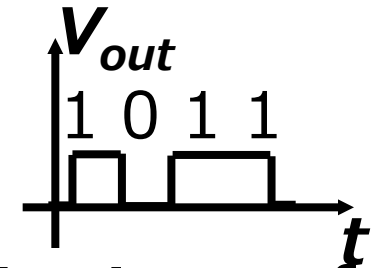


Input waveform

Output waveform



Digital data transferred from mmWave to baseband.

Simple architecture Realizes lower power.

Low-Power 3CH TX and RX Repeaters


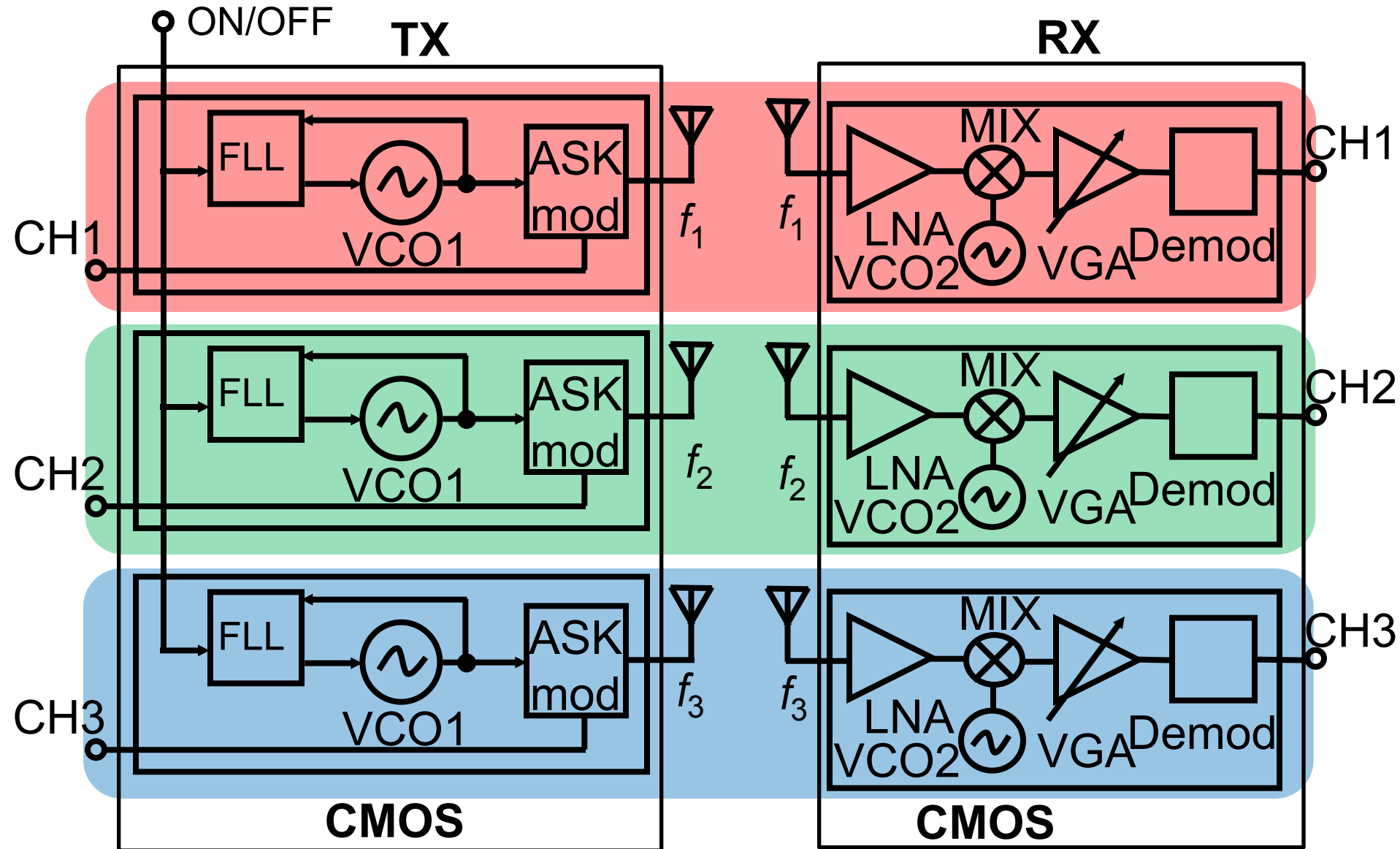


Chip and Module Photographs

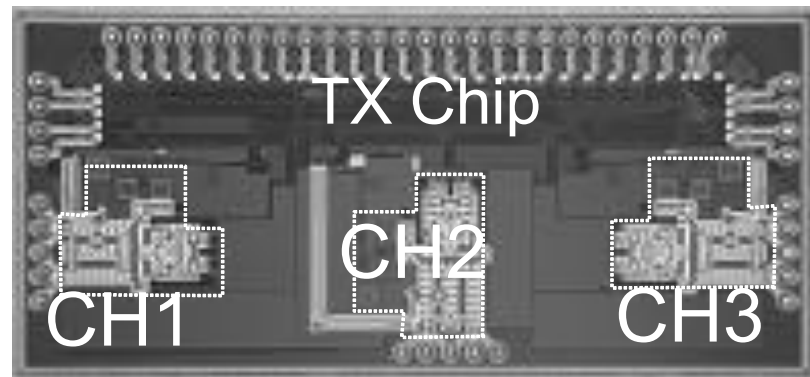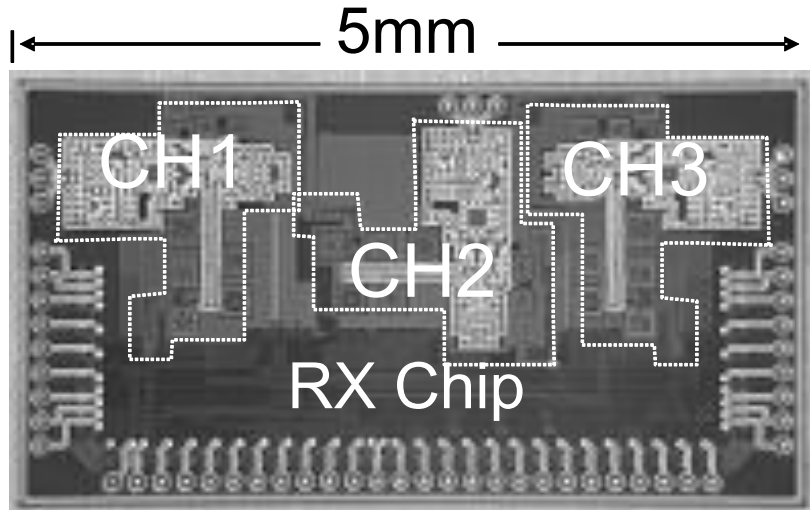

2.7mm

2.3mm

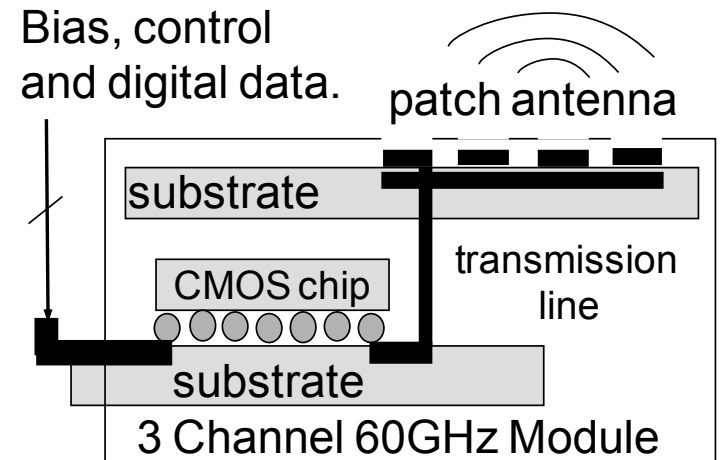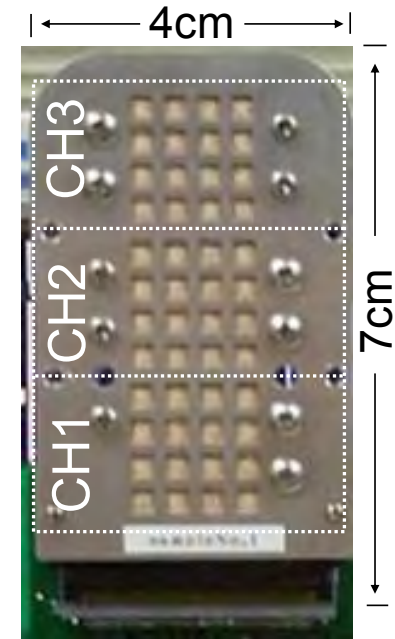

Wireless Communication Measurement




System Spec.	Technology	Data Rate	TX RF Power [dBm]	RX Sensitivity or Noise Figure	Power Consumption (TX / RX) [mW]	Core area TX, RX [mm ²]
This Work	90nm CMOS	1Gbps	5	-52dBm	51 / 116	0.85, 1.92
[5]	90nm CMOS	1Gbps	5	-52dBm	51 / 116	0.85, 1.92


Contents

- mmW / THz CMOS Design
- 60GHz HDMI Transceiver
- 120 / 140GHz Dual Channel Receiver

Worldwide Radio Wave Allocation

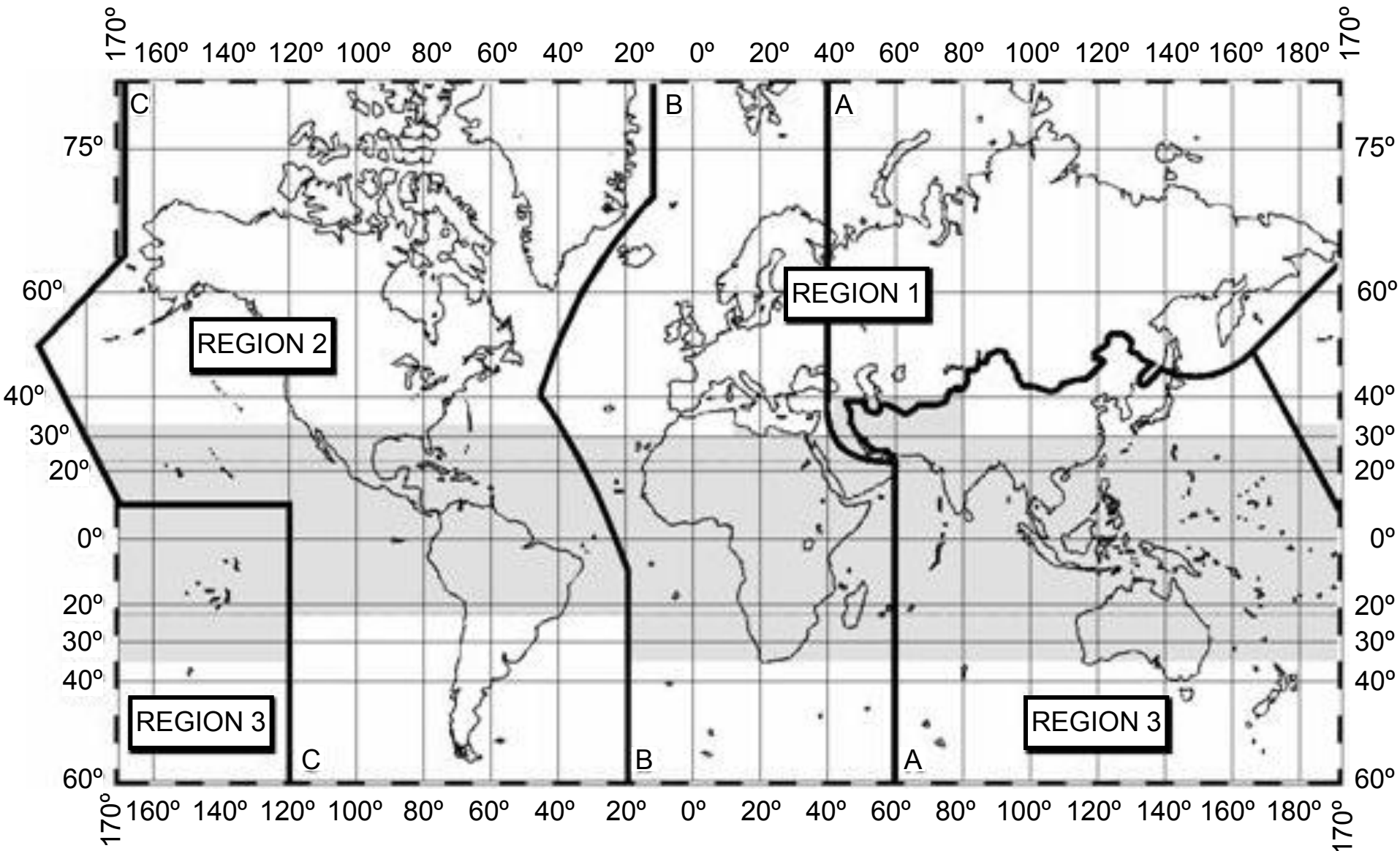

Frequency Allocation in Japan (region 3)

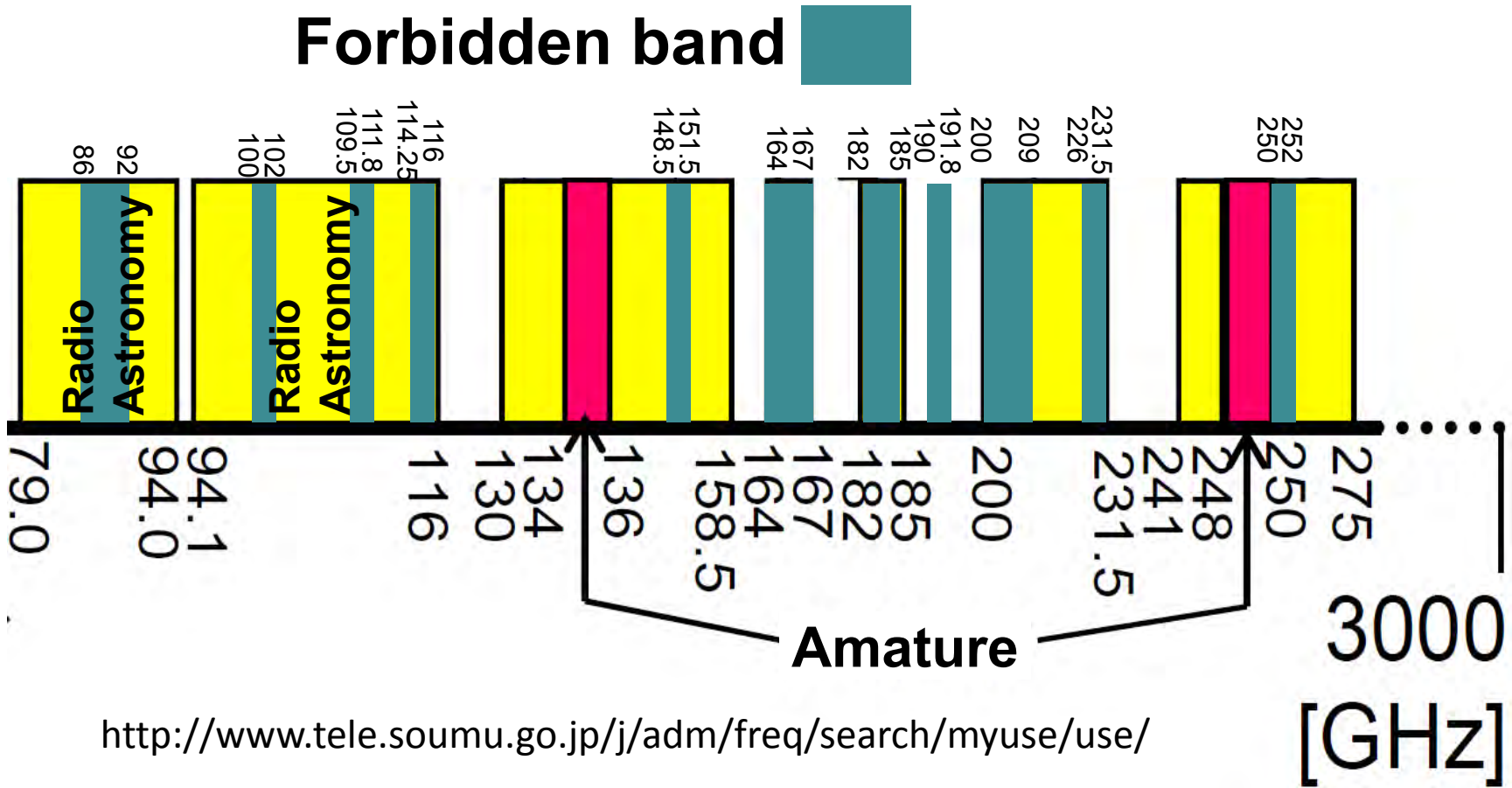


Wireless communication may be available when the forbidden bands are avoided.

Frequency Allocation in Region 1 & 2


Frequency allocation in UK (region 1)

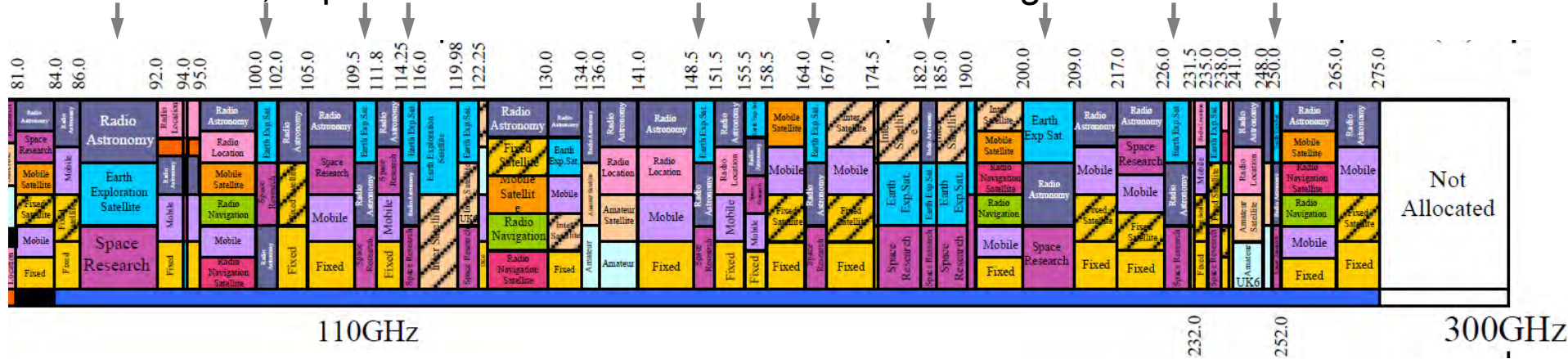Forbidden bands exclusively used by "Radio Astronomy", "Earth Exploration Satellite", "Space Research" are same as those in region 1.




Frequency allocation in USA (region 2)

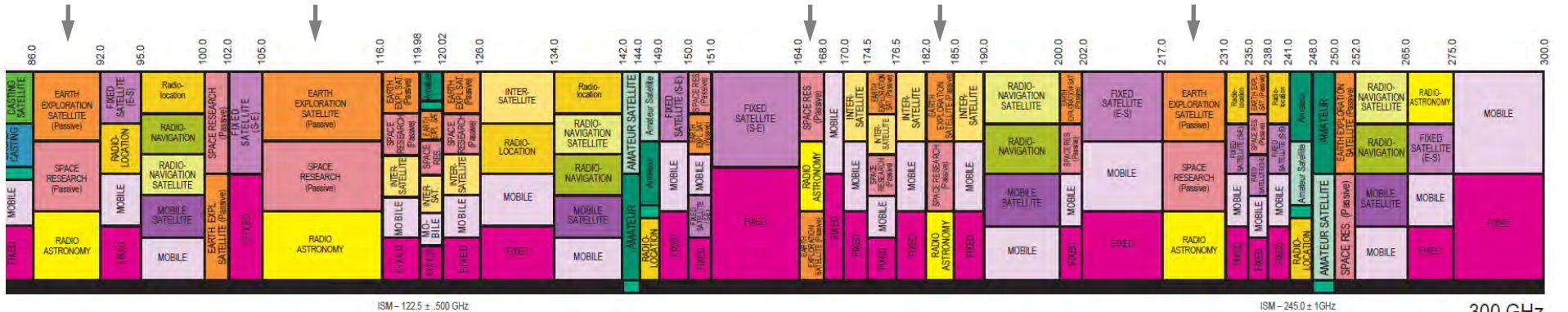Forbidden bands exclusively used by "Radio Astronomy", "Earth Exploration Satellite", "Space Research" are different from those in region 1.



Channelization Plan for THz


Channel Number	Low Freq. (GHz)	Center Freq. (GHz)	High Freq. (GHz)	3dB BW (GHz)	Roll-Off Factor
1	116.589	124.089	131.589	12	0.25
2	132.100	139.600	147.100	12	0.25
3	147.611	155.111	162.611	12	0.25
4	167.000	174.500	182.000	12	0.25

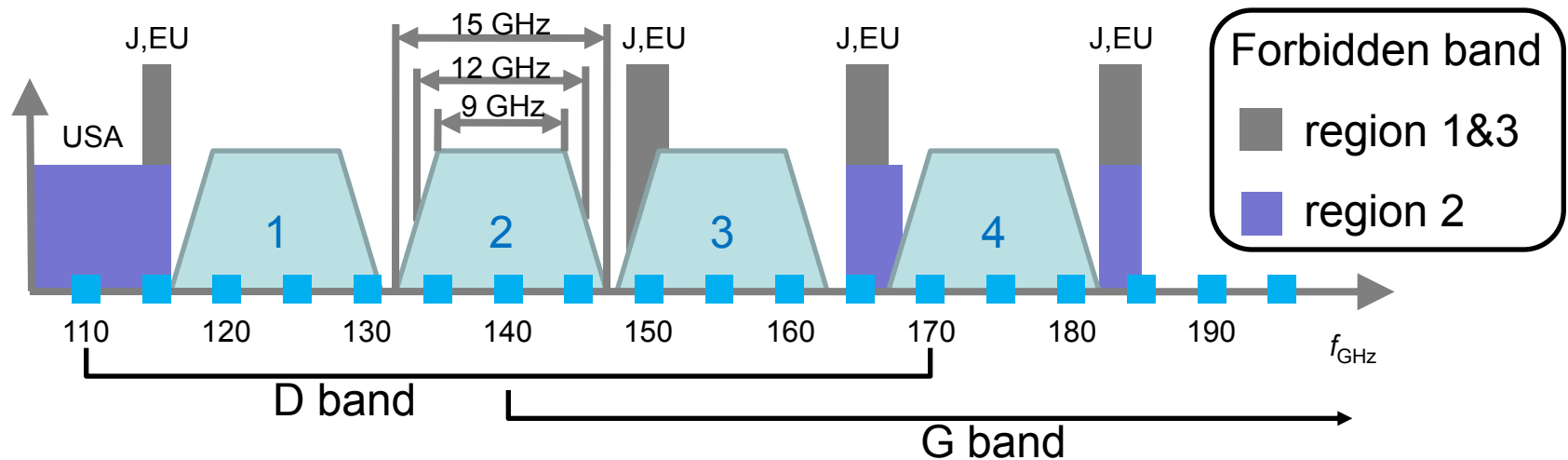


When channels are allocated in D and G bands, three channels are available in worldwide as in 60GHz bands (IEEE 802.15.3c).
 cf: 60GHz-band 2GHz/ch
 D-band+ 15GHz/ch

Dual-Channel ASK Receiver


Input : ASK Signal (120GHz)

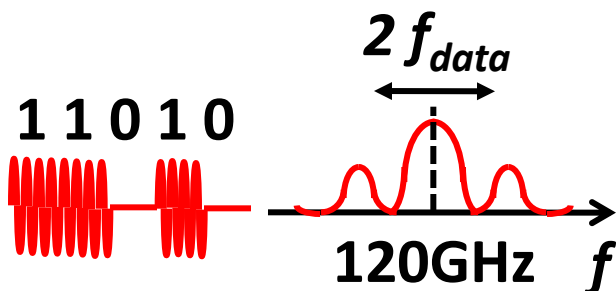

Input : ASK Signal (140GHz)

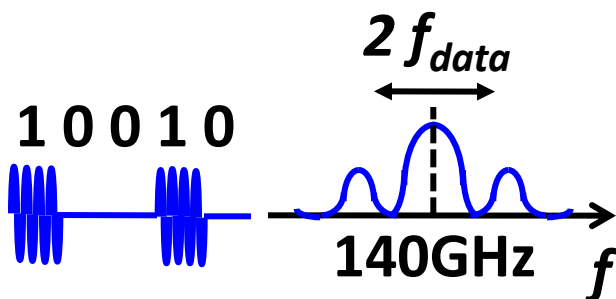


Data Rate : f_{data} [bps]

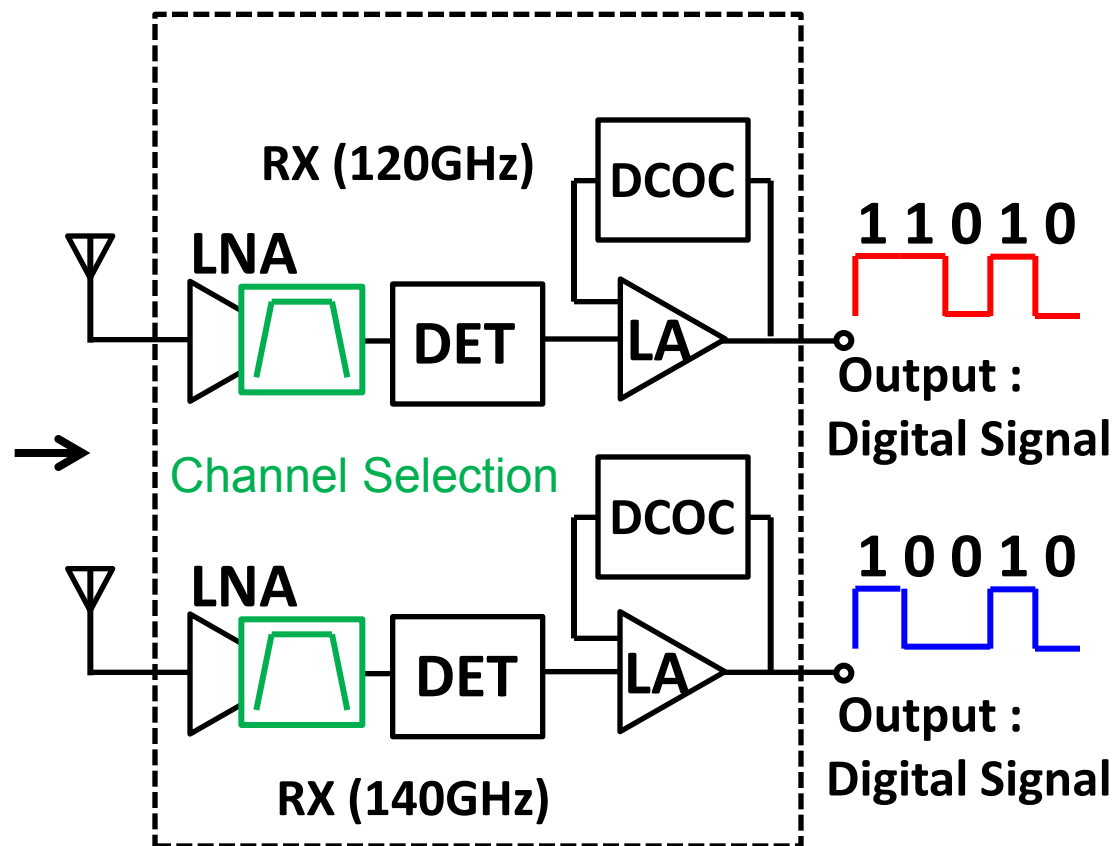


Channel Selection is required for receivers.


Channel Selection using LNA

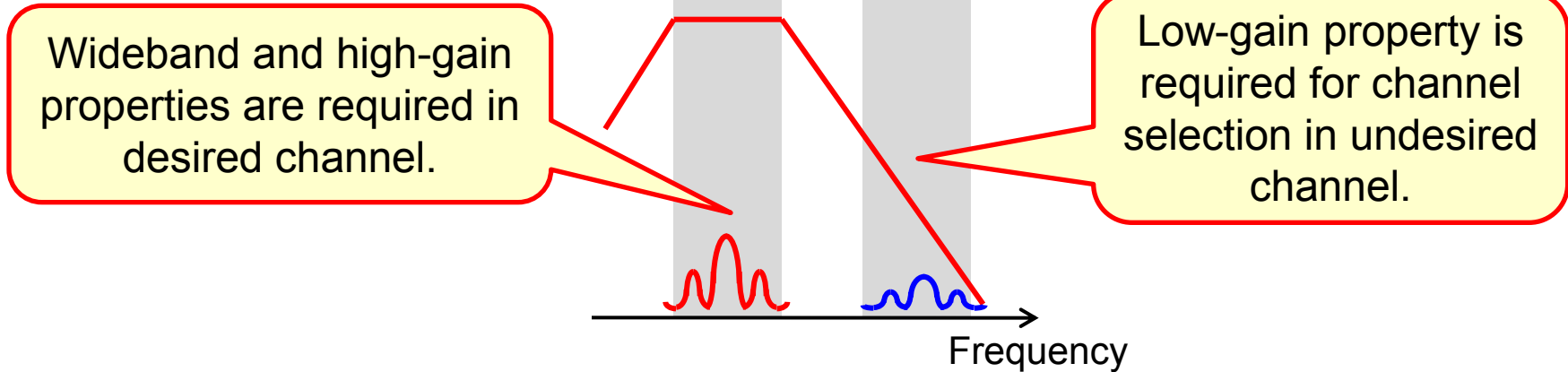


120-GHz LNA
5 stage cascaded amplifier

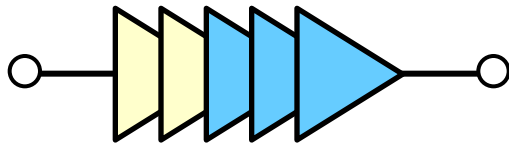

140-GHz LNA
6 stage cascaded amplifier

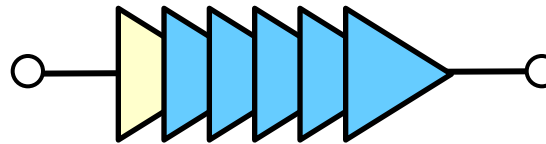

 Cascode amplifier

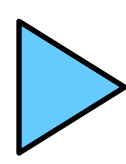
 Common source amplifier

Cascode amplifier : Stability

Common-source amplifier : High gain

Matching frequencies are different : Wideband Gain Flatness

Chip micrograph

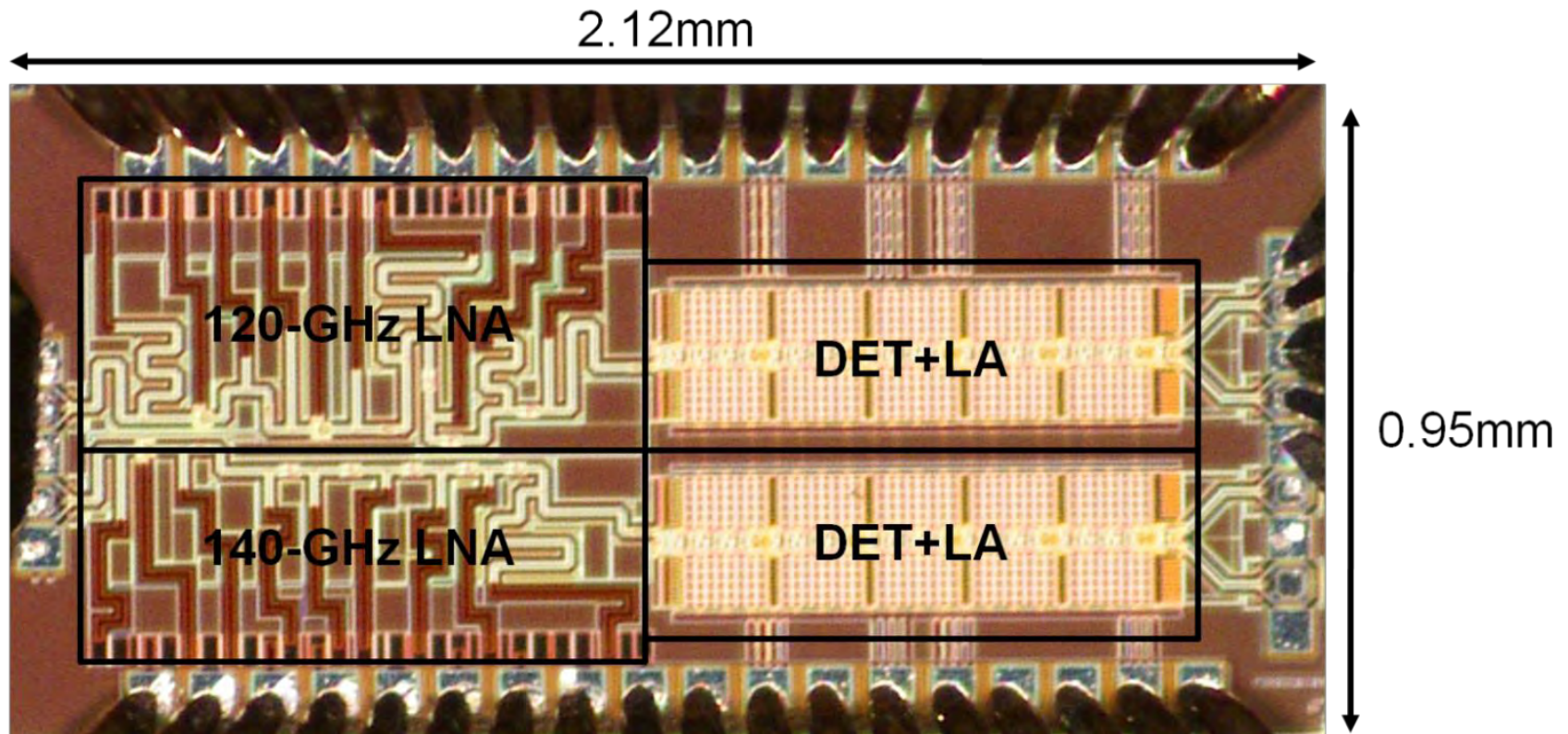

65nm CMOS Technology


Supply Voltage: 1.2V

Power Consumption: 85.7mW (120GHz-RX)


111.7 mW (140GHz-RX)

Frequency Response of LNA

Measured BER

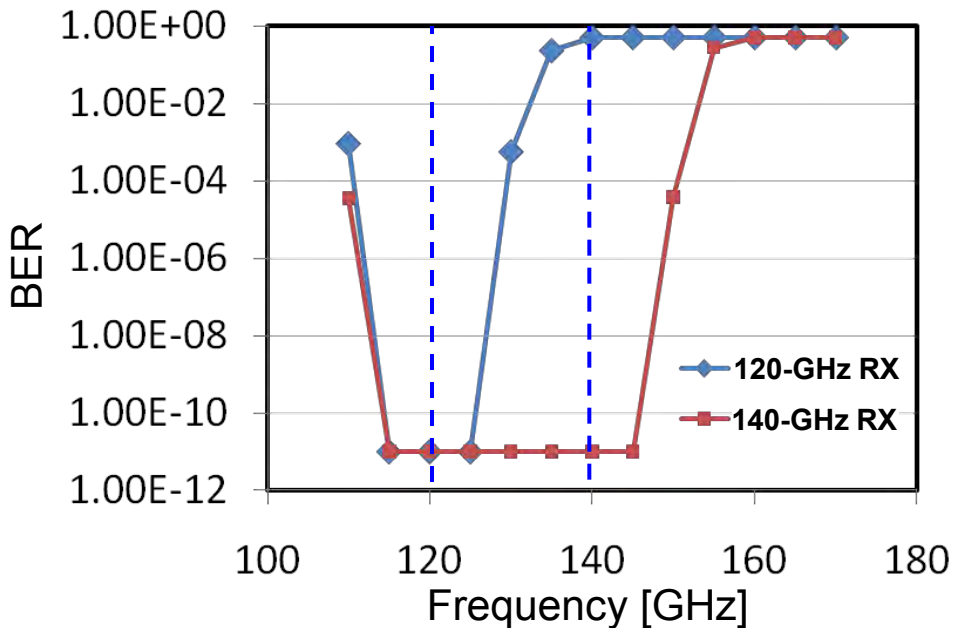


Measured gain of LNA


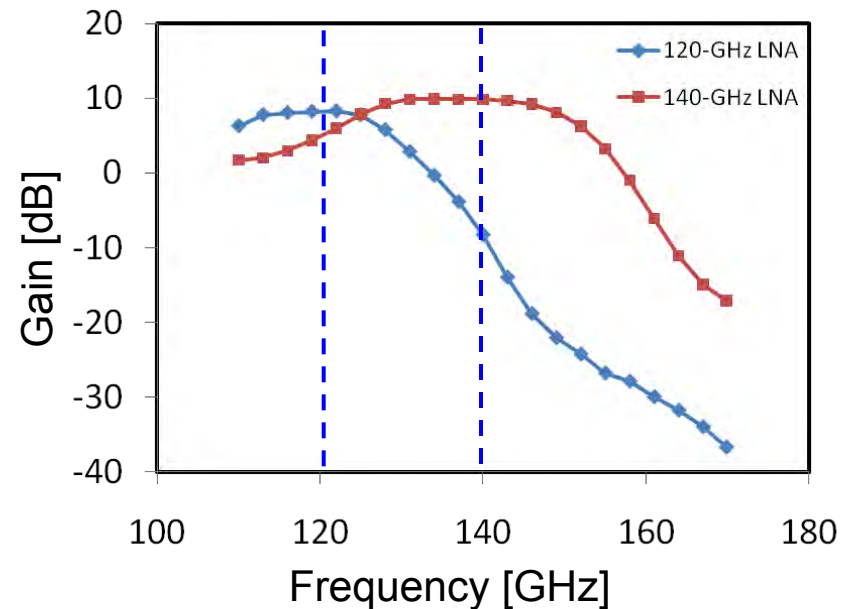


Gain bandwidth of 140-GHz LNA is too wide.
Channel selection is degraded.

Wireless Measurement

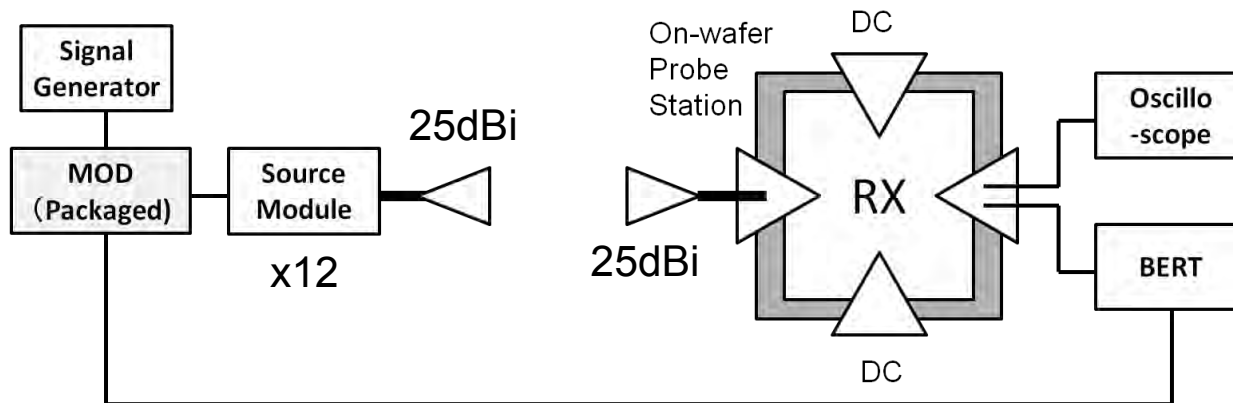

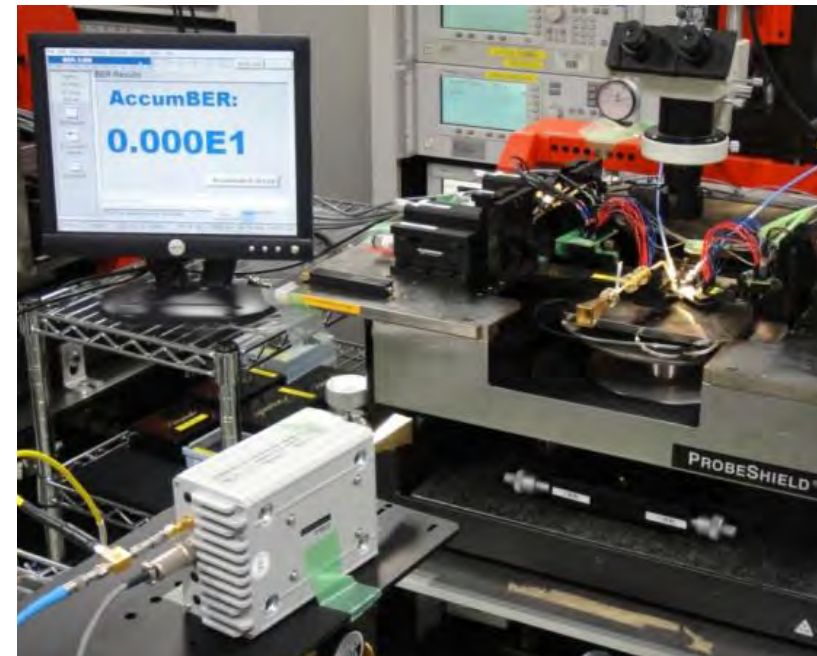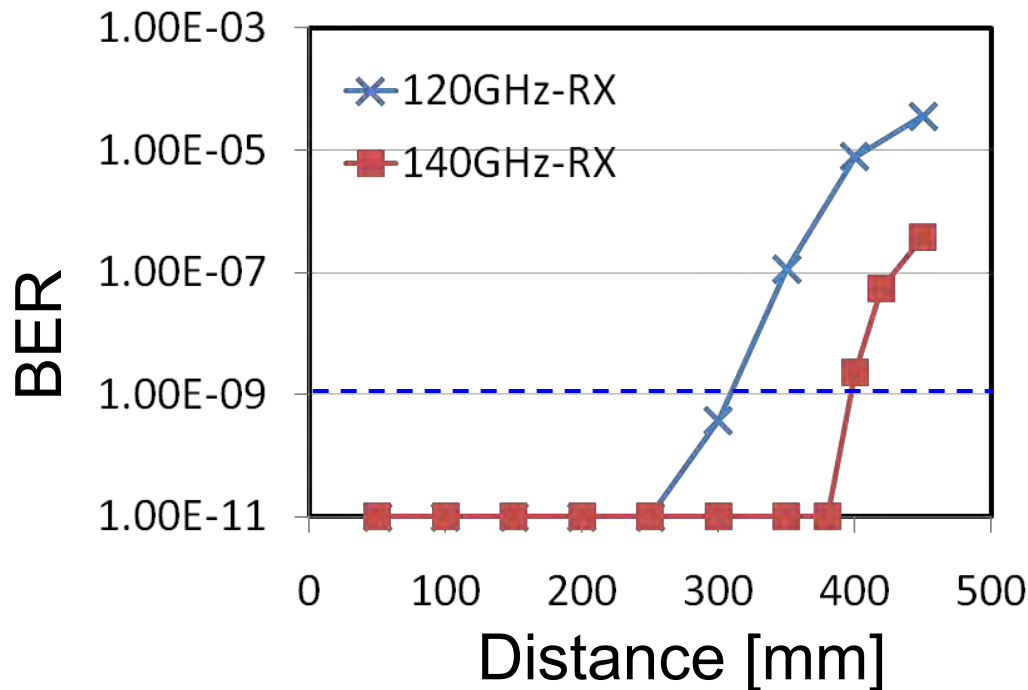Pout@TX-ANT:
-7.8 dBm (120GHz)
-7.2 dBm (140 GHz)
1Gbps 2⁷-1 PRBS



Benchmark Result

	Technology	Frequency [GHz]	# of Channel	Power Consumption [mW]	BER	Maximum Data Rate [Gbps]	Communication Distance [m]
[2]	InP-HEMT	120	Single	750	1.00E-12	10	200
[3]	SiGe BiCMOS	140	Single	1500 (*)	N/A	4	1.15
[4]	65nm CMOS	140	Single	N/A	N/A	N/A	N/A
[5]	SiGe BiCMOS	160	Single	1473	N/A	N/A	N/A
[6]	65nm CMOS	120	Single	80.9 (**)	1.00E-09	9	N/A
This work	65nm CMOS	120 /140	Dual	85.7 (120GHz) 111.7 (140GHz)	1.00E-11	3.0 (120GHz) 3.6 (140GHz)	0.3 (120GHz) 0.4 (140GHz)

(*) Power consumption of transmitter is included

(**) Low-noise amplifier is not included

Required energy per bit : 29pJ/bit (120GHz-RX), 31pJ/bit (140GHz-RX)

Winning Solution

Rick Roberts (Intel)



CMOS possibility for THz is infinite.

Acknowledgements

- This study was partially supported by The Semiconductor Technology Academic Research Center (STARAC), the Core Research for Evolutional Science and Technology (CREST) of the Japan Science and Technology Agency (JST), Extremely Low Power (ELP) project supported by the Ministry of Economy, Trade and Industry (METI) and the New Energy and Industrial Technology Development Organization (NEDO).