

---

# Designing CMOS Wireless System-on-a-chip – analog/RF perspective

---



**David Su**, [dsu@qca.qualcomm.com](mailto:dsu@qca.qualcomm.com)  
*Qualcomm Atheros, San Jose, California*


Japan, Nov 2011

# Outline

---


- **System-on-a-Chip Overview**
  - Transceiver Building Blocks
  - Integration issues
- **System-on-a-Chip Example:**
  - A 1x1 802.11n WLAN SoC
    - Terrovitis et al, 2009 ESSCirC
- **Conclusion**

# SoC Trends: WLAN (1996)

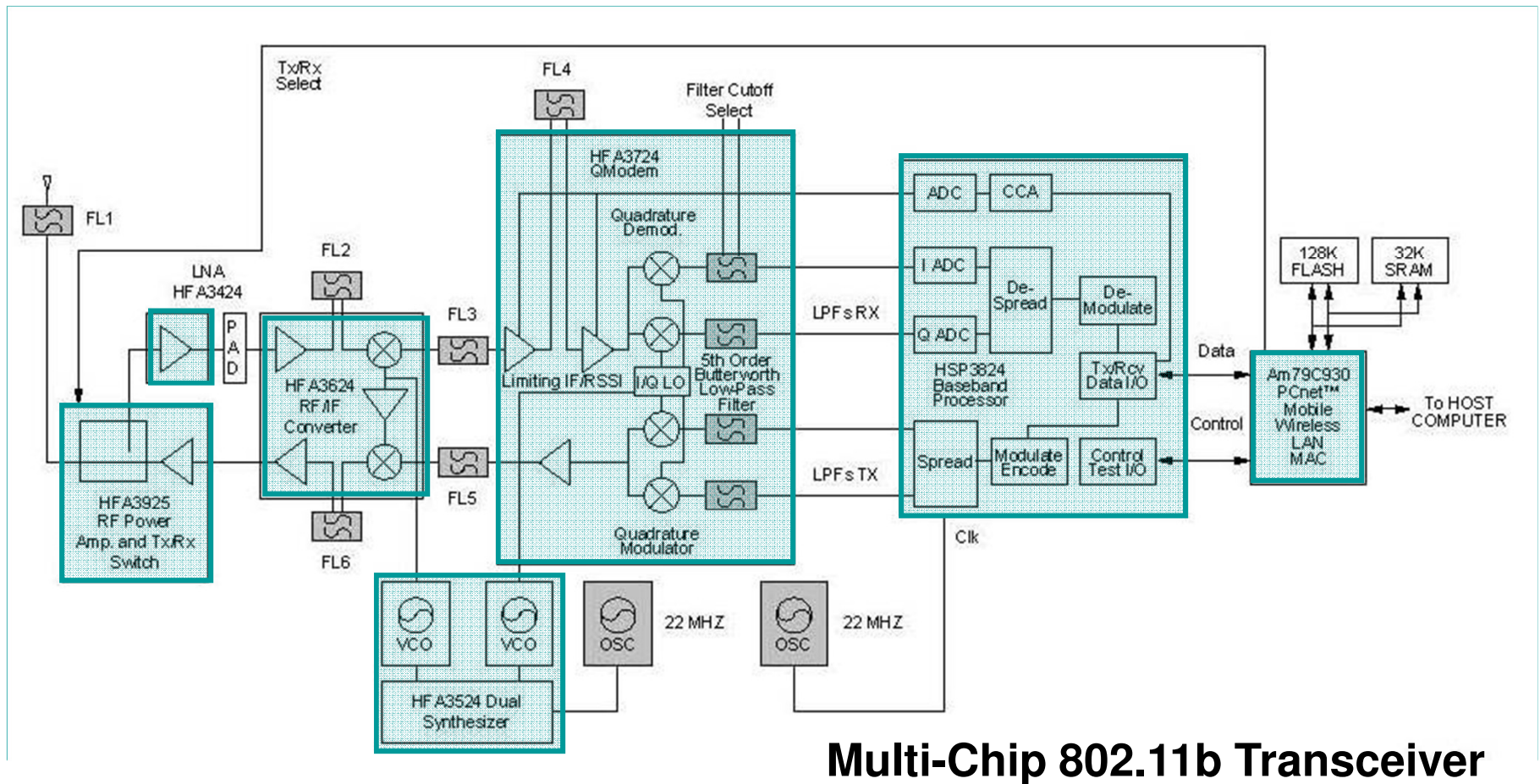


Prism WLAN chipset (Harris Semi) AMD App Note ([www.amd.com](http://www.amd.com))

# WLAN Integration Story

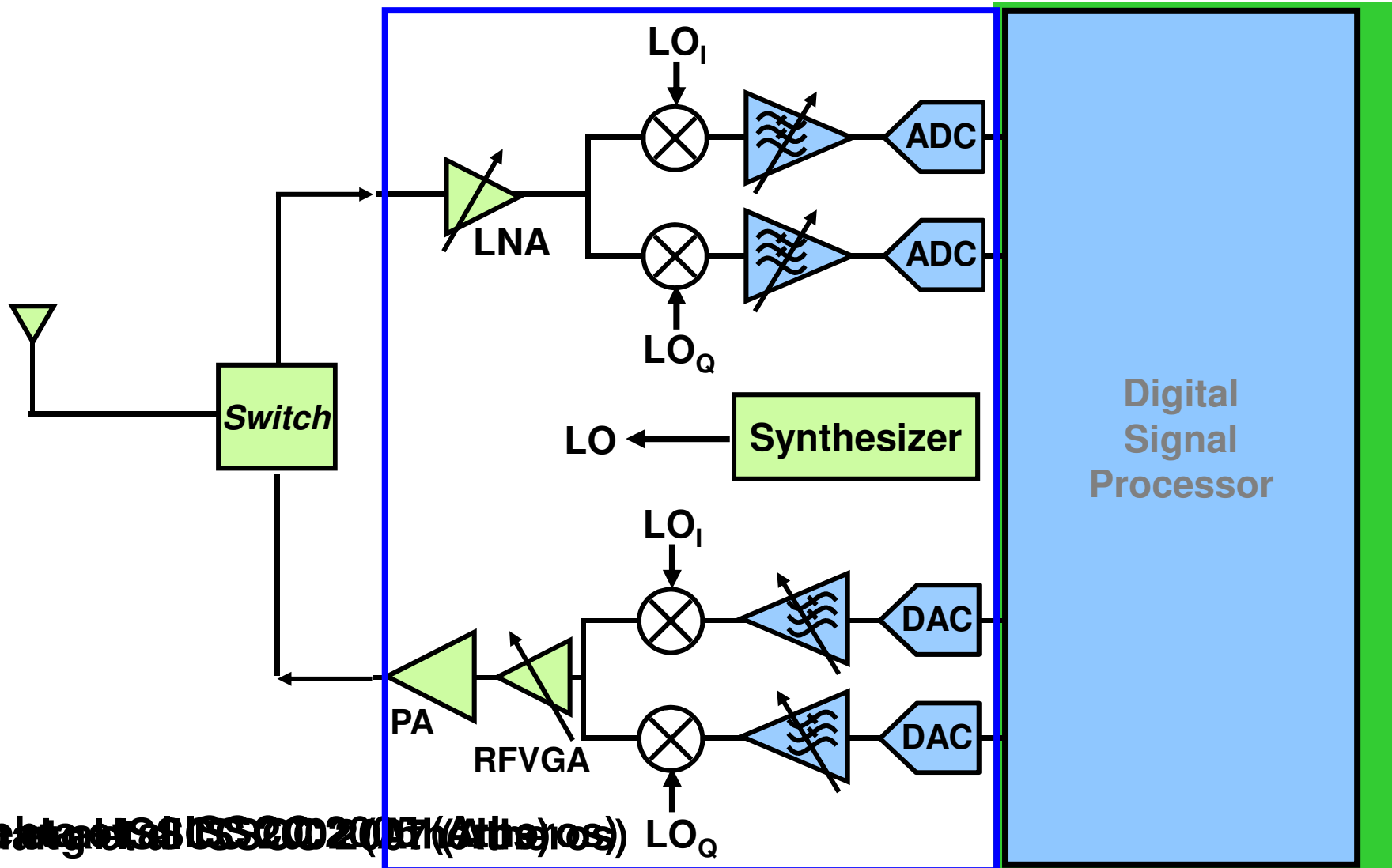

© Intel, 2007 (All rights reserved)

# Soc Trends: WLAN (2011)

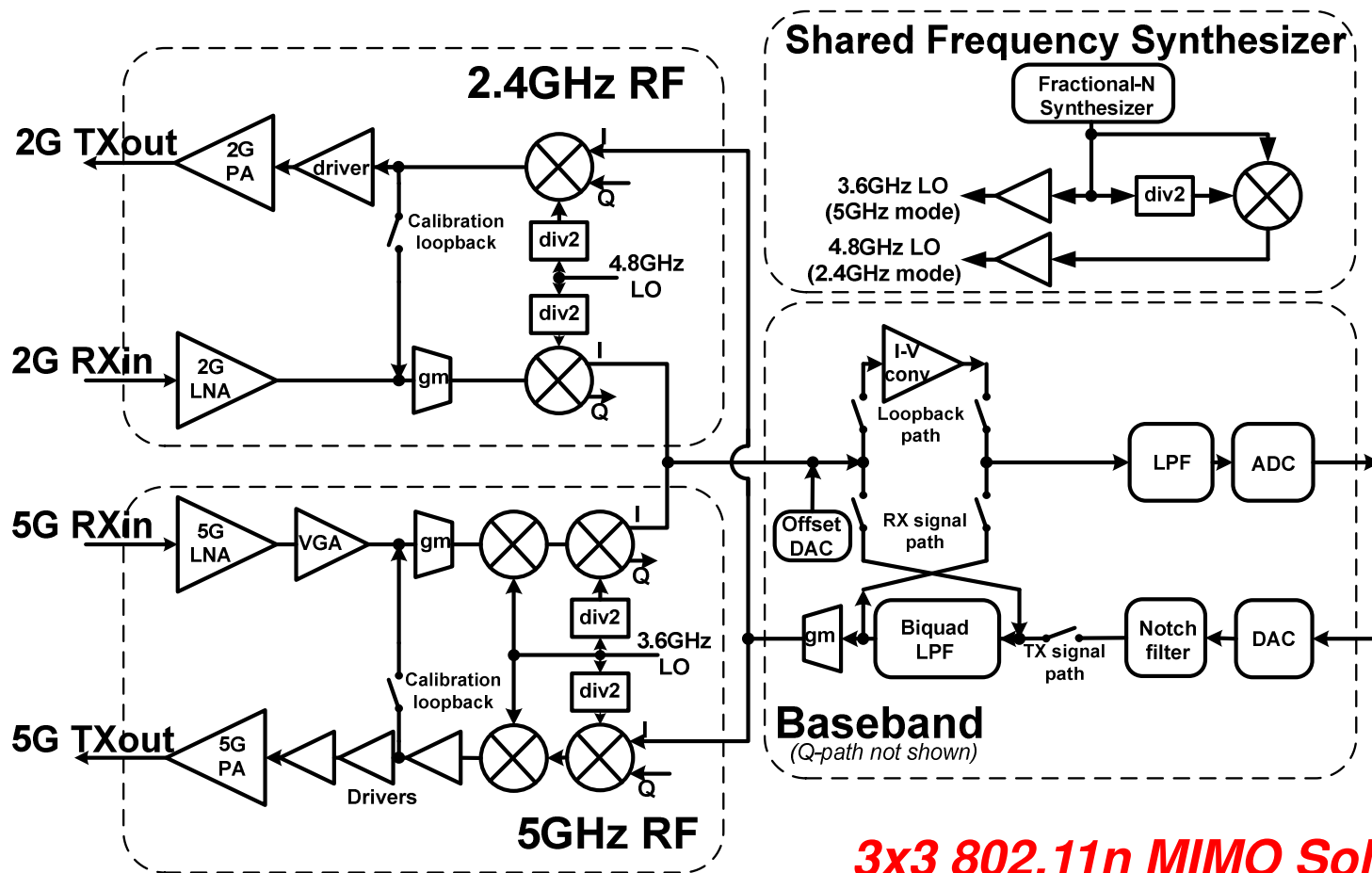

**3x3 802.11n MIMO Solution  
(1 of 3 chains shown)**


Abdollahi-Alibeik et al, ISSCC 2011 (Atheros)

# Advantages of SoC Integration

---

- **Increased functionality**
- **Smaller Size / Form Factor**
- **Lower Power**
  - On-chip interface
- **Lower Cost**
  - Single package
  - Ease of manufacture
    - Minimum RF board tuning
    - Reduced component count
      - Improved reliability

# Cost of WLAN Throughput

 


Zargari, 2007 VLSI Symposium Short Course

(c) D. Su, 2011

Japan


p.7

# Evolution of 802.11 WLAN PHY Rates

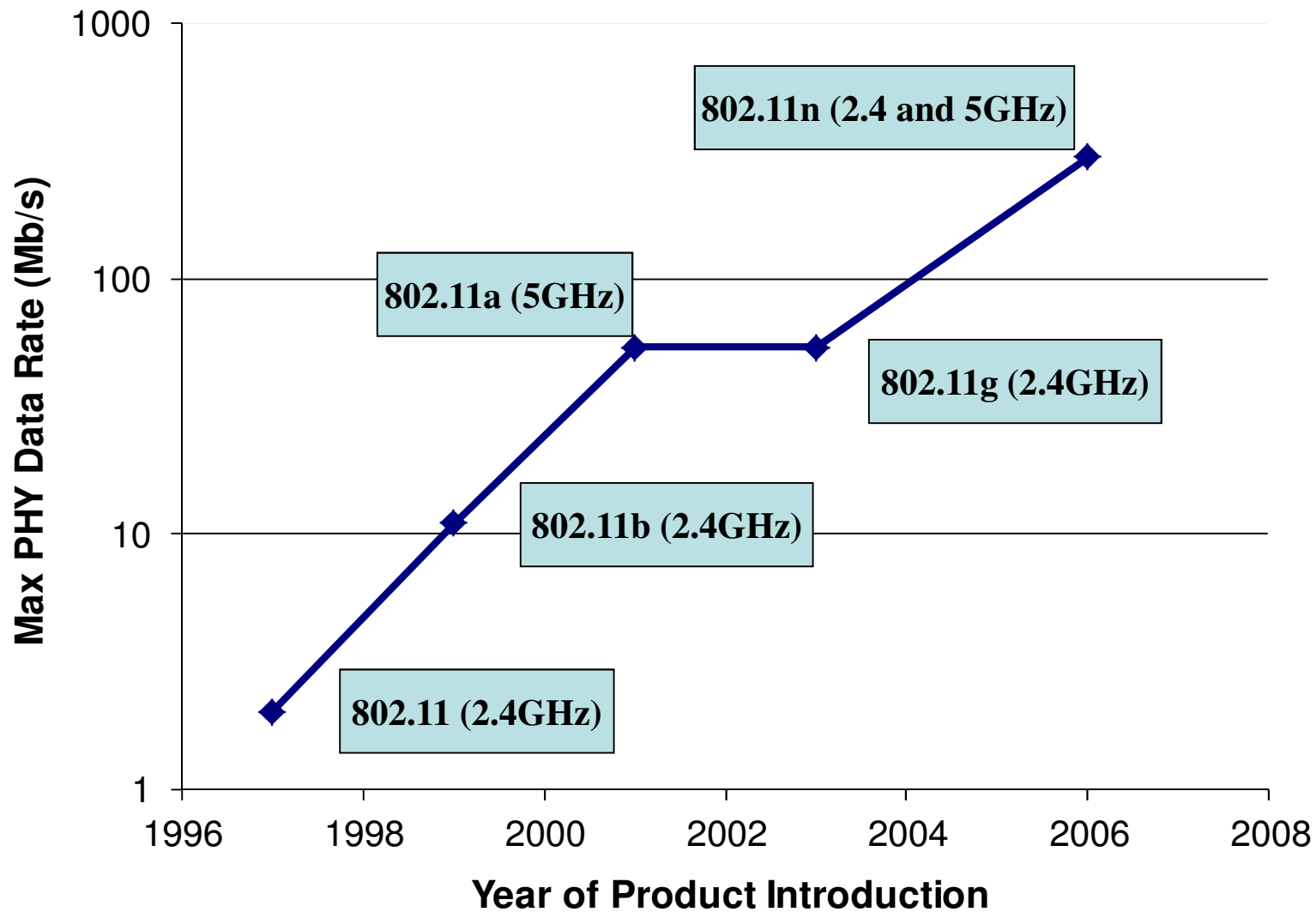



# Wireless SoC Block Diagram

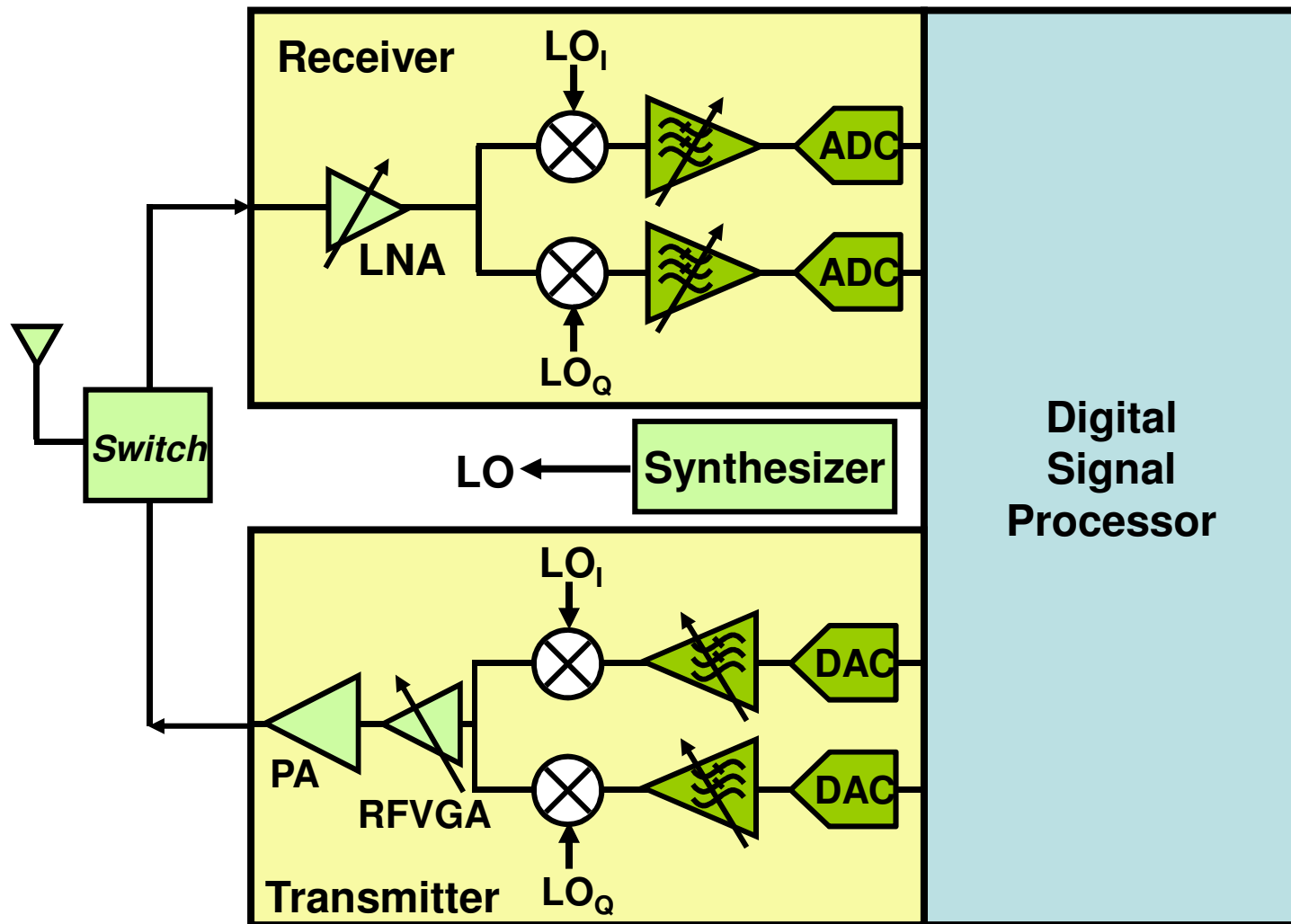


# Low Noise Amplifier

---


- **Low Noise Figure**
  - Sufficient gain
- **Able to accommodate large blockers**
  - Large Dynamic Range
  - Large Common-mode Rejection
  - High Linearity

# LNA with Cascoded Diff Pair

 

- Input match
- Noise Figure

# LNA with Switchable Gain

 

- CMRR at RF
- Switchable gain for high DR

Zargari et al, JSSC Dec 2004 (Atheros)

# Power Amplifier

---

## General Specifications


- ❑ Output power: Saturated power, P1dB
- ❑ Efficiency
- ❑ Linearity: OIP3/IM3, Harmonics
- ❑ Stability/Robustness: VSWR

## Digital Communications


- ❑ Large Peak to Average Ratio → linearity
  - ❑ Transmit Spectral Mask – modest linearity
  - ❑ Error Vector Magnitude (EVM) – high linearity
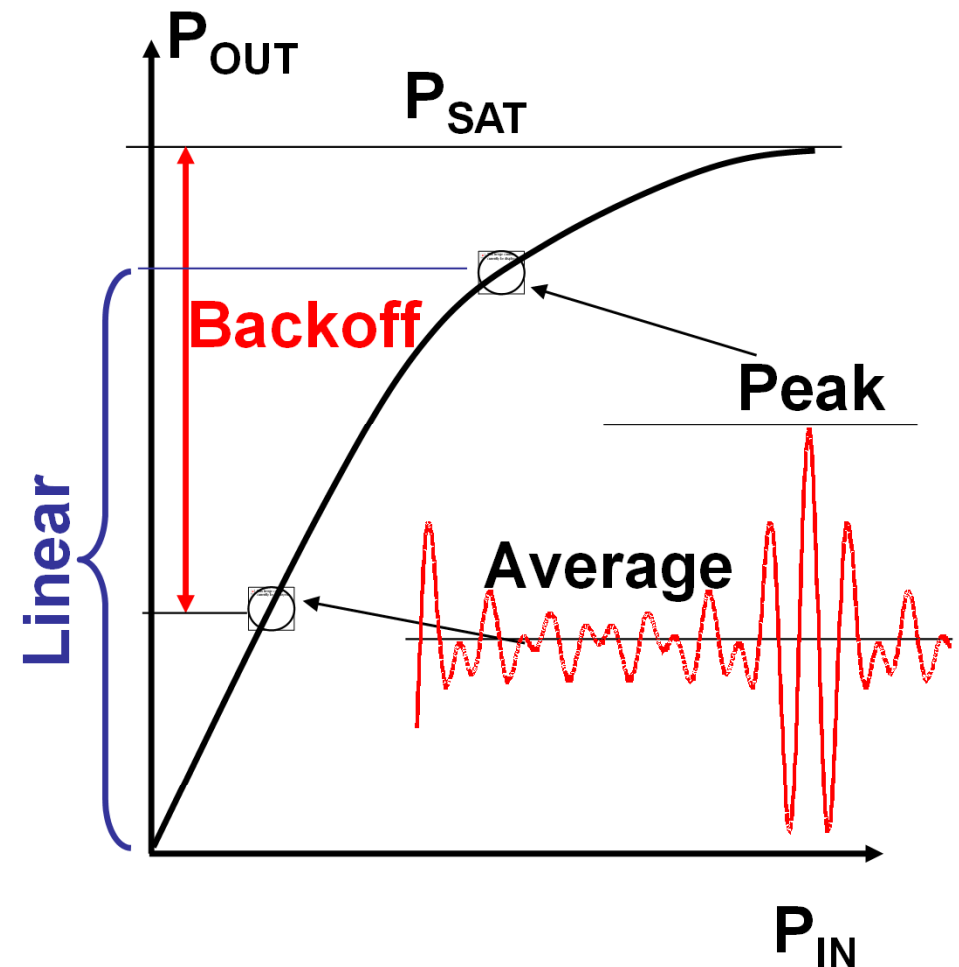
# Peak to Average Ratio


- Information encoded in both amplitude and phase
- Spectral efficient but power inefficient because average output power is much less than maximum output power




# Cascoded Power Amplifier

 

 - Cascoding advantages
  - 3.3V supply voltage
  - Stability
- Capacitive Level-shift
- Differential
  - Off-chip balun



# Cascoded Power Amplifiers

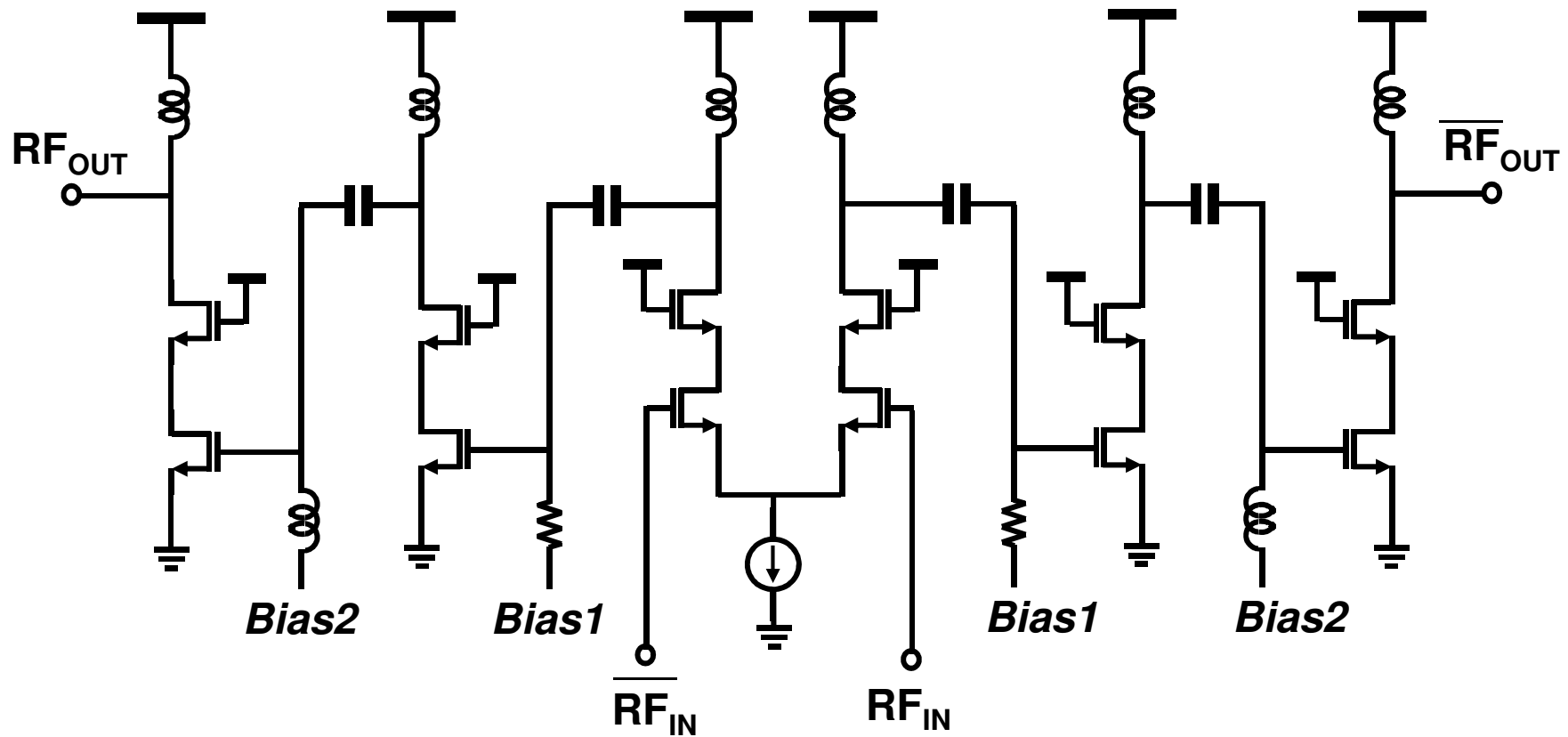


$$P_{MAX} = 22 \text{ dBm}$$

$$P_{OFDM} = 17.8 \text{ dBm (BPSK)}$$

Zargari et al, JSSC Dec 2002 (Atheros)




# Measured Power vs Data Rate

 

# System-on-a-Chip Integration


---

 

- ✓ **Digital Assistance: Calibration Techniques**
- **Digital Interference: Noise Coupling**

# Digital Assisted Analog/RF Design

---

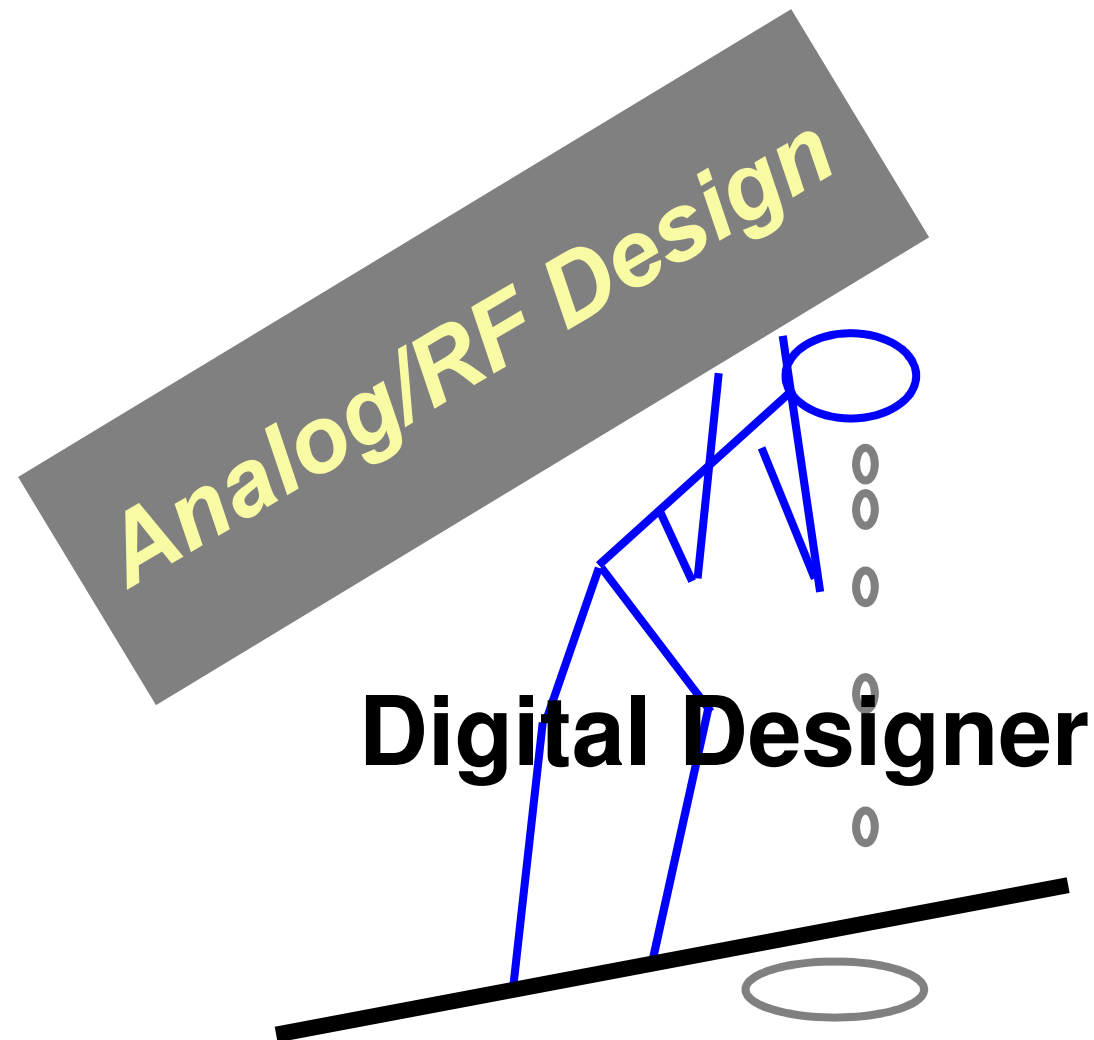

# Digital Assisted Analog/RF Design

---

- **Using digital logic to compensate/correct for imperfections of analog and RF circuits to enable:**
    - **Lower power,**
    - **smaller area,**
    - **improved reliability of analog/RF**
- ➔ resulting in lower cost and improved performance**

# Digital Assistance: Calibration Issues

---


- **Desired properties of calibration:**
  - **Independent of temperature, aging, frequency**
  - **Inexpensive (in time, area and power) to implement**
  - **Do not interfere with system performance**
- **Wireless System-on-a-Chip advantage:**
  - **Calibration building blocks already exist on-chip: transmitter and receiver, data converters, and CPU**
  - **No package pin limitation**

# Calibration Techniques

---


- **Test Signal**
  - **Dedicated test signals from DAC: Tx carrier leak**
  - **RF loop back: Receive filter bandwidth**
  - **Thermal noise: Rx Gain**
  - **Live Rx (signal) traffic: Rx I/Q mismatch**
- **Observation Signal**
  - **Dedicated ADC**
  - **Implicit ADC: Comparator**
- **Tuning Mechanism**
  - **Dedicated DAC**
  - **Implicit DAC:**  
**Selectable capacitors, resistors, transistors**
  - **Digital tuning (if signal is already digital)**

# RF loop back: Tx Carrier Leak

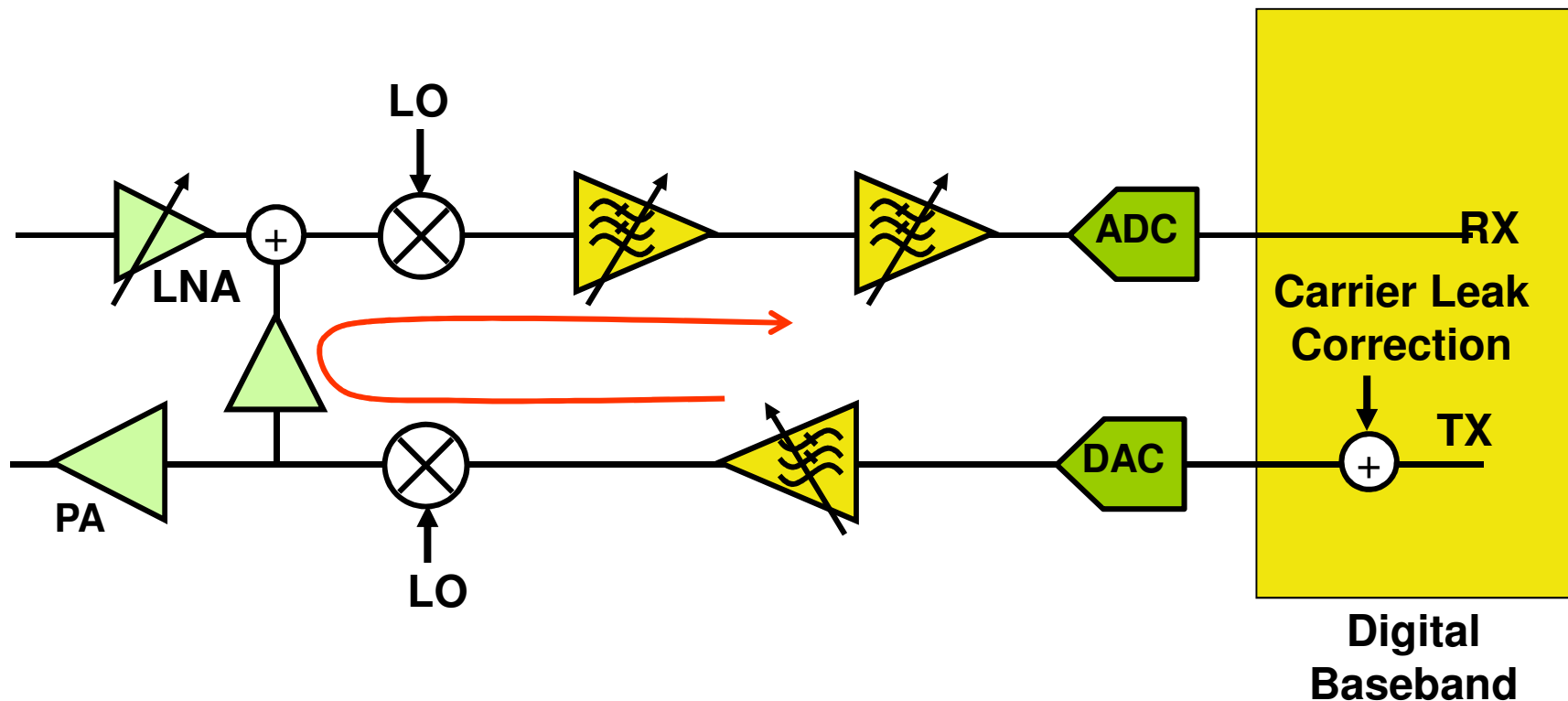

- **Test signal: Tx DAC**
- **Observation signal: RF loop back to Rx ADC**
- **Tuning: Carrier Leak Correction at Tx DAC input**

# Calibrating Low-pass gm-C Filter

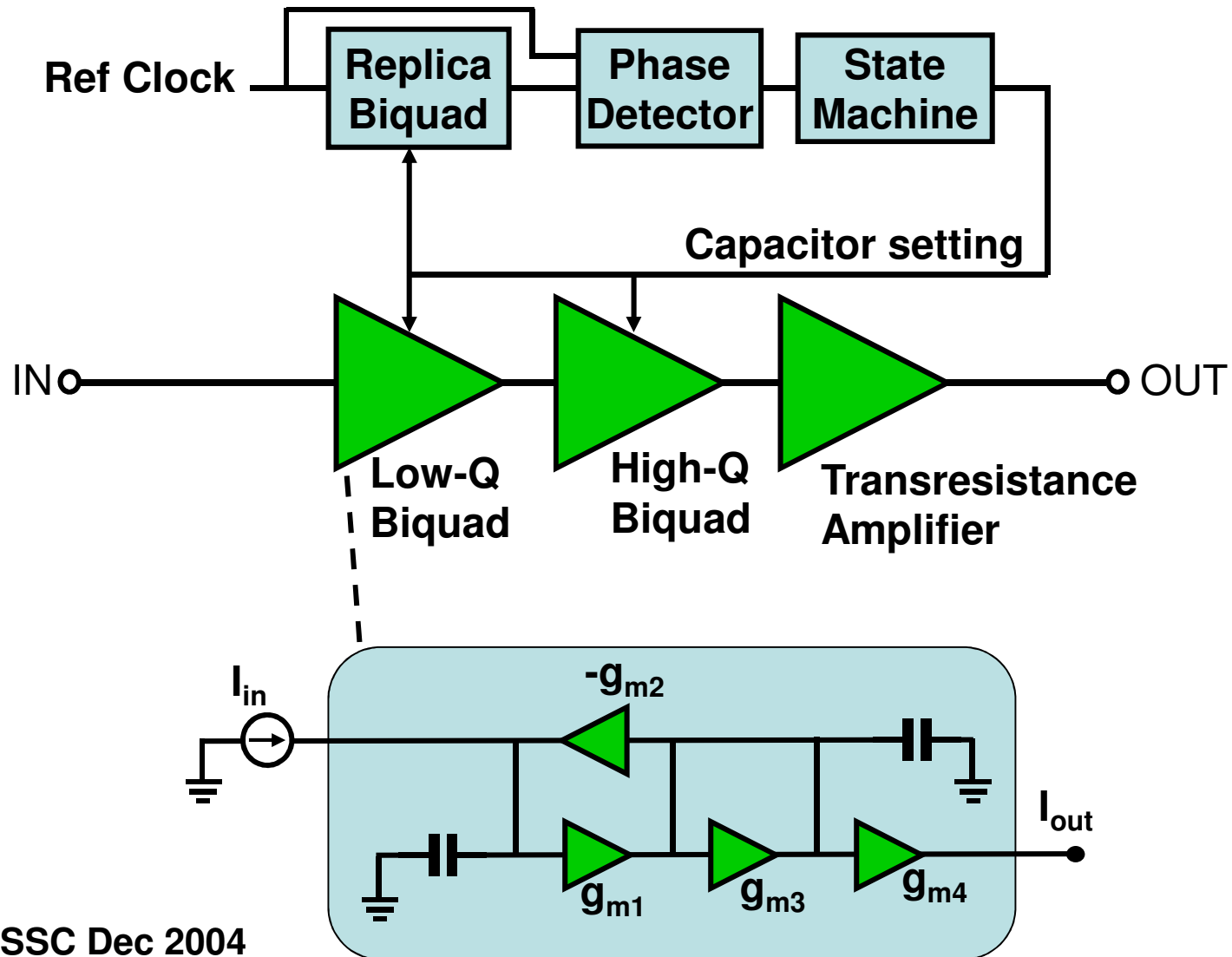

Zargari et al, JSSC Dec 2004

(c) D. Su, 2011


Japan

p.24



# System-on-a-Chip Integration


---

 

- **Digital Assistance: Calibration Techniques**
- ✓ **Digital Interference: Noise Coupling**


# Digital Interference

---

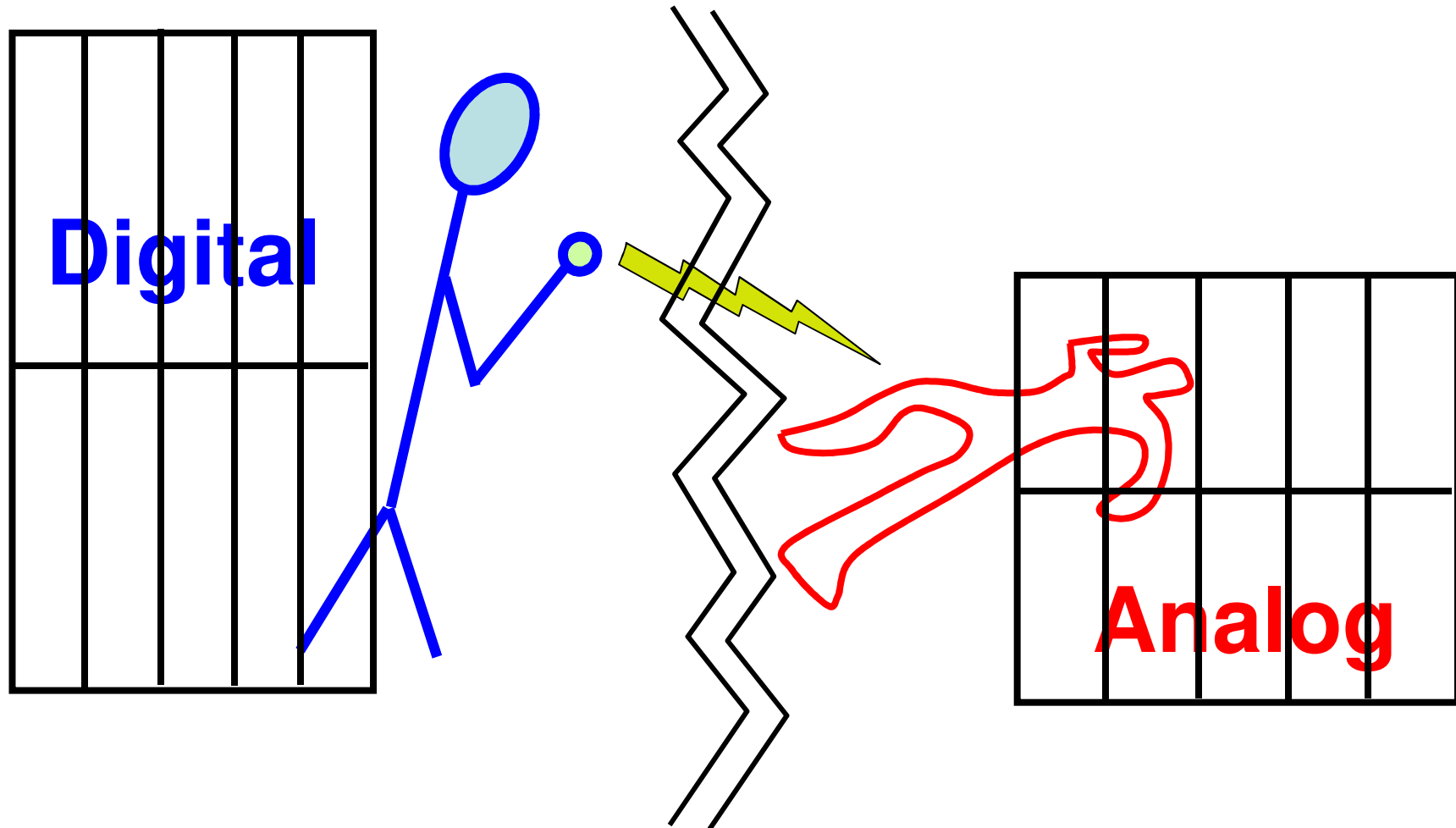

# Digital Interference: Noise Coupling

**Aggressor**

 


**SOURCE:**  
Noisy Digital Circuits

**Accomplice**

**MECHANISM:**  
Noise Coupling



**Victim**

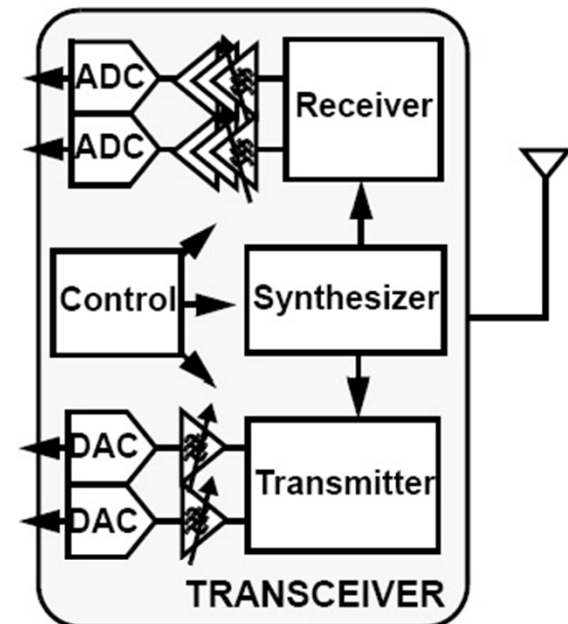

**DESTINATION:**  
Sensitive Analog Circuits

# Noise Source

---

## *Pacify the aggressor*

- **Reduce noise by turning off unused digital**
  - Clock gating
  - Avoid oversized digital buffers
- **Stagger digital switching**
  - Avoid large number of digital pads switching simultaneously
  - Avoid switching digital logic at the same sampling instance of sensitive analog

# Noise Destination

---

## *Strengthen the victim*

- **Increase immunity of sensitive analog and RF circuits**
  - **Common-mode noise rejection**
    - Fully differential topology
  - **Power Supply noise rejection**
    - Good PSRR
    - Dedicated on-chip voltage regulators
- **Avoid package coupling by keeping sensitive nodes on chip**  
**(Example: VCO control voltage)**


# Coupling Mechanism

---

## *Deter the accomplice*

- **Power Supply noise coupling**
  - Separate or star-connected power supplies
- **Capacitive or inductive coupling to sensitive signals and bias voltages**
  - Careful routing of signal traces to reduce parasitic capacitive/inductive coupling
  - Use ground return-path shields
- **Substrate coupling induced  $V_{TH}$  modulation**
  - Low-impedance substrate connection
  - Guard rings
  - Physical separation
  - Deep Nwell

# Frequency Synthesizer

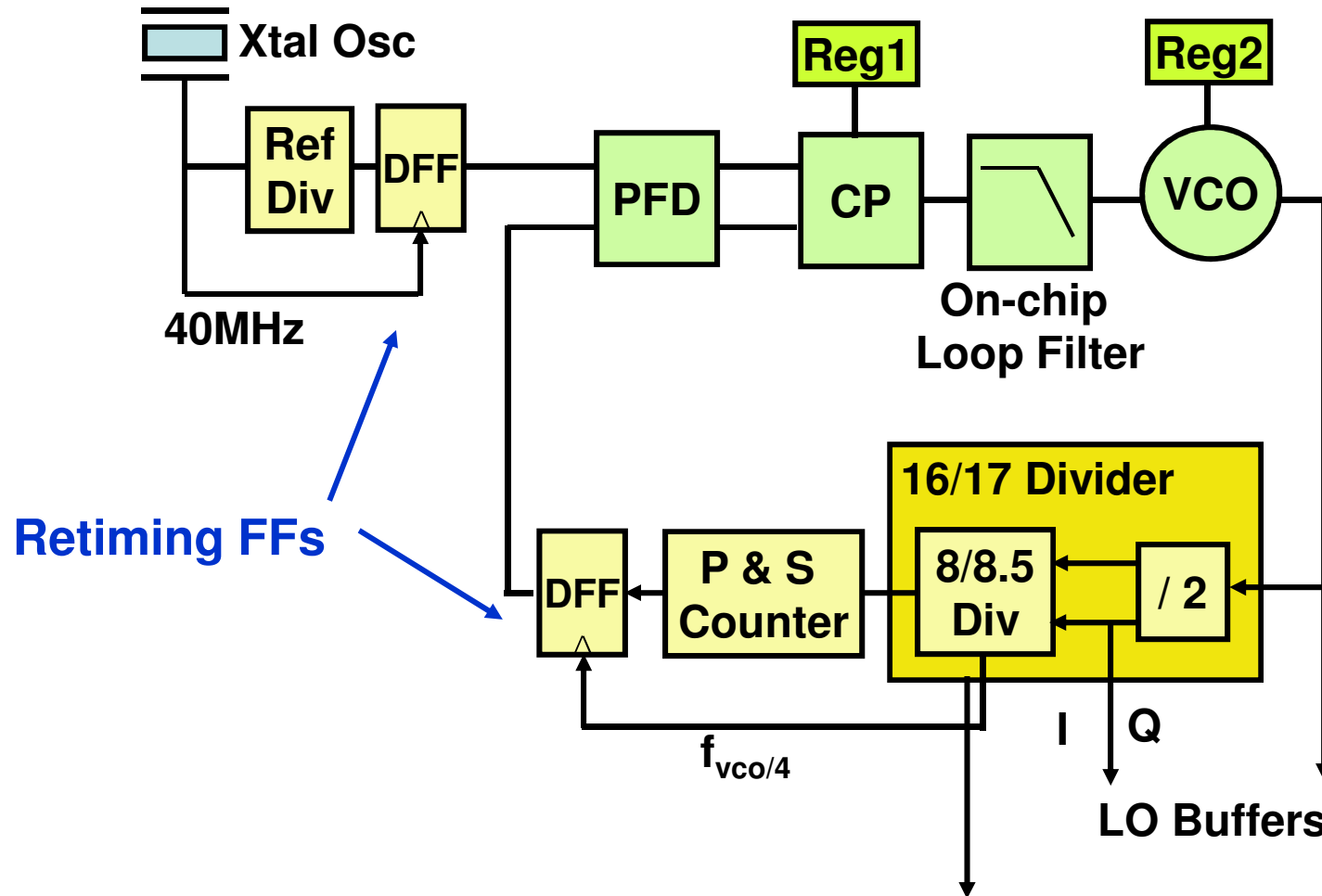

Terrovitis et al, ISSCC 2004 (Atheros)

(c) D. Su, 2011

Japan

p.31

---

# A 1x1 802.11n WLAN SoC with fully integrated RF Front-end Utilizing PA Linearization

---

**Manolis Terrovitis, Michael Mack, Justin Hwang, Brian Kaczynski, Gabriel Tseng\*, Bor-Chin Wang\*, Srenik Mehta, David Su**

**Atheros Communications, Santa Clara, California**

**\*Atheros Communications, Hsinchu, Taiwan**

**From presentation by Dr. Manolis Terrovitis  
at the 35<sup>th</sup> European Solid-State Circuits Conference in  
Athens on September 16, 2009**






# SoC Design Goals

---

- **Design a low cost, small form factor, and high performance 802.11 system**
- **Eliminate external components (Power Amplifier, Low-Noise Amplifier, Transmit/Receive switch)**
- **Power Amp Linearization for maximum transmit linear output power and efficiency**


# SoC Block Diagram

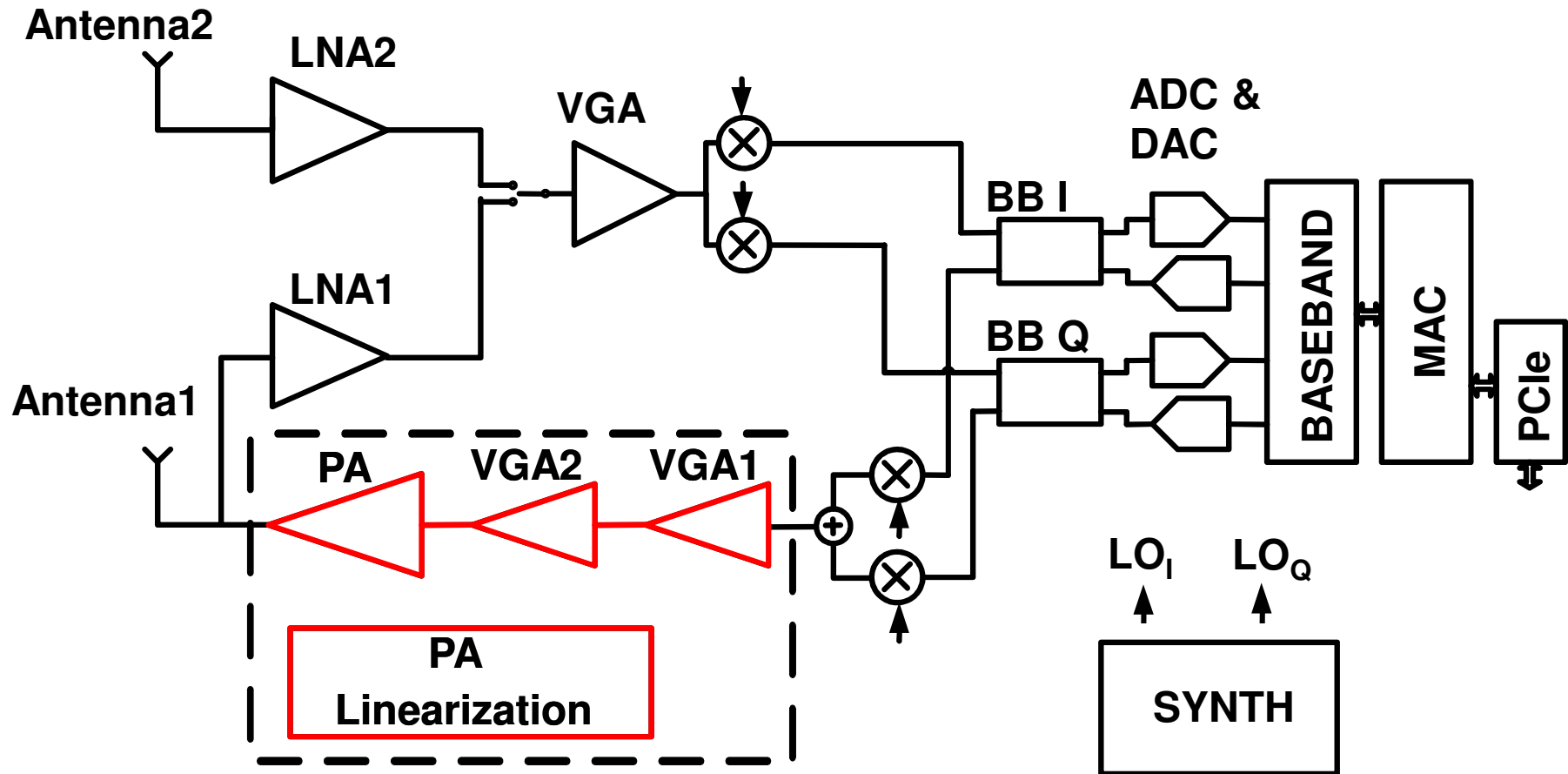

Ref: Zargari et al, Dec. 2008, JSSC.


Terrovitis et al, ESSCIRC 2009 (Atheros)

# Combined RF Frontend

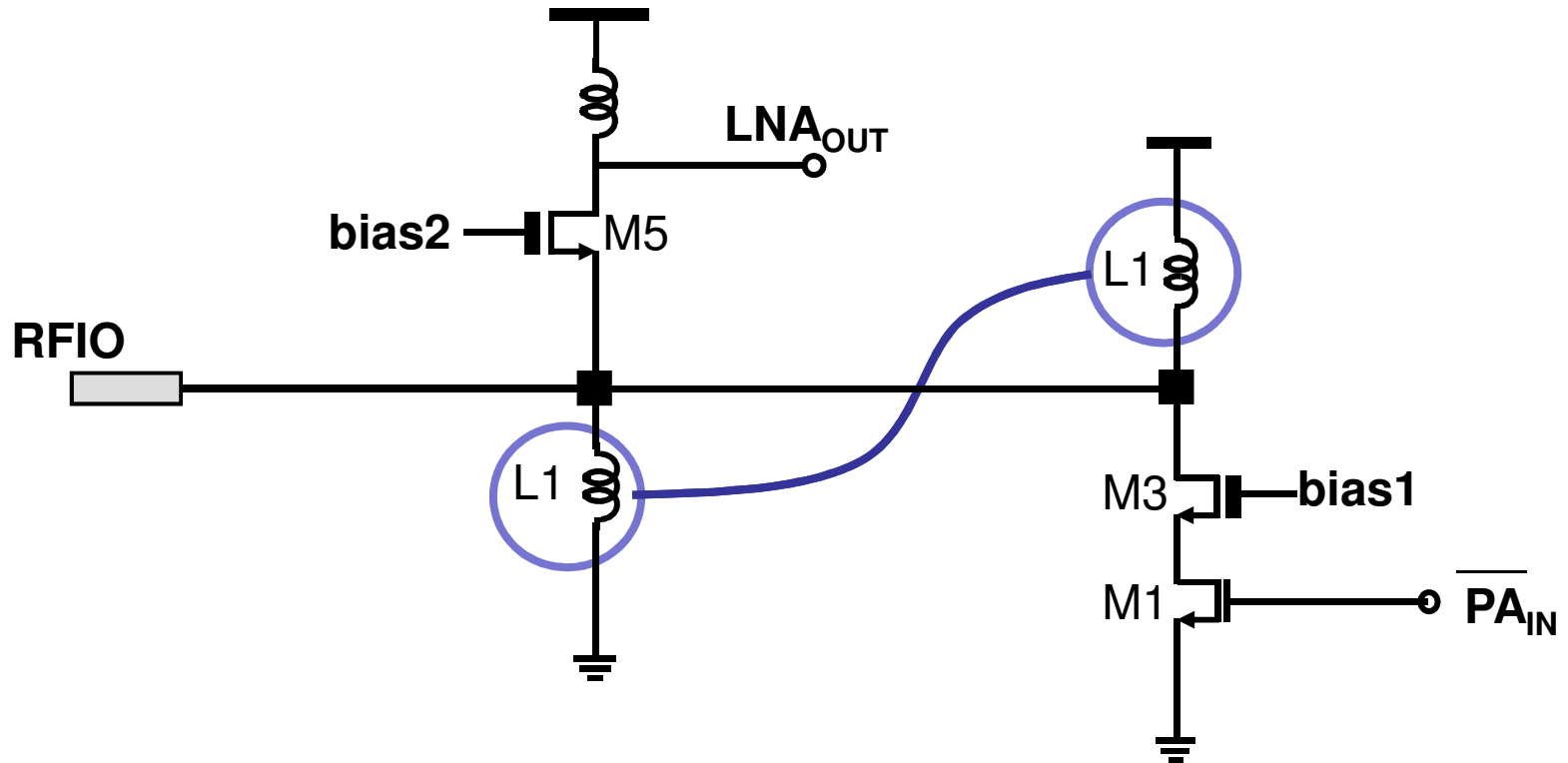

- PA, LNA, T/R Switch
- Large swing
- Low impedance

# Combined RF Frontend

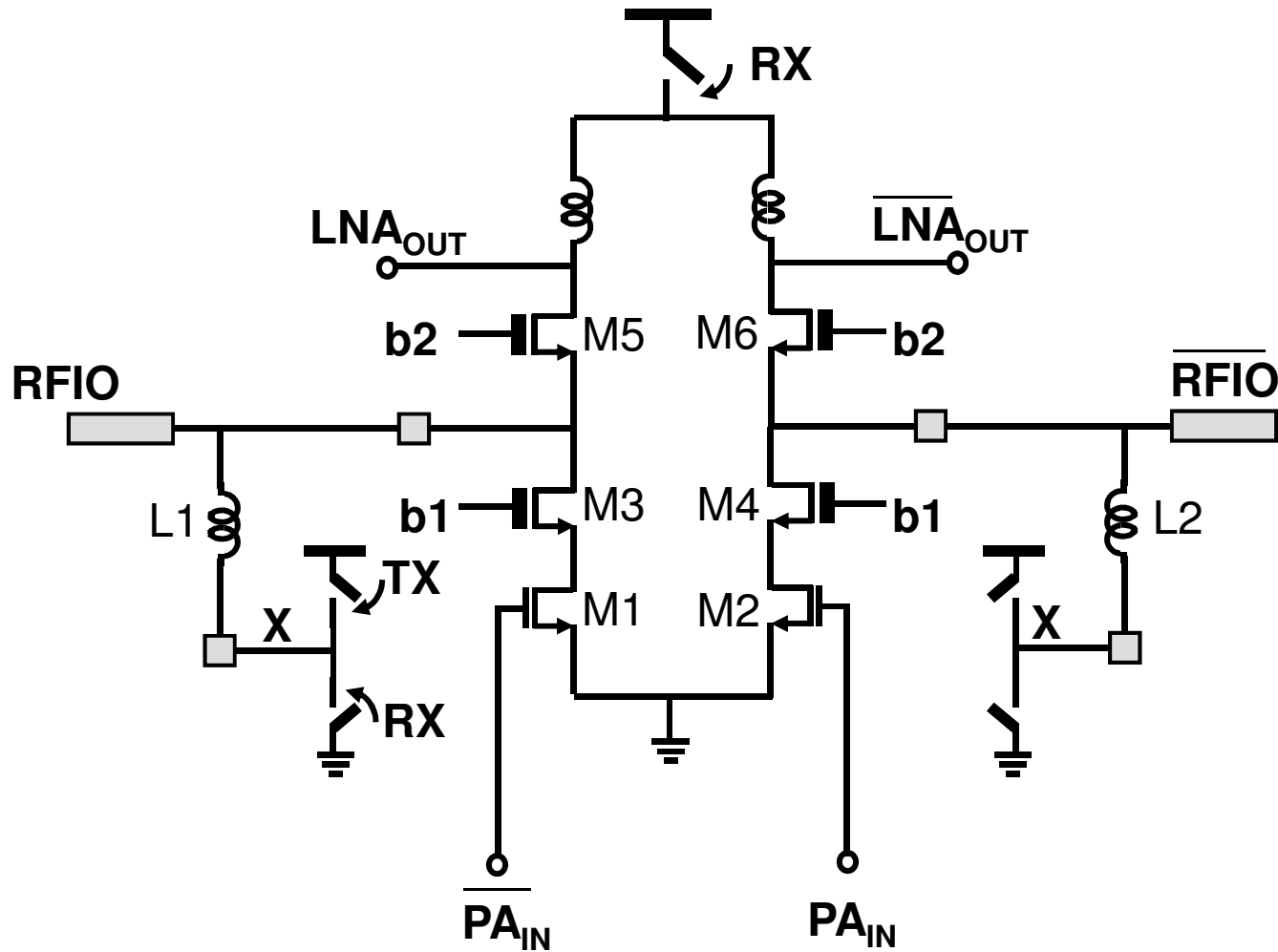

# Linearized RF Power Amp


---

**Transistors are *cheap* on an System-on-a-Chip**

- **Use linearization technique to improve linearity and efficiency of the Power Amplifier**

# Envelope Feedback


---

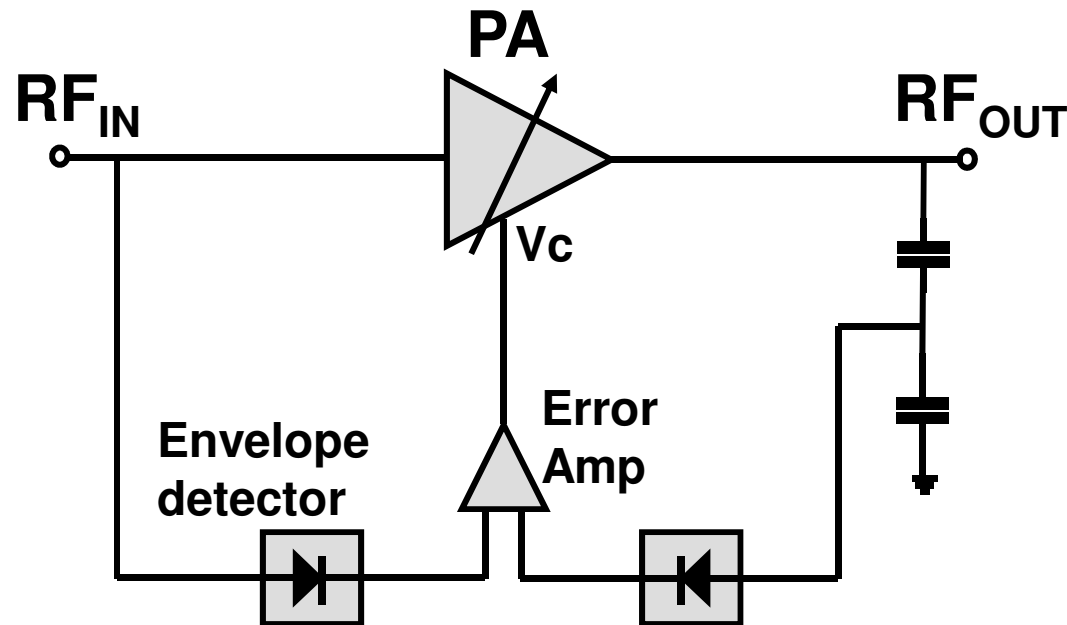


- **Linearizes Gain**
- **Fixes Gain over process and temperature**
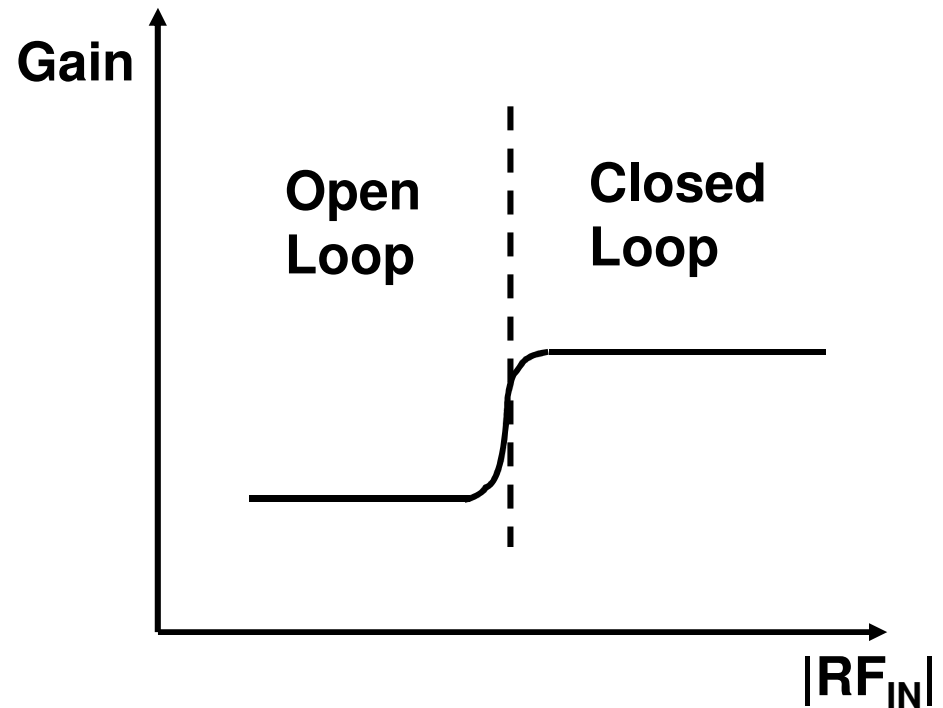
# Envelope FB Linearization Issues

- Phase distortion is not corrected
- Envelope detectors do not respond for low signal
  - Loop opens at low amplitude
  - Offset Correction




# Implemented Feedback Loop

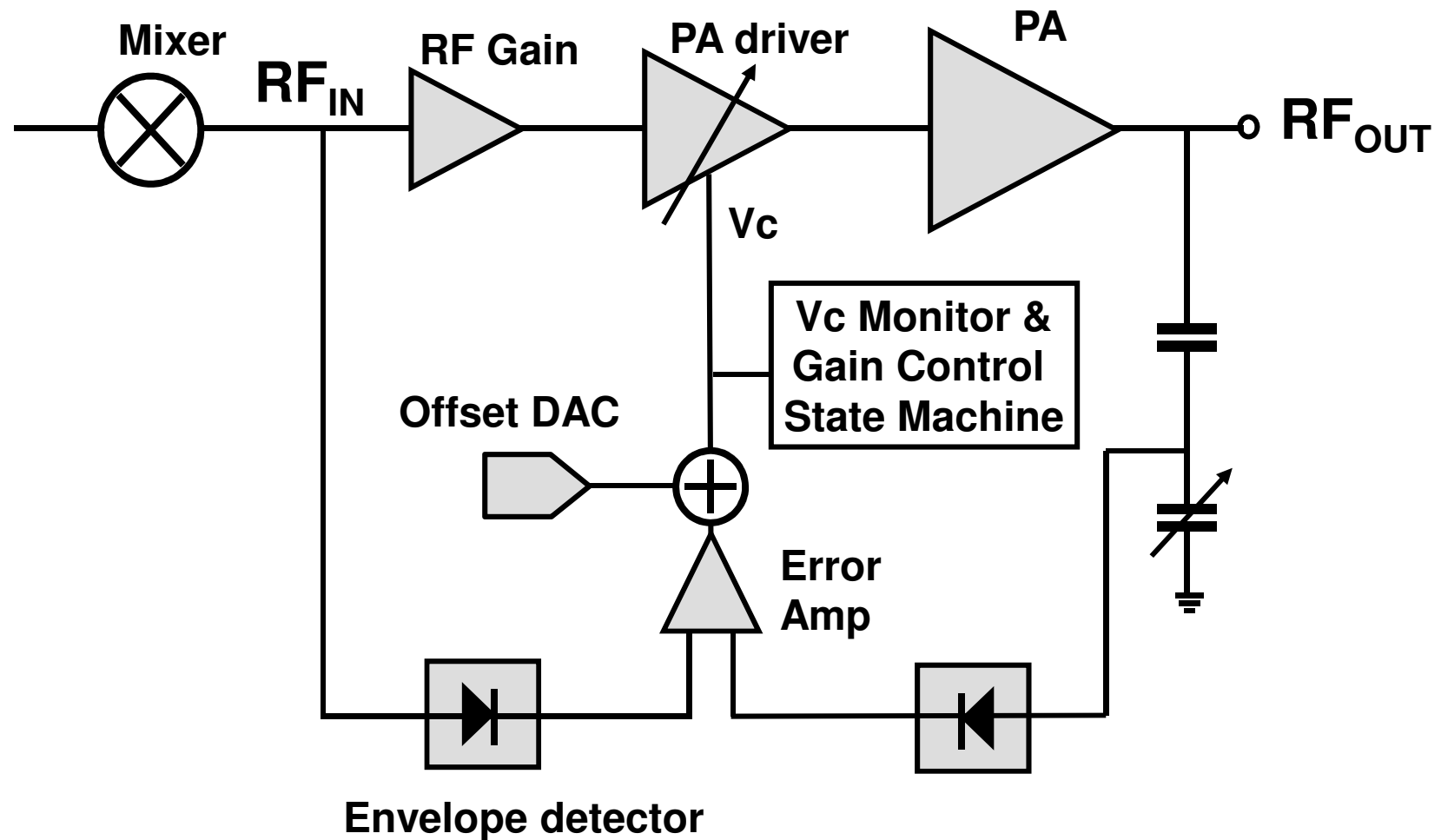




# Fast Envelope Detector

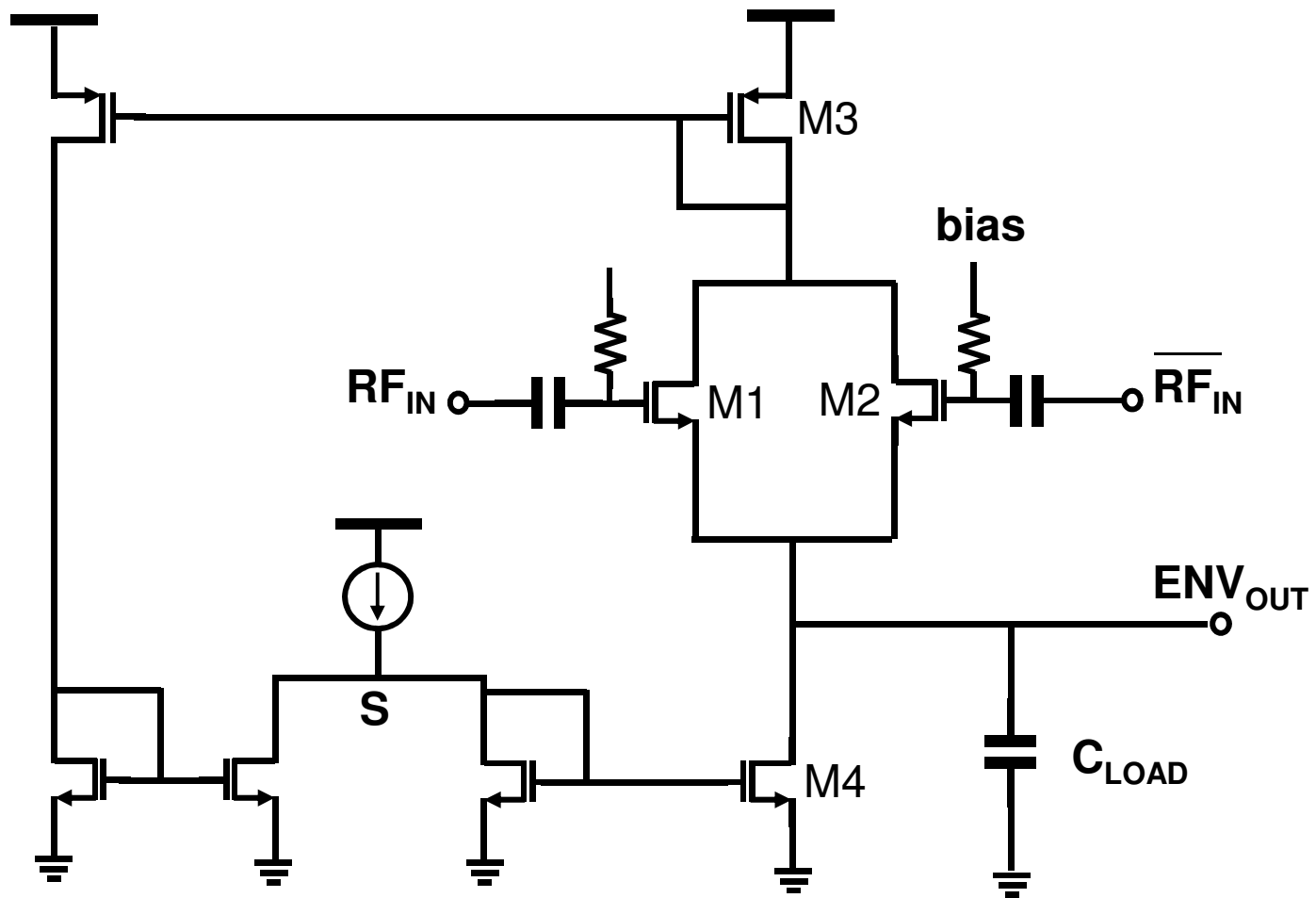


# PA Driver with Variable Load

 


# Sensitivity Measurements

System NF (LNA1/LNA2) = 5.5dB / 3.5dB


Data Rate	Sensitivity LNA1/LNA2 (dBm)
CCK 1Mbps	-97/-99
11g 54Mbps	-76/-78
HT20 65Mbps	-73/-75
HT40 135Mbps	-69/-71.5

 


# Output Power Measurements

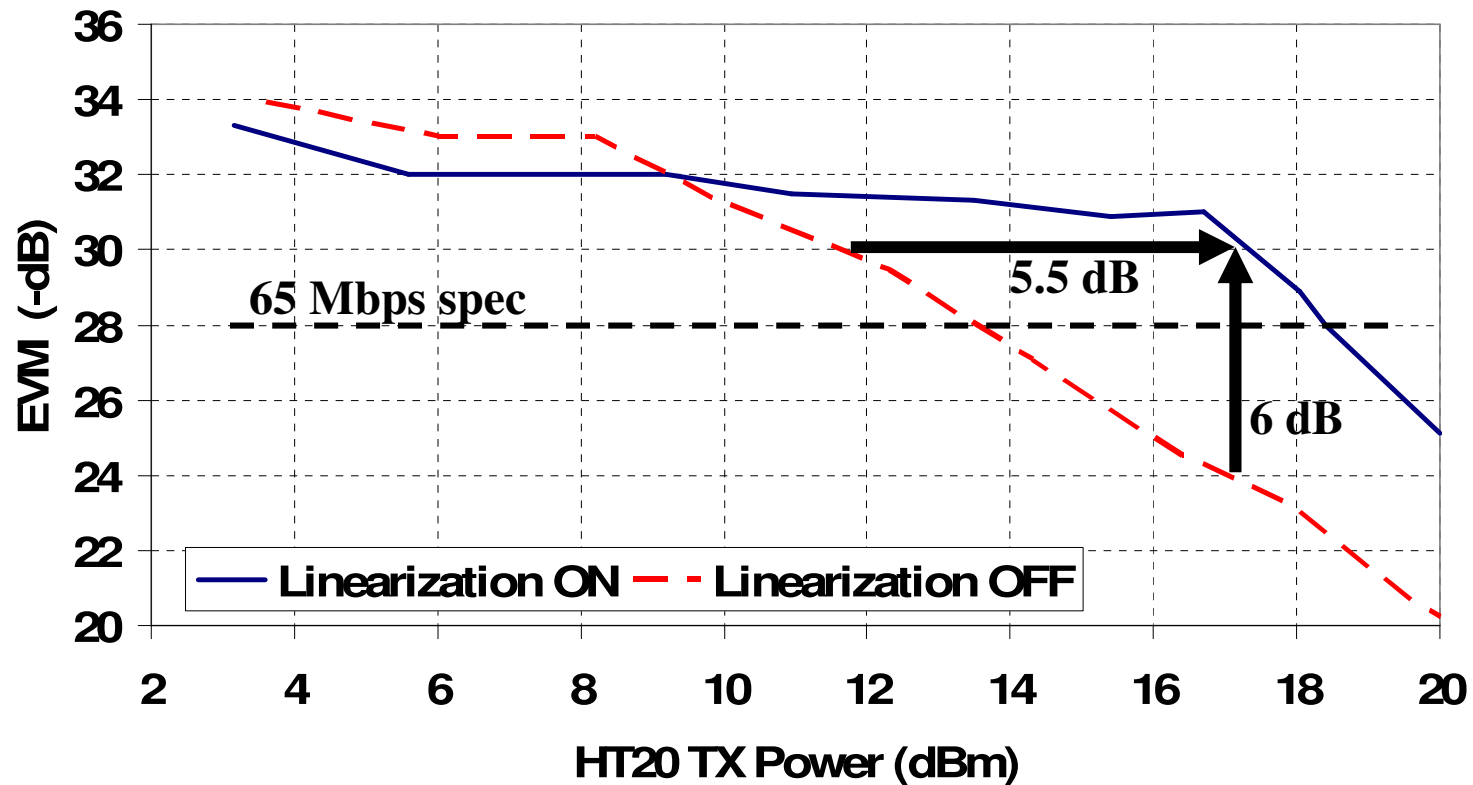
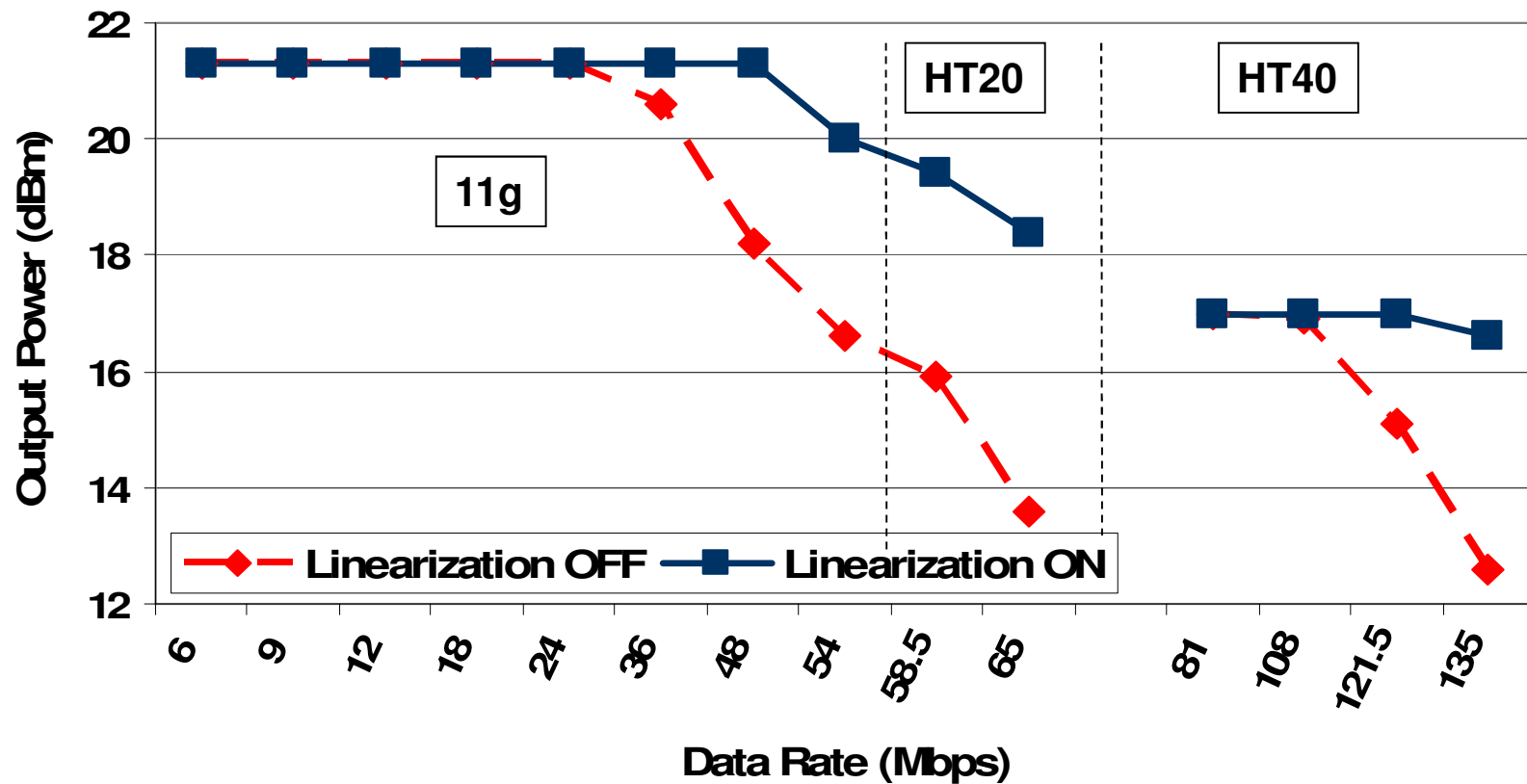
# Max EVM and Mask Compliant Power vs Data Rate



# Chip Micrograph

 

- 0.13 $\mu\text{m}$  CMOS
- 68 pin QFN package
- 19mm<sup>2</sup> Silicon Area
- Current Consumption from 3.3V
  - RX: 210mA
  - TX: 455mA @  
Pout=18.4dBm,  
HT20, EVM=-28dB

# Conclusions

---

- **CMOS has become the technology of choice for integrated radio systems**
- **Integrating a radio in mixed-Signal System-on-a-Chip is no longer a dream but a reality**
- **Wireless SoC can provide significant advantages in size, power, and cost**

# Continuing Challenges

---

- **Multi-mode radios to support several wireless standards**
- **RF design in scaled CMOS**
  - Reduced supply voltage: voltage, current, time...
  - nanometer transistors: leaky, low gm.ro
  - How to reduce area and power
  - More “digital assistance”
- **Challenges of radio designers have been, are, and will continue to be:**
  - Power consumption / Battery life
  - Range
  - Data rate
  - Cost



# Acknowledgments

---

- **Many of the slides are based on previous presentations from Qualcomm Atheros and Stanford University, especially those by:**

**Masoud Zargari,  
Manolis Terrovitis,  
Srenik Mehta,  
William Si,  
William McFarland,  
Lalitkumar Nathawad  
Richard Chang  
Amirpouya Kavousian**